



Building A RISC Microcontroller in an FPGA

- Name : Yap Zi He
- Course : 4 SEL
- Supervisor : PM Muhammad Mun'im
Ahmad Zabidi



Introduction

- **Reduce Instruction Set Computer (RISC)** is a new trend on computer design. The opposite and rather established trend is **Complex Instruction Set Computer (CISC)**, which consist lots of instruction sets, addressing modes, instruction formats and a number of possible instructions length. The complexity of the instruction makes the design more complicated. While RISC tend to reduce the complexity of the instructions set and thus make the design process easier.



Objectives

- The objectives of my project is to design a **RISC Microcontroller** using **VHDL** and implement it in an **FPGA**
- The instructions set and features are based on ATMEL AVR AT90S1200 RISC Microcontroller.

AT90S1200 At First Glance

- 89 Instructions
- 32 General Purpose Registers
- 2 IO Ports (15 pins)
- 1 x 8-bit Timer
- 1 x External Interrupt
- 1 x Analog Comparator



Scopes

- Implement the Complete AT90S1200 Microcontroller in an FPGA
- FPGA unimplementable features (analog comparator and internal pull-up resistors) and unnecessary feature (WatchDog Reset) will be ignored

What is the Challenges ?

1. **AREA** – the design must be able to fit into the targeted FPGA device, which is Altera EPF10K20RC240-4.
2. **SPEED** – the microcontroller must be able to run at a minimum clock speed of 10MHz.




Project Background

- “FPGA Implementation of a RISC microcontroller” – Wan Mohd Khalid

Problems :

1. Project is poorly documented
2. Design using both VHDL and schematics
3. Only 50% instructions designed (behavioral approach)
4. No peripheral features (port, timer, ext int)
5. Project size is too large, require 3 pieces of EPF10K20 !
6. FPGA implementation is not done


Approach

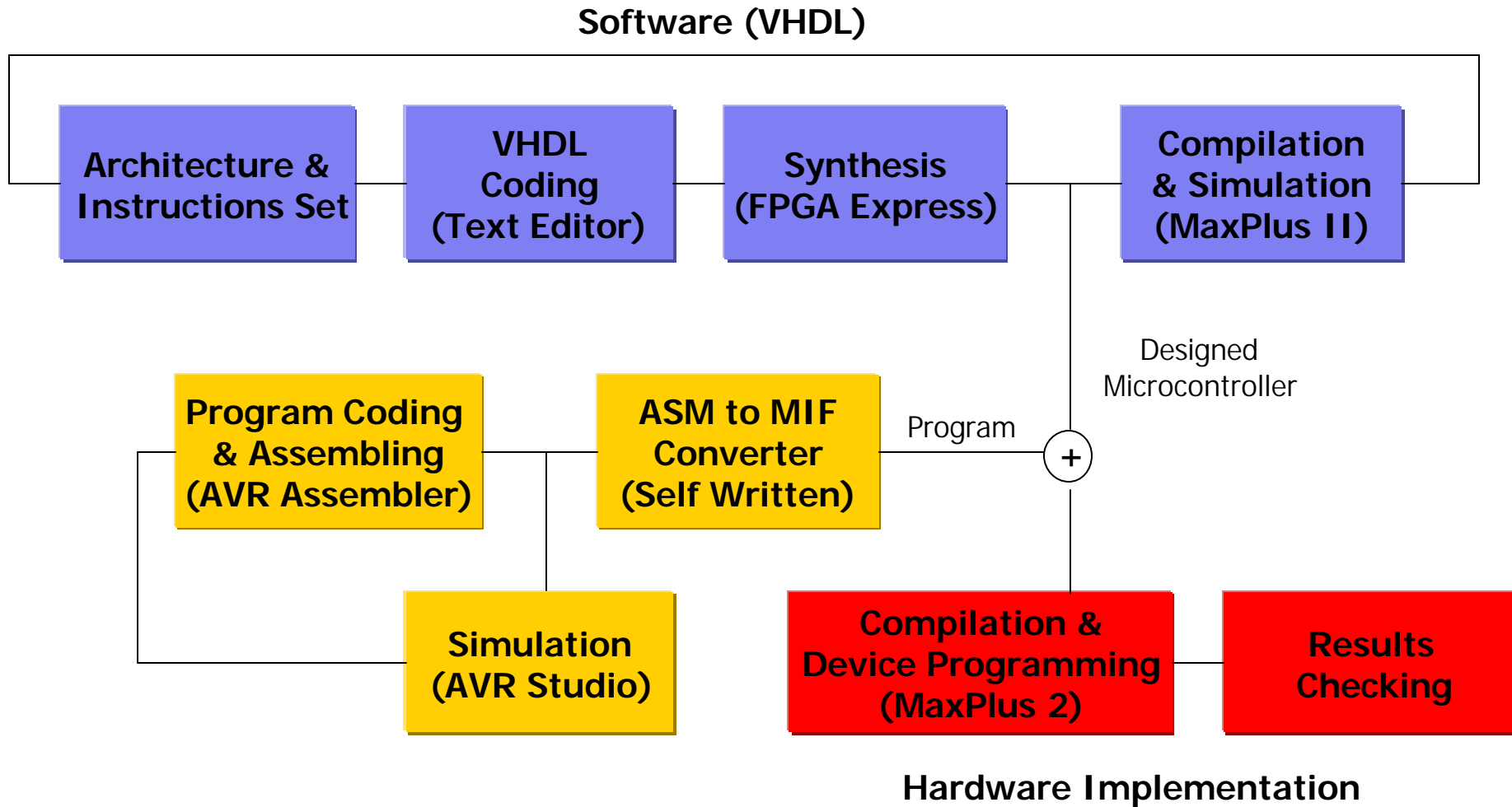

Architecture Overview



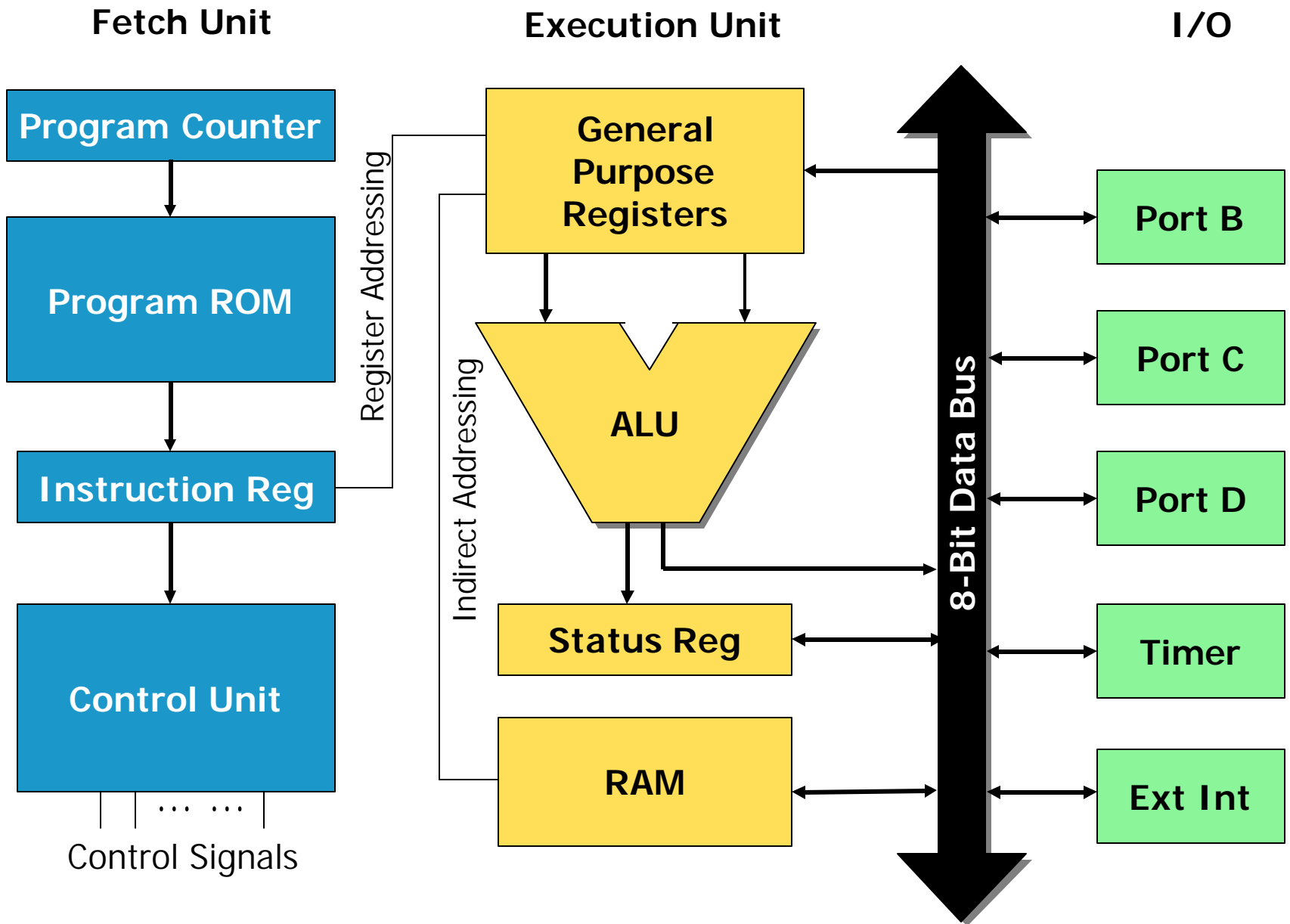- * All IO Ports are 8-bits width (3 ports = 24 pins)
- * External Interrupt and Timer external clock source share the same pin with pin D7



Instructions Cycle / Pipelines

Clock Cycle	1	2	3	4
1 st Instruction	Fetch	Execute		
2 nd instruction		Fetch	Execute	
3 rd instruction			Fetch	Execute


The 2 stage pipelines allowed 1 instruction to be executed on every clock cycle.



Project Highlight : Control Unit

- Designing the control unit is usually the most tedious task in digital system design
- In my design, the control unit is implemented with **Synchronous Mealy Model**.
- The advantages are :-
 1. The control signals are asserted according to clock transition rather than generated by the state as in Moore Model. Thus the control signals appear faster and will speed up the microcontroller.
 2. The control unit for the microcontroller has only **8 states** ! This is because control signals are lock to transition rather than the states. So all single cycle instructions can share the same state.

What is Synchronous Mealy Model ?

 

8 States Control Unit


Wait for Interrupt

Reset — EXE State

Single Cycle Instructions

2 Cycles Instructions

Branch Instructions (3 cycles)

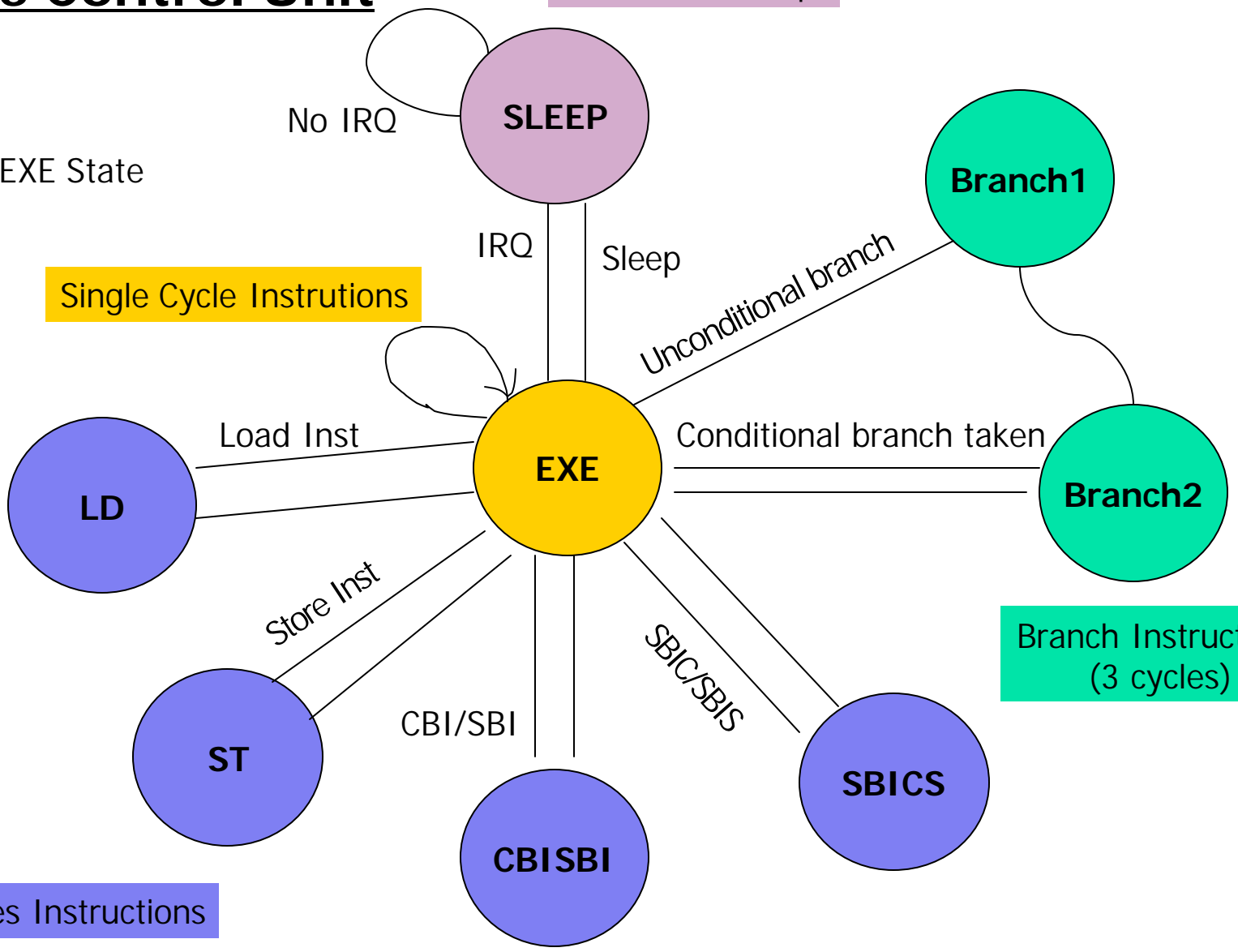



Instructions

The designed microcontroller is capable of executing 92 instructions.

Arithmetic and Logic Instructions (20) :-

ADD, ADC, SUB, SUBI, SBC, SBCI, AND, ANDI, OR, ORI, EOR, COM, NEG, SBR, CBR, INC, DEC, TST, CLR, SER

Branch and Skip Instructions (32) :-

RJMP, RCALL, RET, RETI, CPSE, CP, CPC, CPI, SBRC, SBRS, SBIC, SBIS, BRBS, BRBC, BREQ, BRNE, BRCS, BRCC, BRSH, BRLO, BRMI, BRPL, BRGE, BRLT, BRHS, BRHC, BRTS, BRTC, BRVS, BRVC, BRIE, BRID

Data Transfer Instructions (10) :-

LD Z, LD Z+, LD -Z, ST Z, ST Z+, ST -Z, MOV, LDI, IN, OUT

Bit and Bit Test Instructions (28) :-

SBI, CBI, LSL, LSR, ROL, ROR, ASR, SWAP, BSET, BCLR, BST, BLD, SEC, CLC, SEN, CLN, SEZ, CLZ, SEI, CLI, SES, CLS, SEV, CLV, SET, CLT, SHE, CLH

Misc Instructions (2) :-

NOP, SLEEP

> $20 + 32 + 10 + 28 + 2 = 92$ instructions



Results Achieved

1. VHDL coding and simulation for all the modules in the block diagram has been done successfully.
2. The design has been programmed into FPGA successfully.
3. The FPGA is now a microcontroller and is able to control some real applications (will be demo).

How about the challenges stated ?

AREA – The design fit into the targeted device successfully
(using 92% of EPF10K20RC240-4)

SPEED – The final design clock speed is 12 MHz (target is 10MHz)

AT90S1200 VS My Design

	AT90S1200	RISCMCU
Instructions	89	92
G.P Registers	32	16
Program ROM	512 words	512 words
IO Ports	2 (15 pins)	3 (24 pins)
Addressing Modes	5	8
Speed	4 MHz / 12 MHz	12 MHz*
8-bit Timer	1	1
External Interrupt	1	1
Analog Comparator	1	None
Implementation	CMOS	FPGA
SRAM	None	128 bytes

* 18 MHz can be achieved when implemented in the fastest device from the same family



Recommendations on Future Works

My design is based on AVR AT90S1200. There are many more members in the AVR family which contribute to more instructions and features. The next step will be adding these instructions and features into my design. Example:

Instructions – MUL, DIV, IJMP ...

Features – UART, SPI, 16-bit Timer (with input capture, output compare & PWM)



Conclusion

- The project has achieved all the objectives and fulfilled all the scope specified
- My main contribution is the VHDL source code, which is an AT90S1200 compatible RISC microcontroller