

# AMI and HDB1 Line Codes - VHDL Implementation.

Ribamar Santarosa, ribamar@gmail.com

Outubro/Novembro 2006.

## Abstract

Line codings are methods for coding digital data for making them less susceptible to signal losses during transmission. This project implements the AMI — Alternate Mark Inverse — and HDB1 — High Density Bipolar of order 1 codings. This file documents their implementation.

## 1 Specification.

**AMI.** This coding takes a binary sequency into a ternary sequency having the signals 0, +1, -1 by the following way:

- Inputs of 1 are coded as +1 or -1 alternately.
- Inputs of 0 are coded always as 0.
- Entradas iguais a zero são codificadas como zero;

Example:

```
Input
1 0 1 0 1 1 0 0 0 1 0 1 1 0 0 1 0 1 0 0 0 1 1 1
Output
+1 0 -1 0 +1 -1 0 0 0 +1 0 -1 +1 0 0 -1 0 +1 0 0 0 -1 +1 -1
```

**HDB1.** This coding takes a binary sequency into a ternary sequency having the signals 0, +1, -1 by the following way:

- Inputs of 1 are coded as either +1 or -1.
- Paired inputs of 0 are coded as either +1+1 or -1-1.
- Entradas iguais a zero, isoladas, isto é, seguidas de um e que não foram codificadas em conjunto com outro zero (formando +1+1 ou -1-1), são codificadas como zero;
- Isolated inputs of 0, ie, inputs of 0 not followed by 1 which weren't paired to another 0 (thus forming +1+1 or -1-1) are coded as 0.
- Outputs have always alternate signals. If the last output was -1 and the input is 00, the next output is coded as +1+1, if the last output was -1-1 and the input is 1, the next output is +1.

Example:

Input

1 0 1 0 1 1 0 0 0 1 0 1 1 0 0 1 0 1 0 0 0 0 1 1

Output

+1 0 -1 0 +1 -1 +1 +1 0 -1 0 +1 -1 +1 +1 -1 0 +1 -1 -1 +1 +1 -1 +1

## 2 AMI Encoder.

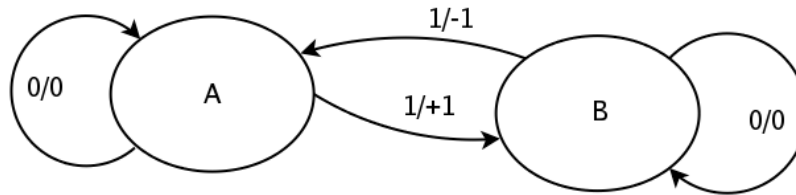


Figure 1: State Map.

Truth Table:

$q$	$e$	$S_0$	$S_1$	$q^+$
0	0	0	0	0
0	1	1	0	1
1	0	0	0	1
1	1	0	1	0

Karnaugh Map isn't necessary:

$$S_0 = e \cdot q'$$

$$S_1 = e \cdot q$$

$$q^+ = e \oplus q$$

## 3 AMI Decoder.

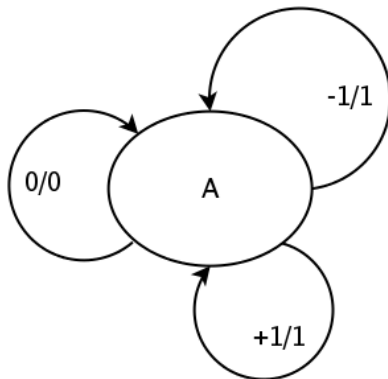


Figure 2: State Map.

Truth Table:

$e_0$	$e_1$	$S$
0	0	0
0	1	1
1	0	1
1	1	X

Karnaugh Map isn't necessary:

$$S = e_0 + e_1$$

## 4 HDB1 Encoder.

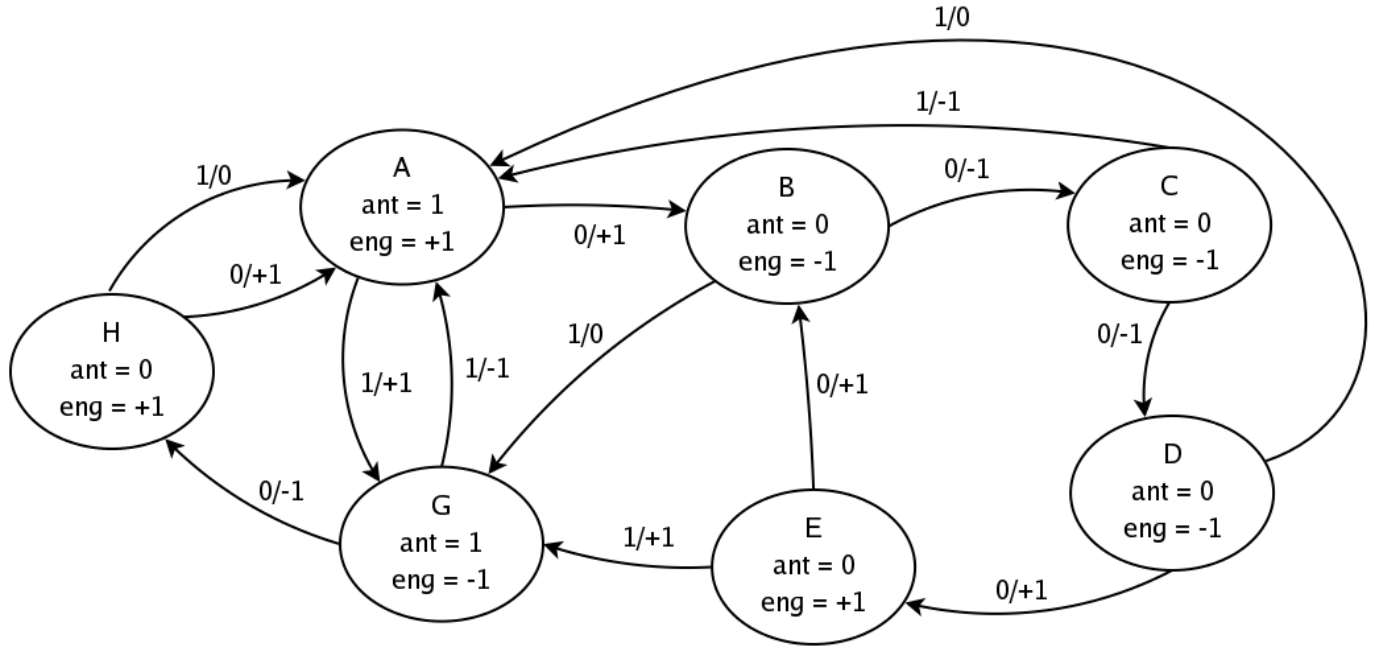


Figure 3: State Map.

Truth Table:

$E$	$q_0$	$q_1$	$q_2$	$q_0^+$	$q_1^+$	$q_2^+$	$S_0$	$S_1$
0	0	0	0	0	0	1	1	0
1	0	0	0	1	1	0	1	0
0	0	0	1	0	1	0	0	1
1	0	0	1	1	1	0	0	0
0	0	1	0	0	1	1	0	1
1	0	1	0	0	0	0	0	1
0	0	1	1	1	0	0	1	0
1	0	1	1	0	0	0	0	0
0	1	0	0	0	0	1	1	0
1	1	0	0	1	1	0	1	0
X	1	0	1	X	X	X	X	X
0	1	1	0	1	1	1	0	1
1	1	1	0	0	0	0	0	1
0	1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	0	1

		$Eq_0$			
		00	01	11	10
$q_0^+$ :	$q_1q_2$	00		1	1
		01	X	X	1
		11	1		
		10		1	

$$q_0^+ = E \cdot q_1' + E' \cdot q_0' \cdot q_1 \cdot q_2 + E' \cdot q_0 \cdot q_1 \cdot q_2'$$

		$Eq_0$			
		00	01	11	10
$q_1^+$ :	$q_1q_2$	00		1	1
		01	1	X	X
		11			
		10	1	1	

$$q_1^+ = E \cdot q_1' + q_1' \cdot q_2 + E' \cdot q_1 \cdot q_2'$$

		$Eq_0$			
		00	01	11	10
$q_2^+$ :	$q_1q_2$	00	1	1	
		01		X	X
		11			
		10	1	1	

$$q_2^+ = E' \cdot q_2'$$

		$Eq_0$				
		00	01	11	10	
$S_0:$	$q_1q_2$	00	1	1	1	1
		01		X	X	
		11	1	1		
		10				

$$S_0 = q_1' \cdot q_2' + E' \cdot q_1 \cdot q_2$$

		$Eq_0$			
		00	01	11	10
$S_1:$	$q_1q_2$	00	1	X	X
		01			
		11			
		10	1	1	1

$$S_1 = q_1 \cdot q_2' + E' \cdot q_1' \cdot q_2$$

## 5 HDB1 Decoder.

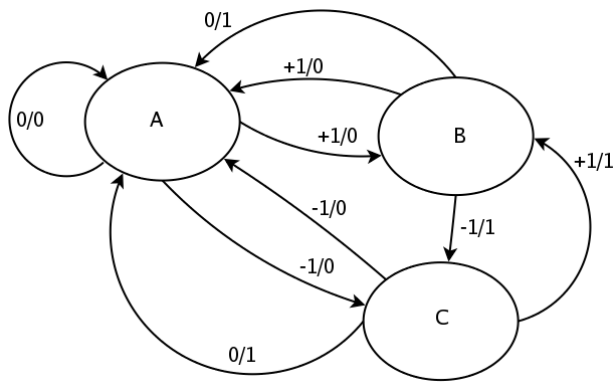


Figure 4: State Map.

Truth Table:

$e_1$	$e_0$	$q_1$	$q_0$	$q_0^+$	$q_1^+$	$S$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	X	X	X
0	1	0	0	0	1	0
0	1	0	1	0	0	0
0	1	1	0	0	1	1
0	1	1	1	X	X	X
1	0	0	0	0	1	0
1	0	0	1	1	0	1
1	0	1	0	0	0	0
1	0	1	1	X	X	X
1	1	0	0	X	X	X
1	1	0	1	X	X	X
1	1	1	0	X	X	X
1	1	1	1	X	X	X

		$q_1q_0$			
		00	01	11	10
$q_0:$	$e_0e_1$	00		X	
		01		X	
		11	X	X	X
		10		1	X

$$q_0^+ = q_0' \cdot e_0$$

		$q_1q_0$			
		00	01	11	10
$q_1:$	$e_0e_1$	00		X	
		01	1	X	1
		11	X	X	X
		10	1		X

$$q_1^+ = q_1' \cdot e_1$$

$S:$

		$q_1 q_0$			
		00	01	11	10
$e_1 e_2$	00		1	X	1
	01			X	1
	11	X	X	X	X
	10		1	X	

$$S = q_0 \cdot e'_0 + q_1 \cdot e'_1$$