

How to design your own CPU on FPGAs with VHDL

A Lecture by Dr. Juergen Sauermann

Copyright (C) 2009, 2010 by Dr. Juergen Sauermann

Note: Due to scaling, the figures (and some other things) in this PDF file look pretty bad. Please use the HTML version of this document instead. You can get the HTML version by one of the following:

- Go to <http://www.opencores.org> and log in.
- Go to the Projects page and select project "CPU Lecture" in the Soc section.
- Click Latest version: download
- Unpack the tar file (tar -xvzf)
- Open index.html with your browser

or:

- Check out the project: **svn co http://opencores.org/ocsvn/cpu_lecture/cpu_lecture**
- Open index.html with your browser

Table of Contents

1 INTRODUCTION AND OVERVIEW.....	1
1.1 Prerequisites.....	1
1.2 Other useful links.....	1
1.3 Structure of this Lecture.....	2
1.4 Naming Conventions.....	2
1.5 Directory Structure.....	2
1.6 Other Useful Tools.....	3
2 TOP LEVEL.....	4
2.1 Design Purpose.....	4
2.2 Top Level Design.....	4
2.3 General Structure of our VHDL Files.....	6
2.3.1 Header and Library Declarations.....	6
2.3.2 Entity Declaration.....	6
2.3.3 Entity Architecture.....	6
2.4 avr_fpga.vhd.....	6
2.4.1 Header and Library Declarations.....	7
2.4.2 Entity Declaration.....	8
2.4.3 Architecture of the Top Level Entity.....	8
2.5 Component Tree.....	14
3 DIGRESSION: PIPELINING.....	16
4 THE CPU CORE.....	22
5 OPCODE FETCH.....	27
5.1 Program Memory.....	29
5.2.1 Dual Port Memory.....	29
5.2.2 Look-ahead for two word instructions.....	29
5.2.3 Memory block instantiation and initialization.....	32
5.2.3 Delayed PC.....	34
5.3 Two Cycle Opcodes.....	34
5.4 Interrupts.....	35
6 DATA PATH.....	37
6.1 Register File.....	39
6.1.1 Register Pair.....	39
6.1.2 The Status Register.....	40
6.1.3 Register File Components.....	40
6.1.4 Addressing of General Purpose Registers.....	42
6.1.5 Addressing of General Purpose Register Pairs.....	42
6.1.6 Requirements on the Register File.....	42
6.1.7 Reading Registers or Register Pairs.....	42
6.1.8 Writing Registers or Register Pairs.....	45
6.1.9 Addressing Modes.....	48
6.2 Data memory.....	52
6.3 Arithmetic/Logic Unit (ALU).....	52
6.3.3 Arithmetic and Logic Functions.....	53
6.3.4 Output and Flag Multiplexing.....	54
6.3.5 Individual ALU Operations.....	55

Table of Contents

6 DATA PATH	
<u>6.3.5 Temporary Z and T Flags</u>57
<u>6.4 Other Functions</u>57
7 OPCODE DECODER60
<u>7.1 Inputs of the Opcode Decoder</u>60
<u>7.2 Outputs of the Opcode Decoder</u>60
<u>7.3 Structure of the Opcode Decoder</u>61
<u>7.4 Default Values for the Outputs</u>62
<u>7.5 Checklist for the Design of an Opcode</u>62
<u>7.6 Opcode Implementations</u>62
<u>7.6.1 The NOP instruction</u>62
<u>7.6.2 8-bit Monadic Instructions</u>62
<u>7.6.3 8-bit Dyadic Instructions, Register/Register</u>63
<u>7.6.4 8-bit Dyadic Instructions, Register/Immediate</u>65
<u>7.6.5 16-bit Dyadic Instructions</u>66
<u>7.6.6 Bit Instructions</u>66
<u>7.6.7 Multiplication Instructions</u>67
<u>7.6.8 Instructions Writing To Memory or I/O</u>68
<u>7.6.9 Instructions Reading From Memory or I/O</u>68
<u>7.6.10 Jump and Call Instructions</u>70
<u>7.6.11 Instructions Not Implemented</u>74
<u>7.7 Index of all Instructions</u>74
8 INPUT/OUTPUT77
<u>8.1 Interface to the CPU</u>77
<u>8.2 CLR Signal</u>77
<u>8.3 Connection the FPGA Pins</u>77
<u>8.4 I/O Read</u>78
<u>8.5 I/O Write</u>79
<u>8.6 Interrupts</u>80
<u>8.7 The UART</u>81
<u>8.7.1 The UART Baud Rate Generator</u>81
<u>8.7.2 The UART Transmitter</u>82
<u>8.7.3 The UART Receiver</u>83
9 TOOLCHAIN SETUP85
<u>8.1 Functional Simulation</u>87
<u>8.2 Timing Simulation and FPGA Configuration</u>89
<u>8.3 Downloading and Building the Tools</u>89
<u>8.4 Preparing the Memory Content</u>94
<u>8.5 Performing the Functional Simulation</u>96
<u>8.5.1 Preparing a Testbench</u>96
<u>8.5.2 Defining Memory Modules</u>97
<u>8.5.3 Creating the testbench executable</u>100
<u>8.6 Building the Design</u>102
<u>8.6.1 Creating an UCF file</u>102
<u>8.6.2 Synthesis and Implementation</u>103
<u>8.7 Creating a Programming File</u>104
<u>8.8 Configuring the FPGA</u>104

Table of Contents

<u>9 TOOLCHAIN SETUP</u>	
8.8.1 Configuring the FPGA via JTAG Boundary Scan.....	104
8.8.2 Flashing PROMs.....	104
<u>10 LISTING OF alu.vhd</u>	105
<u>11 LISTING OF avr_fpga.vhd</u>	112
<u>12 LISTING OF baudgen.vhd</u>	116
<u>13 LISTING OF common.vhd</u>	118
<u>14 LISTING OF cpu_core.vhd</u>	121
<u>15 LISTING OF data_mem.vhd</u>	126
<u>16 LISTING OF data_path.vhd</u>	130
<u>17 LISTING OF io.vhd</u>	135
<u>18 Listing of opc_deco.vhd</u>	139
<u>19 LISTING OF opc_fetch.vhd</u>	150
<u>20 LISTING OF prog_mem_content.vhd</u>	153
<u>21 LISTING OF prog_mem.vhd</u>	156
<u>22 LISTING OF reg_16.vhd</u>	161
<u>23 LISTING OF register_file.vhd</u>	163
<u>24 LISTING OF segment7.vhd</u>	170
<u>25 LISTING OF status_reg.vhd</u>	173
<u>26 LISTING OF uart_rx.vhd</u>	175
<u>27 LISTING OF uart_tx.vhd</u>	177
<u>28 LISTING OF RAMB4_S4_S4.vhd</u>	179
<u>29 LISTING OF test_tb.vhd</u>	182
<u>30 LISTING OF avr_fpga.ucf</u>	184
<u>31 LISTING OF Makefile</u>	185

Table of Contents

<u>32 LISTING OF hello.c.....</u>	186
<u>33 LISTING OF make_mem.cc.....</u>	187
<u>34 LISTING OF end_conv.cc.....</u>	190

1 INTRODUCTION AND OVERVIEW

This lecture describes in detail how you can design a CPU (actually an embedded system) in VHDL.

The CPU has an instruction set similar to the instruction set of the popular 8-bit CPUs made by **Atmel**. The instruction set is described in http://www.atmel.com/dyn/resources/prod_documents/doc0856.pdf. We use an existing CPU so that we can reuse a software tool chain (**avr-gcc**) for this kind of CPU and focus on the hardware aspects of the design. At the end of the lecture, however, you will be able to design your own CPU with a different instruction set.

We will not implement the full instruction set; only the fraction needed to explain the principles, and to run a simple "Hello world" program (and probably most C programs) will be described.

1.1 Prerequisites

Initially you will need two programs:

- **ghdl** from <http://ghdl.free.fr> (a free VHDL compiler and simulator) and
- **gtkwave** from <http://gtkwave.sourceforge.net> (a free visualization tool for the output of ghdl).

These two programs allow you to design the CPU and simulate its functions.

Later on, you will need a FPGA toolchain for creating FPGA design files and to perform timing simulations. For this lecture we assume that the free **Xilinx Webpack** tool chain is used (<http://www.xilinx.com>). The latest version of the Xilinx Webpack provides ISE 11 (as of Nov. 2009) but we used ISE 10.1 because we used an FPGA board providing a good old Spartan 2E FPGA (actually an xc2s300e device) which is no longer supported in ISE 11.

Once the CPU design is finished, you need a C compiler that generates code for the AVR CPU. For downloading **avr-gcc**, start here:

http://www.avrfreaks.net/wiki/index.php/Documentation:AVR_GCC#AVR-GCC_on_Uinx_and_Linux

In order to try out the CPU, you will need some FPGA board and a programming cable. We used a Memec "Spartan-IIIE LC Development Kit" board and an Avnet "Parallel Cable 3" for this purpose. These days you will want to use a more recent development environment. When the hardware runs, the final thing to get is a software toolchain, for example **avr-gcc** for the instruction set and memory layout used in this lecture. Optional, but rather helpful, is **eclipse** (<http://www.eclipse.org>) with the AVR plugin.

Another important prerequisite is that the reader is familiar with VHDL to some extent. You do not need to be a VHDL expert in order to follow this lecture, but you should not be a VHDL novice either.

1.2 Other useful links.

A good introduction into VHDL design with open source tools can be found here:

http://www.armadeus.com/wiki/index.php?title=How_to_make_a_VHDL_design_in_Ubuntu/Debian

1.3 Structure of this Lecture

This lecture is organized as a sequence of lessons. The first lessons will describe the VHDL files of the CPU design in a top-down fashion.

Then follows a lesson on how to compile, simulate and build the design.

Finally there is a listing of all design files with line numbers. Pieces of these design files will be spread over the different lessons and explained there in detail. In the end, all code lines in the appendix should have been explained, with the exception of comments, empty lines and the like. Repetitions such as the structure of VHDL files or different opcodes that are implemented in the same way, will only be described once.

All source files are provided (without line numbers) in a tar file that is stored next to this lecture.

1.4 Naming Conventions

In all lessons and in the VHDL source files, the following conventions are used:

VHDL entities and components and VHDL keywords are written in **lowercase**. Signal names and variables are written in **UPPERCASE**. Each signal has a prefix according to the following rules:

I_ for inputs of a VHDL entity.

Q_ for outputs of a VHDL entity.

L_ for local signals that are generated by a VHDL construct (e.g. by a signal assignment).

x_ with an uppercase x for signals **generated** by an instantiated entity.

For every instantiated component we choose an uppercase letter x (other than I, L, or Q). All signals driven by the component then get the prefix **Q_** (if the instantiated component drives an output of the entity being defined) or the prefix **x_** (if the component drives an internal signal).

Apart from the prefix, we try to keep the name of a signal the same across different VHDL files. Unless the prefix matters, we will use the signal name **without its prefix** in our descriptions.

Another convention is that we use one VHDL source file for every entity that we define and that the name of the file (less the .vhd extension) matches the entity name.

1.5 Directory Structure

Create a directory of your choice. In that directory, **mkdir** the following sub-directories:

app for building the program that will run on the CPU (i.e. **hello.c**)

simu for object files generated by **ghdl**

src for VHDL source files of the CPU and **avr_fpga.ucf**

test for a VHDL testbench

tools for tools **end_conv** and **make_mem**

work working directory for **ghdl**

Initially the directory should look like this:

1 INTRODUCTION AND OVERVIEW

```
# ls -R .
./app:
hello.c

./simu:

./src:
alu.vhd
avr_fpga.ucf
avr_fpga.vhd
baudgen.vhd
common.vhd
COPYING
cpu_core.vhd
data_mem.vhd
data_path.vhd
io.vhd
opc_deco.vhd
opc_fetch.vhd
prog_mem_content.vhd
prog_mem.vhd
reg_16.vhd
register_file.vhd
segment7.vhd
status_reg.vhd
uart_rx.vhd
uart_tx.vhd
uart.vhd

./test:
RAMB4_S4_S4.vhd
test_tb.vhd

./tools:
end_conv.cc
make_mem.cc

./work:
```

1.6 Other Useful Tools

This lecture was prepared with 3 excellent tools:

- **vim** 7.1.38 for preparing the text of the lecture,
- **txt2html** 2.46 for converting the text into html, and
- **dia** 0.5 for drawing the figures.

2 TOP LEVEL

This lesson defines what we want to create and the top level VHDL file for it.

2.1 Design Purpose

We assume that the purpose of the design is to build an FPGA with the following features:

- a CPU similar to the Atmel ATmega8,
- a serial port with a fixed baud rate, and
- an output for a single digit 7-segment display.

It is assumed that a suitable hardware exists.


2.2 Top Level Design

A CPU with I/O is a somewhat complicated beast. In order to tame it, we break it down into smaller and smaller pieces until the pieces become trivial.

The trick is to perform the breakdown at points where the connection between the pieces is weak (meaning that it consists of only a few signals).

The top level of our FPGA design, and a few components around the FPGA, looks like this:

2 TOP LEVEL

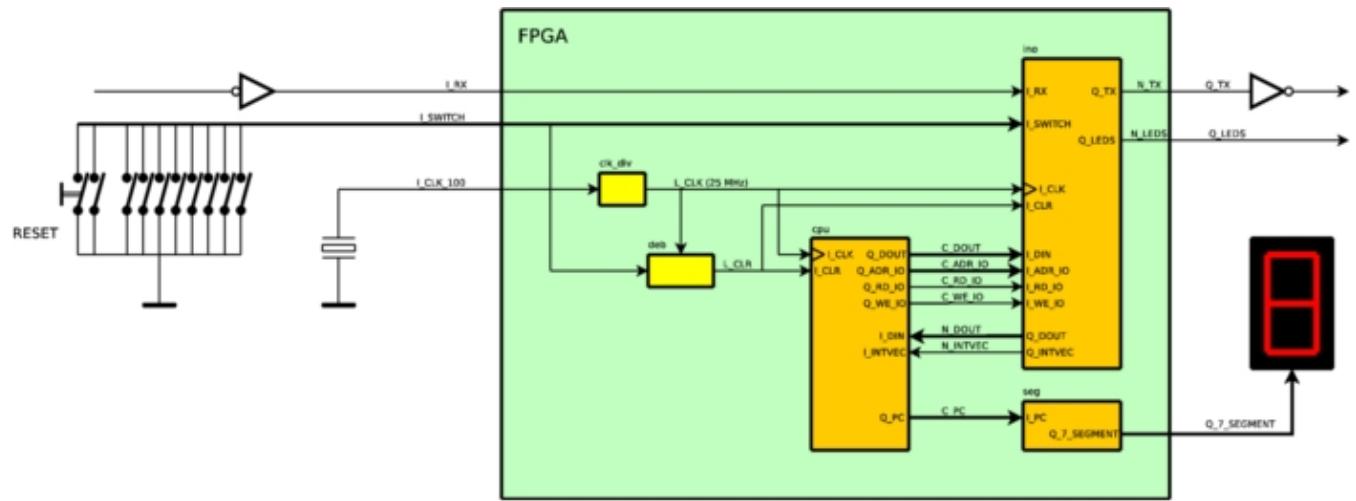

This design consists of 2 big sub-components **cpu** and **ino**, a small sub-component **seg**, and some local processes like **clk_div** and **deb** that are not broken down in other VHDL files, but rather written directly in VHDL.

cpu and **ino** are described in lessons 4 and 8.

seg is a debug component that has the current program counter (**PC**) of the CPU as input and displays it as 4 hex digits that show up one by one with a short break between every sequence of hex digits. Since **seg** is rather board specific, we will not describe it in detail in this lecture.

The local processes are described further down in this lesson. Before that we explain the structure that will be used for all VHDL source file.

2.3 General Structure of our VHDL Files

2.3.1 Header and Library Declarations

Each VHDL source file starts with a comment containing a copyright notice (all files are released under the GPL) and the purpose of the file. Then follows a declaration of the libraries being used.

2.3.2 Entity Declaration

After the header and libraries, the entity that is defined in the VHDL file is declared. We declare one entity per VHDL file. The declaration consists of the name of the entity, the inputs, and the outputs of the entity. In this declaration the order of input and outputs does not matter, but we try to stick to the convention to declare the inputs before the outputs.

There is one exception: the file **common.vhd** does not define an entity, but a VHDL package. This package contains the definitions of constants that are used in more than one VHDL source file. This ensures that changes to these constants happen in all files using them.

2.3.3 Entity Architecture

Finally, the architecture of the entity is specified. The architecture consists of a header and a body.

In the header we declare the components, functions, signals, and constants that are used in the body.

The body defines how the items declared in the header are being used (i.e. instantiated, interconnected etc.). This body contains, so to say, the "intelligence" of the design.

2.4 avr_fpga.vhd

The top level of our design is defined in **avr_fpga.vhd**. Since this is our first VHDL file we explain it completely, line by line. Later on, we will silently skip repetitions of parts that have been described in other files or that are very similar.

2.4.1 Header and Library Declarations

avr_fpga.vhd starts with a copyright header.

```

1  -----
2  --
3  -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann
4  --
5  -- This code is free software: you can redistribute it and/or modify
6  -- it under the terms of the GNU General Public License as published by
7  -- the Free Software Foundation, either version 3 of the License, or
8  -- (at your option) any later version.
9  --
10 -- This code is distributed in the hope that it will be useful,
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
13 -- GNU General Public License for more details.
14 --
15 -- You should have received a copy of the GNU General Public License
16 -- along with this code (see the file named COPYING).
17 -- If not, see http://www.gnu.org/licenses/.
18 --
19 -----
20 -----
21 --
22 -- Module Name:      avr_fpga - Behavioral
23 -- Create Date:     13:51:24 11/07/2009
24 -- Description:    top level of a CPU
25 --
26 -----
27

```

src/avr_fpga.vhd

The libraries used are more or less the same in all VHDL files:

```

28 library IEEE;
29 use IEEE.STD_LOGIC_1164.ALL;
30 use IEEE.STD_LOGIC_ARITH.ALL;
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;
32

```

src/avr_fpga.vhd

The only Xilinx specific components needed for this lecture are the block RAMs. For functional simulation we provide compatible components written in VHDL. For FPGAs from other vendors you can probably include their FPGA libraries, but we have not tested this.

2.4.2 Entity Declaration

For a top level entity, the inputs and outputs of the entities are the pins of the FPGA.

For a lower level entity, the inputs and outputs of the entity are associated ("connected") with the inputs and outputs of the instance of the entity in a higher level entity. For this to work, the inputs and outputs of the declaration should match the component declaration in the architecture of another entity that instantiates the entity being declared.

Since we discuss the top-level, our inputs and outputs are pins of the FPGA. The top level entity is declared like this:

```

33      entity avr_fpga is
34          port (
35              I_CLK_100      : in  std_logic;
36              I_SWITCH      : in  std_logic_vector(9 downto 0);
37              I_RX          : in  std_logic;
38              Q_7_SEGMENT   : out std_logic_vector(6 downto 0);
39              Q_LEDS        : out std_logic_vector(3 downto 0);
40              Q_TX          : out std_logic);

```

src/avr_fpga.vhd

We therefore have the following FPGA pins:

Pin	Purpose
I_CLK_100	a 100 MHz Clock from the board.
I_SWITCH	a 8 bit DIP switch and two single push-buttons.
I_RX	the serial input of our UART.
Q_7_SEGMENT	7 lines to the LEDs of a 7-segment display.
Q_LEDS	4 lines to single LEDs
Q_TX	the serial output of our UART.

The lower 8 bits of **SWITCH** come from a DIP switch while the upper two bits come from two push-buttons. The two push-buttons are used as reset buttons, while the DIP switch goes to the I/O component from where the CPU can read the value set on the switch.

2.4.3 Architecture of the Top Level Entity

The architecture has a head and a body, The head starts with the **architecture** keyword. The body starts with **begin** and ends with **end**, like this:

```
43      architecture Behavioral of avr_fpga is
```

2 TOP LEVEL

```
src/avr_fpga.vhd

107      begin

src/avr_fpga.vhd

184          Q_TX      <= N_TX;

src/avr_fpga.vhd
```

2.4.3.1 Architecture Header

As we have seen in the first figure in this lesson, the top level uses 3 components: **cpu**, **io**, and **seg**. These components have to be declared in the header of the architecture. The architecture contains component declarations, signal declarations and others. We normally declare components and signals in the following order:

- declaration of functions
- declaration of constants
- declaration of the first component (type)
- declaration of signals driven by (an instance of) the first component
- declaration of the second component (type)
- declaration of signals driven by (an instance of) the second component
- ...
- declaration of signals driven by local processes and the like.

The first component declaration **cpu_core** and the signals driven by its instances are:

```
45  component cpu_core
46      port (  I_CLK        : in  std_logic;
47                I_CLR        : in  std_logic;
48                I_INTVEC    : in  std_logic_vector( 5 downto 0);
49                I_DIN        : in  std_logic_vector( 7 downto 0);
50
51                Q_OPC        : out std_logic_vector(15 downto 0);
52                Q_PC         : out std_logic_vector(15 downto 0);
53                Q_DOUT       : out std_logic_vector( 7 downto 0);
54                Q_ADR_IO     : out std_logic_vector( 7 downto 0);
55                Q_RD_IO      : out std_logic;
56                Q_WE_IO      : out std_logic);
57  end component;
58
59  signal  C_PC         : std_logic_vector(15 downto 0);
60  signal  C_OPC        : std_logic_vector(15 downto 0);
61  signal  C_ADR_IO     : std_logic_vector( 7 downto 0);
62  signal  C_DOUT       : std_logic_vector( 7 downto 0);
63  signal  C_RD_IO      : std_logic;
64  signal  C_WE_IO      : std_logic;
```

2 TOP LEVEL

src/avr_fpga.vhd

The second component declaration **io** and its signals are:

```
66      component io
67          port ( I_CLK      : in  std_logic;
68                  I_CLR      : in  std_logic;
69                  I_ADDR_IO  : in  std_logic_vector( 7 downto 0);
70                  I_DIN      : in  std_logic_vector( 7 downto 0);
71                  I_RD_IO    : in  std_logic;
72                  I_WE_IO    : in  std_logic;
73                  I_SWITCH   : in  std_logic_vector( 7 downto 0);
74                  I_RX       : in  std_logic;
75
76                  Q_7_SEGMENT : out std_logic_vector( 6 downto 0);
77                  Q_DOUT     : out std_logic_vector( 7 downto 0);
78                  Q_INTVEC   : out std_logic_vector(5 downto 0);
79                  Q_LEDS     : out std_logic_vector( 1 downto 0);
80                  Q_TX       : out std_logic);
81      end component;
82
83      signal N_INTVEC      : std_logic_vector( 5 downto 0);
84      signal N_DOUT        : std_logic_vector( 7 downto 0);
85      signal N_TX          : std_logic;
86      signal N_7_SEGMENT   : std_logic_vector( 6 downto 0);
```

src/avr_fpga.vhd

Note: Normally we would have used **I_** as a prefix for signals driven by instance **ino** of **io**. This conflicts, however, with the prefix reserved for inputs and we have used the next letter **n** of **ino** as prefix instead.

The last component is **seg**:

```
88      component segment7
89          port ( I_CLK      : in  std_logic;
90
91                  I_CLR      : in  std_logic;
92                  I_OPC      : in  std_logic_vector(15 downto 0);
93                  I_PC       : in  std_logic_vector(15 downto 0);
94
95                  Q_7_SEGMENT : out std_logic_vector( 6 downto 0));
96      end component;
97
98      signal S_7_SEGMENT   : std_logic_vector( 6 downto 0);
```

src/avr_fpga.vhd

2 TOP LEVEL

The local signals, which are not driven by any component, but by local processes and inputs of the entity, are:

```
100      signal L_CLK          : std_logic := '0';
101      signal L_CLK_CNT       : std_logic_vector( 2 downto 0 ) := "000";
102      signal L_CLR           : std_logic;           -- reset, active low
103      signal L_CLR_N         : std_logic := '0';    -- reset, active low
104      signal L_C1_N          : std_logic := '0';    -- switch debounce, active low
105      signal L_C2_N          : std_logic := '0';    -- switch debounce, active low
106
107      begin
src/avr_fpga.vhd
```

The **begin** keyword in the last line marks the end of the header of the architecture and the start of its body.

2.4.3.2 Architecture Body

We normally use the following order in the architecture body:

- components instantiated
- processes
- local signal assignments

Thus the architecture body is more or less using the same order as the architecture header. The component instantiations instantiate one or more instances of a component type and connect the "ports" of the instantiated component to the signals in the architecture.

The first component declared was **cpu** so we also instantiate it first:

```
109      cpu : cpu_core
110      port map(  I_CLK        => L_CLK,
111                  I_CLR        => L_CLR,
112                  I_DIN        => N_DOUT,
113                  I_INTVEC     => N_INTVEC,
114
115                  Q_ADR_IO     => C_ADR_IO,
116                  Q_DOUT       => C_DOUT,
117                  Q_OPC        => C_OPC,
118                  Q_PC         => C_PC,
119                  Q_RD_IO      => C_RD_IO,
120                  Q_WE_IO      => C_WE_IO);
```

```
src/avr_fpga.vhd
```

2 TOP LEVEL

The first line instantiates a component of type **cpu_core** and calls the instance **cpu**. The following lines map the names of the ports in the component declaration (in the architecture header) to either inputs of the entity, outputs of the entity, or signals declared in the architecture header.

We take **cpu** as an opportunity to explain our naming convention for signals. Our rule for entity inputs and outputs has the consequence that all left sides of the port map have either an **I_** prefix or an **O_** prefix. This follows from the fact that a component instantiated in one architecture corresponds to an entity declared in some other VHDL file and there the **I_** or **O_** convention applies,

The next observation is that all component outputs either drive an entity output or a local signal that starts with the letter chosen for the instantiated component. This is the **C_** in the **cpu** case. The **cpu** does not drive an entity output directly (so all outputs map to **C_** signals), but in the **io** outputs there is one driving an entity output (see below).

Finally the component inputs can be driven from more or less anywhere, but from the prefix (**L_** or not) we can see if the signal is directly driven by another component (when the prefix is not **L_**) or by some logic defined further down in the architecture (signal assignments, processes).

Thus for the **cpu** component we can already tell that this component drives a number of local signals (that are not entity outputs but inputs to other components or local processes)> These signals are those on the right side of the port map starting with **C_**. We can also tell that there are some local processes generating a clock signal **L_CLK** and a reset signal **L_CLR**, and the **ino** component (which uses prefix **N_**) drives an interrupt vector **N_INTVEC** and a data bus **N_DOUT**.

The next two components being instantiated are **ino** of type **io** and **seg** of type **segment7**:

```
122      ino : io
123      port map(  I_CLK      => L_CLK,
124                  I_CLR      => L_CLR,
125                  IADR_IO   => CADR_IO,
126                  IDIN      => CDOUT,
127                  IRD_IO    => CRD_IO,
128                  I_RX       => I_RX,
129                  ISWITCH   => ISWITCH(7 downto 0),
130                  IWE_IO    => CWE_IO,
131
132                  Q7_SEGMENT => N7_SEGMENT,
133                  QDOUT     => NDOUT,
134                  QINTVEC   => NINTVEC,
135                  QLEDS     => QLEDS(1 downto 0),
136                  QTX        => NTX;
137
138      seg : segment7
139      port map(  I_CLK      => L_CLK,
140                  ICLR      => LCLR,
141                  IOPC      => COPC,
142                  IPC       => CPC,
143
144                  Q7_SEGMENT => S7_SEGMENT);
```

src/avr_fpga.vhd

2 TOP LEVEL

Then come the local processes. The first process divides the 100 MHz input clock from the board into a 25 MHz clock used by the CPU. The design can, with some tuning of the timing optimizations, run at 33 MHz, but for our purposes we are happy with 25 MHz.

```
148      clk_div : process(I_CLK_100)
149      begin
150          if (rising_edge(I_CLK_100)) then
151              L_CLK_CNT      <= L_CLK_CNT + "001";
152              if (L_CLK_CNT = "001") then
153                  L_CLK          <= '1';
154              elsif (L_CLK_CNT = "100") then
155                  L_CLK          <= '0';
156                  L_CLK_CNT      <= "000";
157              end if;
src/avr_fpga.vhd
```

The second process is **deb**. It debounces the push-buttons used to reset the **cpu** and **ino** components. When either button is pushed ('0' on **SWITCH(8)** or **SWITCH(9)**) then **CLR_N** goes low immediately and stays low for two more cycles after the button was released.

```
161      -- reset button debounce process
162      --
163      deb : process(L_CLK)
164      begin
165          if (rising_edge(L_CLK)) then
166              -- switch debounce
167              if ((I_SWITCH(8) = '0') or (I_SWITCH(9) = '0')) then      -- pushed
168                  L_CLR_N      <= '0';
169                  L_C2_N       <= '0';
170                  L_C1_N       <= '0';
171              else
172                  L_CLR_N      <= L_C2_N;                                -- released
173                  L_C2_N       <= L_C1_N;
174                  L_C1_N       <= '1';
175          end if;
src/avr_fpga.vhd
```

Finally we have the signals driven directly from other signals. This kind of signal assignments are the same as processes, but use a simpler syntax for frequently used logic.

2 TOP LEVEL

```
177      end process;
178
179      L_CLR      <= not L_CLR_N;
180
181      Q_LEDS(2)    <= I_RX;
182      Q_LEDS(3)    <= N_TX;


src/avr_fpga.vhd
```

CLR is generated by inverting **CLR_N**. The serial input and the serial output are visualized by means of two LEDs. The 7 segment output can be driven from two sources: from a software controlled I/O register in the I/O unit, or from the seven segment component (that shows the current PC and opcode) being executed. The latter component is quite useful for debugging purposes.

Note: We use a **_N** suffix to denote an active low signal. Active low signals normally come from some FPGA pin since inside the FPGA active low signals have no advantage over active high signals. In the good old TTL days active low signals were preferred for strobe signals since the HIGH to LOW transition in TTL was faster than the LOW to high transition. Some active low signals we see today are left-overs from those days. Another common case is switches and push-buttons that are held high with a pull-up resistor when open and short-cut to ground when the switch is closed.

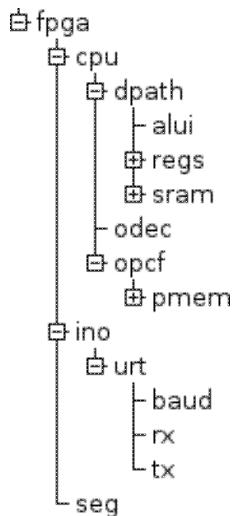2.5 Component Tree

The following figure shows the breakdown of almost all components in our design. Only the memory modules in **sram** and **pmem** and the individual registers in **regs** are hidden because they would blow up the structure without providing too much information.



We have already discussed the top level **fpga** and its 3 components **cpu**, **ino**, and **seg**.

2 TOP LEVEL

The **cpu** will be further broken down into a data path **dpath**, an opcode decode **odec**, and an opcode fetch **opcf**. The data path consist of a 16-bit ALU **alui**, a register file **regs**, and a data memory **sram**. The opcode fetch contains a program counter **pcnt** and a program memory **pmem**.

The **ino** contains a **uart** that is further broken down into a baud rate generator **baud**, a serial receiver **rx**, and a serial transmitter **tx**.


3 DIGRESSION: PIPELINING

In this short lesson we will give a brief overview of a design technique known as pipelining. Most readers will already be familiar with it; those readers should take a day off or proceed to the next lesson.

Assume we have a piece of combinational logic that happens to have a long propagation delay even in its fastest implementation. The long delay is then caused by the slowest path through the logic, which will run through either many fast elements (like gates) or a number of slower elements (like adders or multipliers), or both.

That is the situation where you should use pipelining. We will explain it by an example. Consider the circuit shown in the following figure.

3 DIGRESSION: PIPELINING

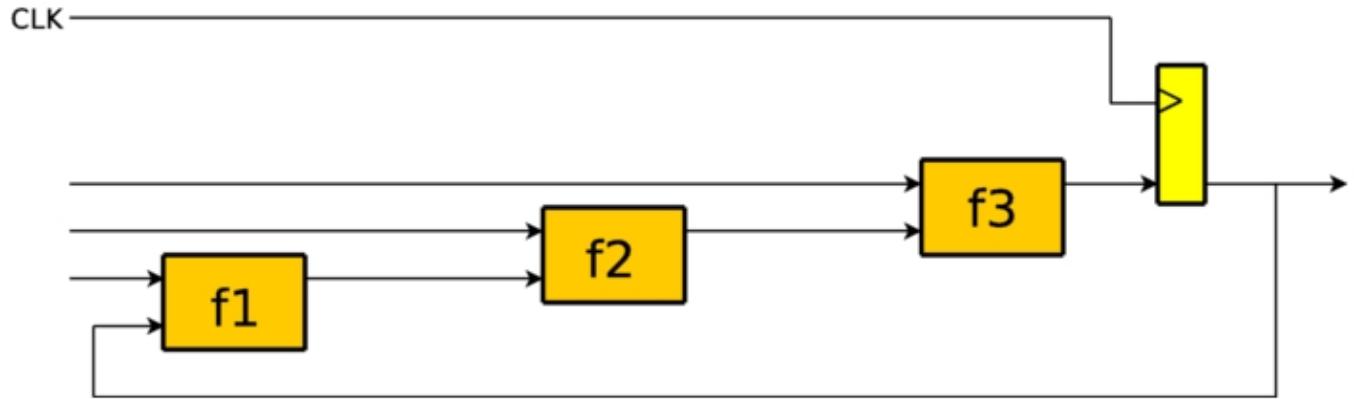


The circuit is a sequential logic which consists of 3 combinational functions f_1 , f_2 , and f_3 and a flip-flop at the output of f_3 .

Let t_1 , t_2 , and t_3 be the respective propagation delays of f_1 , f_2 , and f_3 . Assume that the slowest path of the combinational logic runs from the upper input of f_1 towards the output of f_3 . Then the total delay of the combinational is $t = t_1 + t_2 + t_3$. The entire circuit cannot be clocked faster than with frequency $1/t$.

Now pipelining is a technique that slightly increases the delay of a combinational circuit, but thereby allows different parts of the logic at the same time. The slight increase in total propagation delay is more than compensated by a much higher throughput.

3 DIGRESSION: PIPELINING

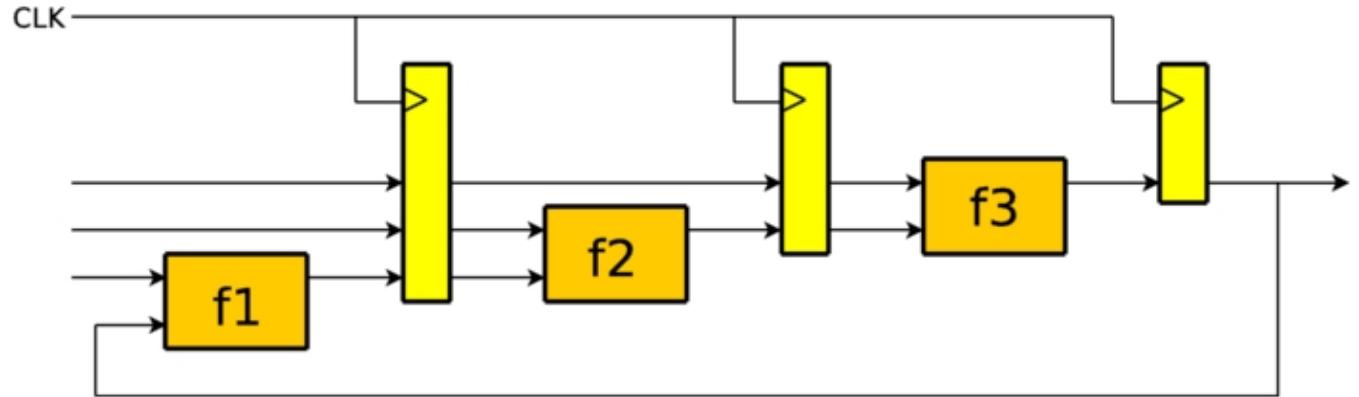Pipelining divides a complex combinational logic with an accordingly long delay into a number of stages and places flip-flops between the stages as shown in the next figure.



The slowest path is now $\max(t_1, t_2, t_3)$ and the new circuit can be clocked with frequency $1/\max(t_1, t_2, t_3)$ instead of $1/(t_1 + t_2 + t_3)$. If the functions f_1 , f_2 , and f_3 had equal propagation delays, then the max. frequency of the new circuit would have tripled compared to the old circuit.


It is generally a good idea when using pipelining to divide the combinational logic that shall be pipelined into pieces with similar delay. Another aspect is to divide the combinational logic at places where the number of connections between the pieces is small since this reduces the number of flip-flops that are being inserted.

3 DIGRESSION: PIPELINING

The first design of the CPU described in this lecture had the opcode decoding logic (which is combinational) and the data path logic combined. That design had a worst path delay of over 50 ns (and hence a max. frequency of less than 20 MHz). After splitting of the opcode decoder, the worst path delay was below 30 ns which allows for a frequency of 33 MHz. We could have divided the pipeline into even more stages (and thereby increasing the max. frequency even further). This would, however, have obscured the design so we did not do it.

The reason for the improved throughput is that the different stages of a pipeline work in parallel while without pipelining the entire logic would be occupied by a single operation. In a pipeline the single operation is often displayed like this (one color = one operation).

3 DIGRESSION: PIPELINING

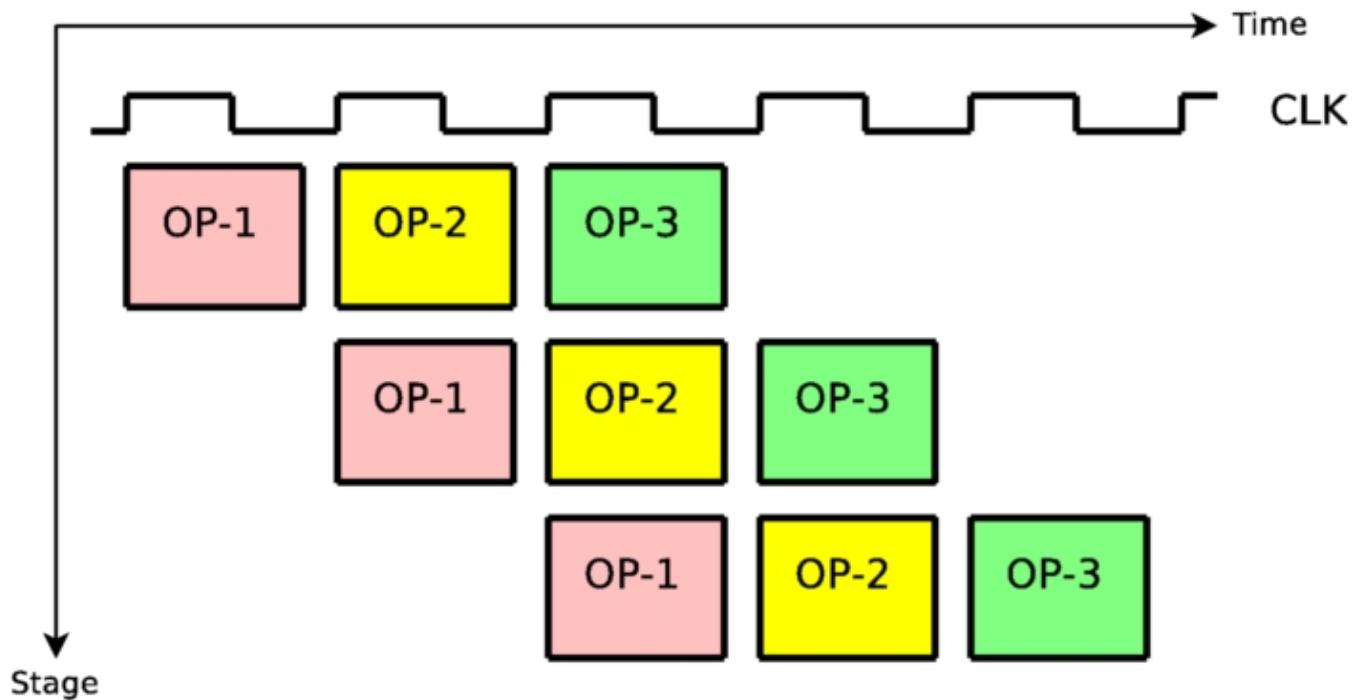

This kind of diagram shows how an operation is distributed over the different stages over time.

To summarize, pipelining typically results in:

- a slightly more complex design,

3 DIGRESSION: PIPELINING

- a moderately longer total delay, and
- a considerable improvement in throughput.

4 THE CPU CORE

In this lesson we will discuss the core of the CPU. These days, the same kind of CPU can come in different flavors that differ in the clock frequency that they support, bus sizes, the size of internal caches and memories and the capabilities of the I/O ports they provide. We call the common part of these different CPUs the **CPU core**. The CPU core is primarily characterized by the instruction set that it provides. One could also say that the CPU core is the implementation of a given instruction set.

The details of the instruction set will only be visible at the next lower level of the design. At the current level different CPUs (with different instruction sets) will still look the same because they all use the same structure. Only some control signals will be different for different CPUs.

We will use the so-called **Harvard architecture** because it fits better to FPGAs with internal memory modules. Harvard architecture means that the program memory and the data memory of the CPU are different. This gives us more flexibility and some instructions (for example **CALL**, which involves storing the current program counter in memory while changing the program counter and fetching the next instruction) can be executed in parallel).

Different CPU cores differ in the instruction set that they support. The types of CPU instructions (like arithmetic instructions, move instructions, branch instructions, etc.) are essentially the same for all CPUs. The differences are in the details like the encoding of the instructions, operand sizes, number of registers addressable, and the like).

Since all CPUs are rather similar apart from details, within the same base architecture (Harvard vs. von Neumann), the same structure can be used even for different instruction sets. This is because the same cycle is repeated again and again for the different instructions of a program. This cycle consists of 3 phases:

- Opcode fetch
- Opcode decoding
- Execution

Opcode fetch means that for a given value of the program counter **PC**, the instruction (opcode) stored at location PC is read from the program memory and that the PC is advanced to the next instruction.


Opcode decoding computes a number of control signals that will be needed in the execution phase.

Execution then executes the opcode which means that a small number of registers or memory locations is read and/or written.

In theory these 3 phases could be implemented in a combinational way (a static program memory, an opcode decoder at the output of the program memory and an execution module at the output of the opcode decoder). We will see later, however, that each phase has a considerable complexity and we therefore use a 3 stage pipeline instead.


In the following figure we see how a sequence of three opcodes ADD, MOV, and JMP is executed in the pipeline.

4 THE CPU CORE

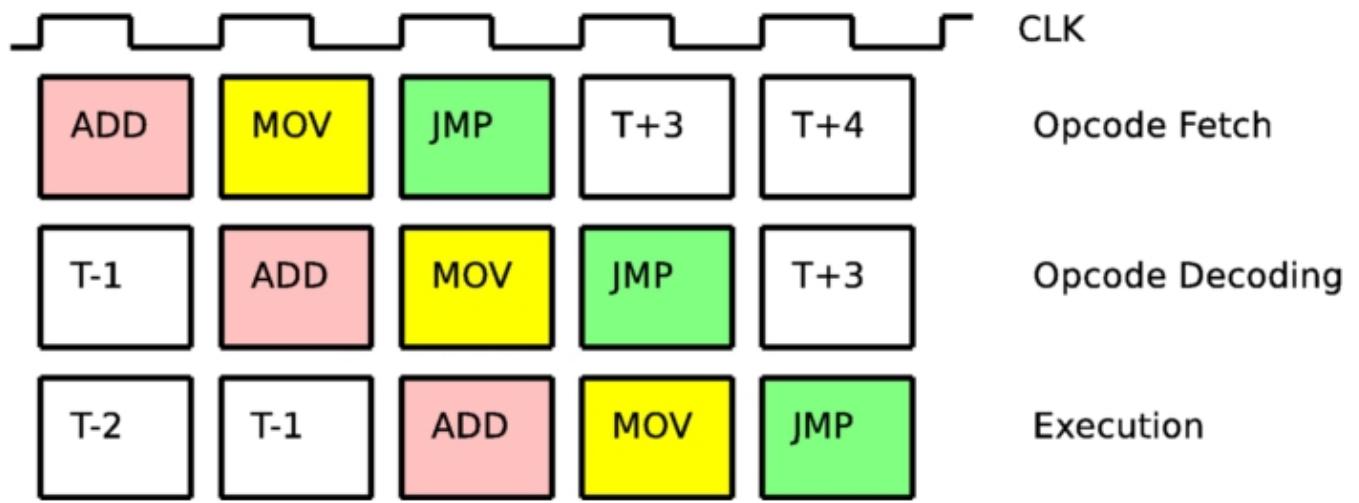

From the discussion above we can already predict the big picture of the CPU core. It consists of a pipeline with 3 stages opcode fetch, opcode decoder, and execution (which is called data path in the design because the operations required by the execution more or less imply the structure of the data paths in the execution stage:

4 THE CPU CORE

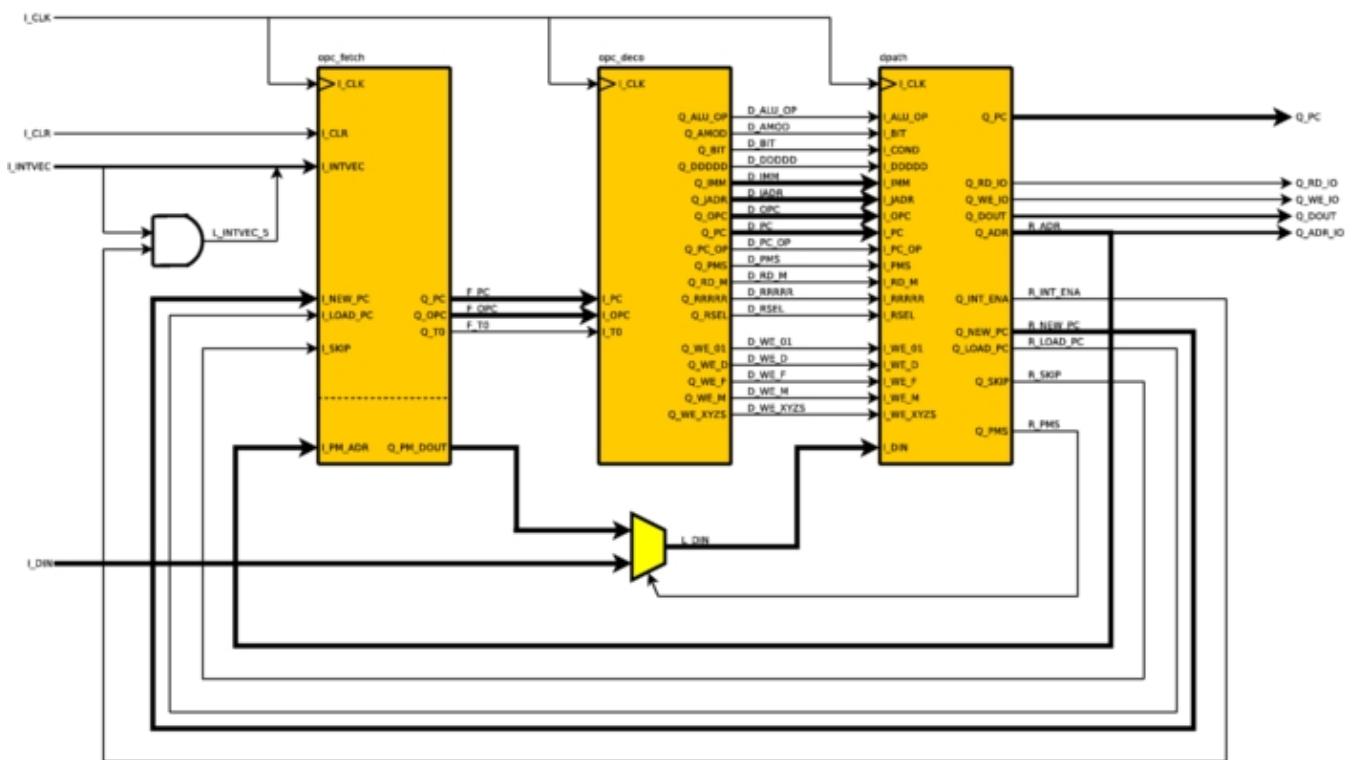

4 THE CPU CORE

The pipeline consists of the **opc_fetch** stage that drives **PC**, **OPC**, and **T0** signals to the opcode decoder stage. The **opc_deco** stage decodes the **OPC** signal and generates a number of control signals towards the execution stage. The execution stage then executes the decoded instruction.

The control signals towards the execution stage can be divided into 3 groups:

1. Select signals (**ALU_OP**, **AMOD**, **BIT**, **DDDDD**, **IMM**, **OPC**, **PMS**, **RD_M**, **RRRRR**, and **RSEL**). These signals control details (like register numbers) of the instruction being executed.
2. Branch and timing signals (**PC**, **PC_OP**, **WAIT**, (and **SKIP** in the reverse direction)). These signals control changes in the normal execution flow.
3. Write enable signals (**WE_01**, **WE_D**, **WE_F**, **WE_M**, and **WE_XYZS**). These signals define if and when registers and memory locations are updated.

We come to the VHDL code for the CPU core. The entity declaration must match the instantiation in the top-level design. Therefore:

```
33      entity cpu_core is
34          port (  I_CLK      : in  std_logic;
35                  I_CLR      : in  std_logic;
36                  I_INTVEC   : in  std_logic_vector( 5 downto 0);
37                  I_DIN      : in  std_logic_vector( 7 downto 0);
38
39                  Q_OPC      : out std_logic_vector(15 downto 0);
40                  Q_PC       : out std_logic_vector(15 downto 0);
41                  Q_DOUT     : out std_logic_vector( 7 downto 0);
42                  Q_ADR_IO   : out std_logic_vector( 7 downto 0);
43                  Q_RD_IO    : out std_logic;
44                  Q_WE_IO    : out std_logic);
```

src/cpu_core.vhd

The declaration and instantiation of **opc_fetch**, **opc_deco**, and **dpath** simply reflects what is shown in the previous figure.

The multiplexer driving **DIN** selects between data from the I/O input and data from the program memory. This is controlled by signal **PMS** (**program memory select**):

```
240      L_DIN      <= F_PM_DOUT when (D_PMS = '1') else I_DIN(7 downto 0);
```

src/cpu_core.vhd

4 THE CPU CORE

The interrupt vector input **INTVEC** is **and**'ed with the global interrupt enable bit in the status register (which is contained in the data path):

```
241      L_INTVEC_5      <= I_INTVEC(5) and R_INT_ENA;
```

src/cpu_core.vhd

This concludes the discussion of the CPU core and we will proceed with the different stages of the pipeline. Rather than following the natural order (opcode fetch, opcode decoder, execution), however, we will describe the opcode decoder last. The reason is that the opcode decoder is a consequence of the design of the execution stage. Once the execution stage is understood, the opcode decoder will become obvious (though still complex).

5 OPCODE FETCH

In this lesson we will design the opcode fetch stage of the CPU core. The opcode fetch stage is the simplest stage in the pipeline. It is the stage that put life into the CPU core by generating a sequence of opcodes that are then decoded and executed. The opcode fetch stage is sometimes called the **sequencer** of the CPU.

Since we use the Harvard architecture with separate program and data memories, we can simply instantiate the program memory in the opcode fetch stage. If you need more memory than your FPGA provides internally, then you can design address and data buses towards an external memory instead (or in addition). Most current FPGAs provide a lot of internal memory, so we can keep things simple.

The opcode fetch stage contains a sub-component **pmem**, which is the program memory. The main purpose of the opcode fetch stage is to manipulate the program counter (**PC**) and to produce opcodes. The **PC** is a local signal:

```
69      signal L_PC          : std_logic_vector(15 downto 0);  
  
src/opc_fetch.vhd
```

The **PC** is updated on every clock with its next value. The **T0** output is cleared when the **WAIT** signal is raised. This causes the **T0** output to be '1' on the first cycle of a 2 cycle instruction and '0' on the second cycle:

```
86      lpc: process(I_CLK)  
87      begin  
88          if (rising_edge(I_CLK)) then  
89              L_PC      <= L_NEXT_PC;  
90              L_T0      <= not L_WAIT;  
91          end if;  
92      end process;
```

```
src/opc_fetch.vhd
```

The next value of the **PC** depends on the **CLR**, **WAIT**, **LOAD_PC**, and **LONG_OP** signals:

```
94      L_NEXT_PC      <= X"0000"      when (I_CLR      = '1')  
95      else L_PC      when (L_WAIT     = '1')  
96      else I_NEW_PC    when (I_LOAD_PC = '1')  
97      else L_PC + X"0002" when (L_LONG_OP = '1')  
98      else L_PC + X"0001";
```

5 OPCODE FETCH

src/opc_fetch.vhd

The **CLR** signal, which overrides all others, resets the **PC** to 0. It is generated at power on and when the reset input of the CPU is asserted. The **WAIT** signal freezes the **PC** at its current value. It is used when an instruction needs two **CLK** cycles to complete. The **LOAD_PC** signal causes the **PC** to be loaded with the value on the **NEW_PC** input. The **LOAD_PC** signal is driven by the execution stage when a jump instruction is executed. If neither **CLR**, **WAIT**, or **LOAD_PC** is present then the **PC** is advanced to the next instruction. If the current instruction is one of **JMP**, **CALL**, **LDS** and **STS**, then it has a length of two 16-bit words and **LONG_OP** is set. This causes the PC to be incremented by 2 rather than by the normal instruction length of 1:

```
100      -- Two word opcodes:
101      --
102      --         9      3210
103      -- 1001 000d dddd 0000 kkkk kkkk kkkk kkkk - LDS
104      -- 1001 001d dddd 0000 kkkk kkkk kkkk kkkk - SDS
105      -- 1001 010k kkkk 110k kkkk kkkk kkkk kkkk - JMP
106      -- 1001 010k kkkk 111k kkkk kkkk kkkk kkkk - CALL
107      --
108      L_LONG_OP    <= '1' when (((P_OPC(15 downto 9) = "1001010") and
109                                (P_OPC( 3 downto 2) = "11"))           -- JMP, CALL
110                                or ((P_OPC(15 downto 10) = "100100") and
111                                (P_OPC( 3 downto 0) = "0000")))       -- LDS, STS
112      else '0';
```

src/opc_fetch.vhd

The **CLR**, **SKIP**, and **I_INTVEC** inputs are used to force a **NOP** (no operation) opcode or an "interrupt opcode" onto the output of the opcode fetch stage. An interrupt opcode is an opcode that does not belong to the normal instruction set of the CPU (and is therefore not generated by assemblers or compilers), but is used internally to trigger interrupt processing (pushing of the PC, clearing the interrupt enable flag, and jumping to specific locations) further down in the pipeline.

```
133      L_INVALIDATE    <= I_CLR or I_SKIP;
134
135      Q_OPC      <= X"00000000" when (L_INVALIDATE = '1')
136      else P_OPC      when (I_INTVEC(5) = '0')
137      else (X"000000" & "00" & I_INTVEC);      -- "interrupt opcode"
```

src/opc_fetch.vhd

CLR is derived from the reset input and also resets the program counter. **SKIP** comes from the execution stage and is used to invalidate parts of the pipeline, for example when a decision was made to take a

5 OPCODE FETCH

conditional branch. This will be explained in more detail in the lesson about branching.

5.1 Program Memory

The program memory is declared as follows:

```
36      entity prog_mem is
37          port (  I_CLK        : in  std_logic;
38
39              I_WAIT       : in  std_logic;
40              I_PC         : in  std_logic_vector(15 downto 0); -- word address
41              I_PM_ADR    : in  std_logic_vector(11 downto 0); -- byte address
42
43              Q_OPC        : out std_logic_vector(31 downto 0);
44              Q_PC         : out std_logic_vector(15 downto 0);
45              Q_PM_DOUT   : out std_logic_vector( 7 downto 0));
46
47      end prog_mem;
```

src/prog_mem.vhd

5.2.1 Dual Port Memory

The program memory is a dual port memory. This means that two different memory locations can be read or written at the same time. We don't write to the program memory, because we would like to read two addresses at the same time. The reason are the **LPM** (load program memory) instructions. These instructions read from the program memory while the program memory is fetching the next instructions. In a way these instructions violate the Harvard architecture, but on the other hand they are extremely useful for string constants in C. Rather than initializing the (typically smaller) data memory with these constants, one can leave them in program memory and access them using **LPM** instructions,

Without a dual port memory, we would have needed to stop the pipeline during the execution of **LPM** instructions. Use of dual port memory avoids this additional complexity.

The second port used for **LPM** instructions consists of the address input **PM_ADR** and the data output **PM_DOUT**. **PM_ADR** is a 12-bit byte address (and consequently **PM_DOUT** is an 8-bit output). In contrast, the other port uses an 11-bit word address.

The other signals of the program memory belong to the first port which is used for opcode fetches.

5.2.2 Look-ahead for two word instructions

The vast majority of AVR instructions are single-word (16-bit) instructions. There are 4 exceptions, which are **CALL**, **JMP**, **LDS**, and **STS**. These instructions have addresses (the target address for **CALL** and **JMP** and data memory address for **\$LDS#** and **STS**) in the word following the opcode.

There are two ways to handle such opcodes. One way is to look back in the pipeline when the second word is needed. When one of these instructions reaches the execution stage, then the next word is clocked into the


5 OPCODE FETCH

decoding stage (so we could fetch it from there). It might lead to complications, however, when it comes to invalidating the pipeline, insertion of interrupts and the like.

The other way, and the one we choose, is to divide the program memory into an even memory and an odd memory. The internal memory modules in an FPGA are anyhow small and therefore using two memories is almost as simple as using one (both would consist of a number of smaller modules).

There are two cases to consider: (1) an even **PC** (shown on the left of the following figure) and (2) an odd **PC** shown on the right. In both cases do we want the (combined) memory at address **PC** to be stored in the lower word of the **OPC** output and the next word (at **PC+1**) in the upper word of **OPC**.

5 OPCODE FETCH

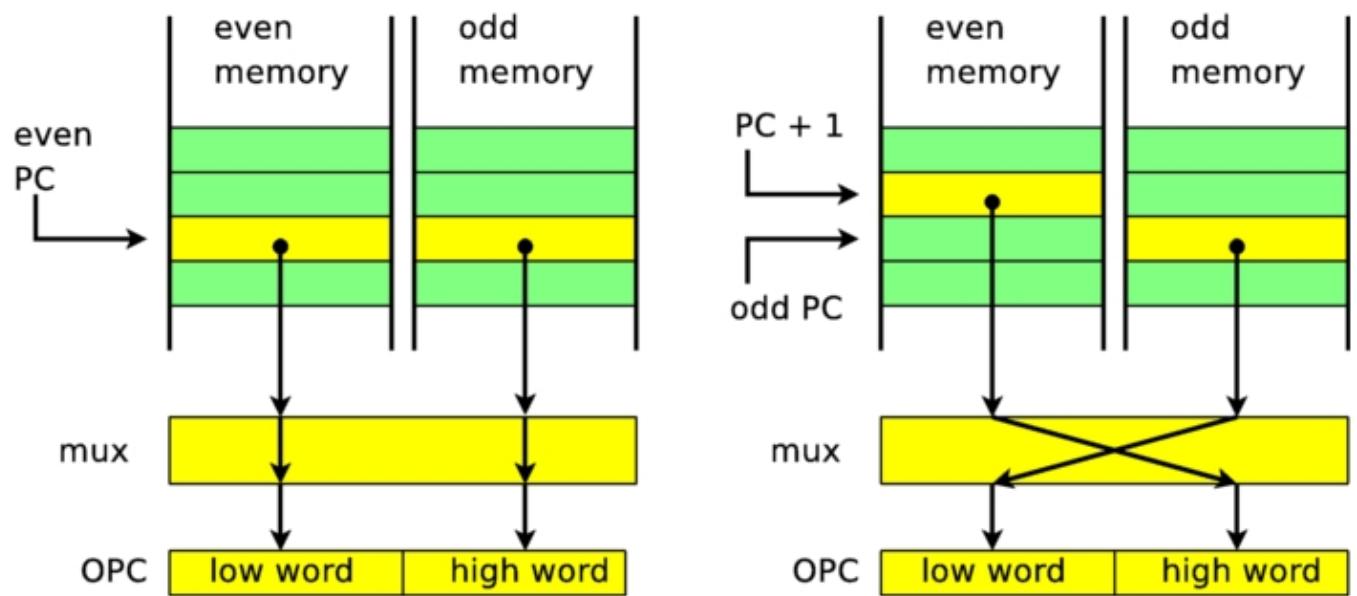

5 OPCODE FETCH

We observe the following:

- the odd memory address is **PC[10:1]** in both cases.
- the even memory address is **PC[10:1] + PC[0]** in both cases.
- the data outputs of the two memories are either straight or crossed, depending (only) on **PC[0]**.

In VHDL, we express this like:

```
252      L_PC_O      <= I_PC(10 downto 1);
253      L_PC_E      <= I_PC(10 downto 1) + ("0000000000" & I_PC(0));
254      Q_OPC(15 downto 0)    <= M_OPC_E when L_PC_O = '0' else M_OPC_O;
255      Q_OPC(31 downto 16)   <= M_OPC_E when L_PC_O = '1' else M_OPC_O;

src/prog_mem.vhd
```

The output multiplexer uses the **PC** and **PM_ADR** of the previous cycle, so we need to remember the lower bit(s) in signals **PC_0** and **PM_ADR_1_0**:

```
224      pc0: process(I_CLK)
225      begin
226          if (rising_edge(I_CLK)) then
227              Q_PC      <= I_PC;
228              L_PM_ADR_1_0    <= I_PM_ADR(1 downto 0);
229              if ((I_WAIT = '0')) then
230                  L_PC_0      <= I_PC(0);
231              end if;
232          end if;
233      end process;
```

```
src/prog_mem.vhd
```

The split into two memories makes the entire program memory 32-bit wide. Note that the PC is a word address, while PM_ADR is a byte address.

5.2.3 Memory block instantiation and initialization.

The entire program memory consists of 8 memory modules, four for the even half (components **pe_0**, **pe_1**, **pe_2**, and **pe_3**) and four for the odd part (**po_0**, **po_1**, **po_2**, and **po_3**).

We explain the first module in detail:

5 OPCODE FETCH

```
102      pe_0 : RAMB4_S4_S4 -----
103      generic map(INIT_00 => pe_0_00, INIT_01 => pe_0_01, INIT_02 => pe_0_02,
104          INIT_03 => pe_0_03, INIT_04 => pe_0_04, INIT_05 => pe_0_05,
105          INIT_06 => pe_0_06, INIT_07 => pe_0_07, INIT_08 => pe_0_08,
106          INIT_09 => pe_0_09, INIT_0A => pe_0_0A, INIT_0B => pe_0_0B,
107          INIT_0C => pe_0_0C, INIT_0D => pe_0_0D, INIT_0E => pe_0_0E,
108          INIT_0F => pe_0_0F)
109      port map(ADDRA => I_PC_E,                               ADDR_B => I_PM_ADR(11 downto 2),
110          CLKA => I_CLK,                                     CLKB => I_CLK,
111          DIA  => "0000",                                    DIB  => "0000",
112          ENA  => I_WAIT_N,                                 ENB  => '1',
113          RSTA => '0',                                     RSTB => '0',
114          WEA  => '0',                                     WEB  => '0',
115          DOA  => M_OPC_E(3 downto 0),                   DOB  => M_PMD_E(3 downto 0));
```

src/prog_mem.vhd

The first line instantiates a module of type **RAMB4_S4_S4**, which is a dual-port memory module with two 4-bit ports. For a Xilinx FPGA you can used these modules directly by uncommenting the use of the UNISIM library. For functional simulation we have provided a **RAMB4_S4_S4.vhd** component in the test directory. This component emulates the real **RAMB4_S4_S4** as good as needed.

The next lines define the content of each memory module by means of a generic map. The elements of the generic map (like **pe_0_00**, **pe_0_01**, and so forth) define the initial memory content of the instantiated module. **pe_0_00**, **pe_0_01**, .. are themselves defined in **prog_mem_content.vhd** which is included in the library section:

```
34      use work.prog_mem_content.all;
```

src/prog_mem.vhd

The process from a C (or C++) source file **hello.c** to the final FPGA is then:

- write, compile, and link **hello.c** (produces **hello.hex**).
- generate **prog_mem_content.vhd** from **hello.hex** (by means of tool **make_mem**, which is provided with this lecture).
- simulate, synthesize and implement the design.
- create a bitmap file.
- flash the FPGA (or serial PROM).

There are other ways of initializing the memory modules, such as updating sections of the bitmap file, but we found the above sequence easier to use.


After the generic map, follows the port map of the memory module. The two addresses **ADDRA** and **ADDRB** of the two ports come from the **PC** and **PM_ADR** inputs as already described.

5 OPCODE FETCH

Both ports are clocked from **CLK**. Since the program memory is read-only, the **DIA** and **DIB** inputs are not used (set to 0000) and **WEA** and **WEB** are 0. **RSTA** and **RSTB** are not used either and are set to 0. **ENA** is used for keeping the **OPC** when the pipeline is stopped, while **ENB** is not used. The memory outputs **DOA** and **DOB** go to the output multiplexers of the two ports.

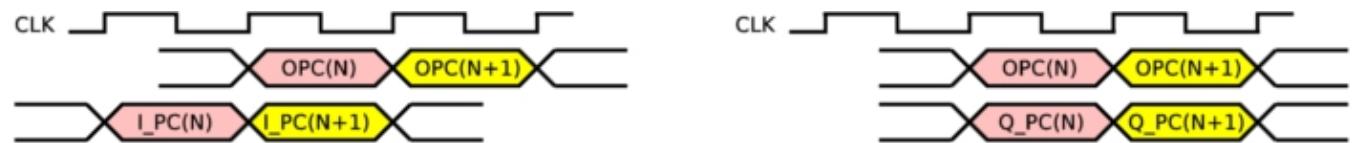5.2.3 Delayed PC

Q_{PC} is **I_{PC}** delayed by one clock. The program memory is a synchronous memory, which has the consequence that the program memory output **OPC** for a given **I_{PC}** is always one clock cycle behind as shown in the figure below on the left.



By clocking **I_{PC}** once, we re-align **Q_{PC}** and **OPC** as shown on the right:

```
227          QPC      <=  IPC;  
src/prog_mem.vhd
```

5.3 Two Cycle Opcodes

The vast majority of instructions executes in one cycle. Some need two cycles because they involve reading of a synchronous memory. For these signals **WAIT** signal is generated on the first cycle:

5 OPCODE FETCH

```

114      -- Two cycle opcodes:
115      --
116      -- 1001 000d dddd .... - LDS etc.
117      -- 1001 0101 0000 1000 - RET
118      -- 1001 0101 0001 1000 - RETI
119      -- 1001 1001 AAAA Abbb - SBIC
120      -- 1001 1011 AAAA Abbb - SBIS
121      -- 1111 110r rrrr 0bbb - SBRC
122      -- 1111 111r rrrr 0bbb - SBRS
123      --
124      L_WAIT      <= '0'  when (L_INVALIDATE = '1')
125      else '0'  when (I_INTVEC(5)  = '1')
126      else L_TO when ((P_OPC(15 downto 9) = "1001000" )      -- LDS etc.
127                  or (P_OPC(15 downto 8) = "10010101")      -- RET etc.
128                  or ((P_OPC(15 downto 10) = "100110")        -- SBIC, SBIS
129                  and P_OPC(8) = '1')
130                  or (P_OPC(15 downto 10) = "111111"))      -- SBRC, SBRS
131      else  '0';

```

src/opc_fetch.vhd

5.4 Interrupts

The opcode fetch stage is also responsible for part of the interrupt handling. Interrupts are generated in the I/O block by setting **INTVEC** to a value with the highest bit set:

```

169          L_INTVEC      <= "101011";           -- _VECTOR(11)
170      end if;
171      elsif (L_TX_INT_ENABLED and not U_TX_BUSY) = '1' then
172          if (L_INTVEC(5) = '0') then      -- no interrupt pending
173              L_INTVEC      <= "101100";           -- _VECTOR(12)
174          end if;
175      else                                -- no interrupt
176          L_INTVEC      <= "000000";

```

src/io.vhd

The highest bit of **INTVEC** indicates that the lower bits contain a valid interrupt number. **INTVEC** proceeds to the cpu core where the upper bit is **and**'ed with the global interrupt enable bit (in the status register):

```

241          L_INTVEC_5      <= I_INTVEC(5) and R_INT_ENA;

```

src/cpu_core.vhd

5 OPCODE FETCH

The (possibly modified) **INTVEC** then proceeds to the opcode fetch stage. If the the global interrupt enable bit was set, then the next valid opcode is replaced by an "interrupt opcode":

```
135      Q_OPC      <= X"00000000" when (L_INVALIDATE = '1')
136      else P_OPC      when (I_INTVEC(5) = '0')
137      else (X"000000" & "00" & I_INTVEC);      -- "interrupt opcode"
src/opc_fetch.vhd
```


The interrupt opcode uses a gap after the **NOP** instruction in the opcode set of the AVR CPU. When the interrupt opcode reaches the execution stage then is causes a branch to the location determined by the lower bits of **INTVEC**, pushes the program counter, and clears the interrupt enable bit. This happens a few clock cycles later. In the meantime the opcode fetch stage keeps inserting interrupt instructions into the pipeline. These additional interrupt instructions are being invalidated by the execution stage when the first interrupt instruction reaches the execution stage.

6 DATA PATH

In this lesson we will describe the data path of the CPU. We discuss the basic elements of the data path, but without reference to particular instructions. The implementation of instructions will be discussed in the next lesson. In this lesson we are more interested in the capabilities of the data path.

The data path consists of 3 major components: a register file, an ALU (arithmetic/logic unit), and the data memory:

6 DATA PATH

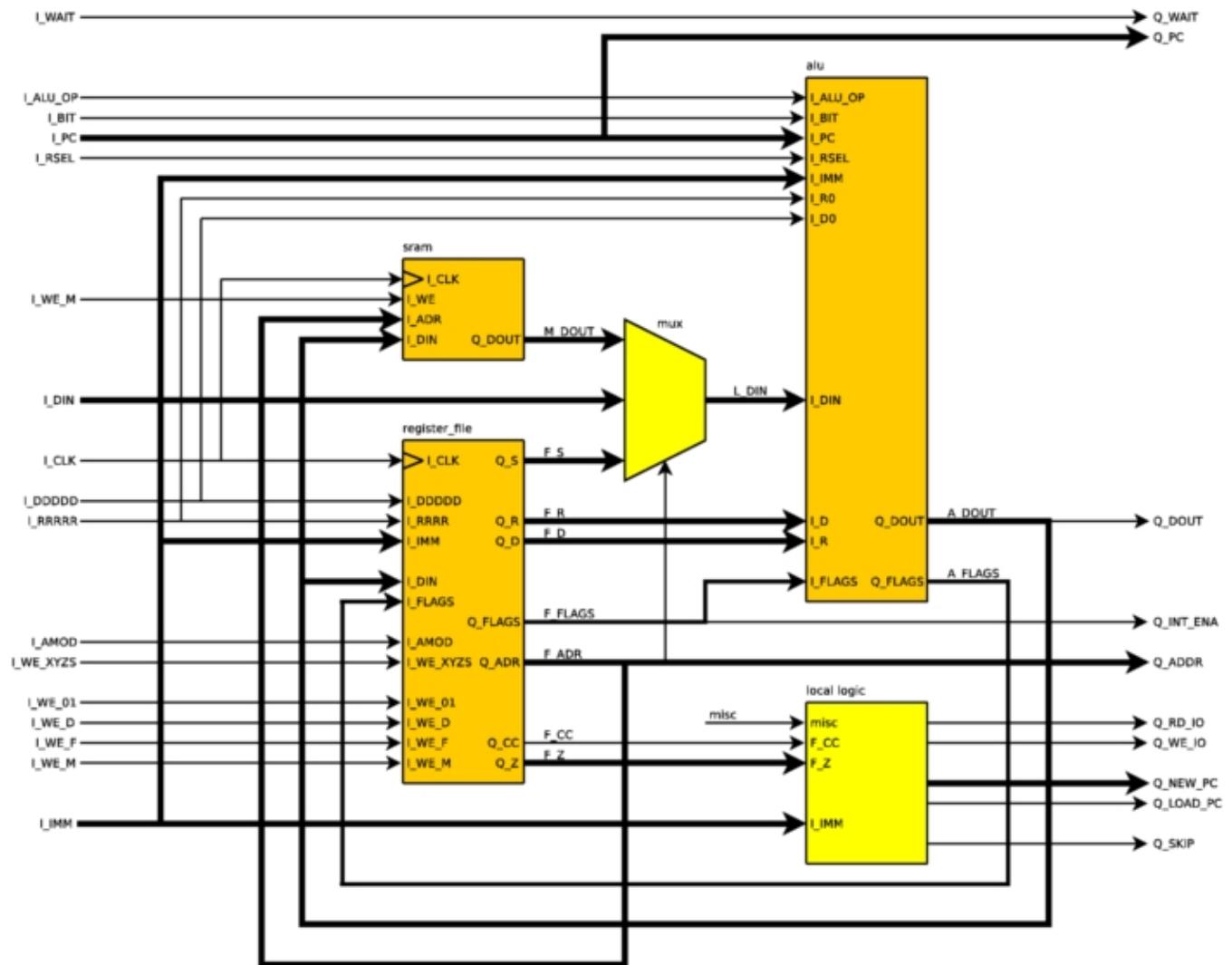

6.1 Register File

The AVR CPU has 32 general purpose 8-bit registers. Most opcodes use individual 8-bit registers, but some that use a pair of registers. The first register of a register pair is always an even register, while the other register of a pair is the next higher odd register. Instead of using 32 8-bit registers, we use 16 16-bit register pairs. Each register pair consists of two 8-bit registers.

6.1.1 Register Pair

A single register pair is defined as:

```

32      entity reg_16 is
33          port (  I_CLK      : in  std_logic;
34
35              I_D       : in  std_logic_vector (15 downto 0);
36              I_WE     : in  std_logic_vector ( 1 downto 0);
37
38              Q        : out std_logic_vector (15 downto 0));
39      end reg_16;
```

src/reg_16.vhd

The **Q** output provides the current value of the register pair. There is no need for a read strobe, because (unlike I/O devices) reading the current value of a register pair has no side effects.

The register pair can be written by setting one or both bits of the **WE** input. If both bits are set then the all 16 bits of **D** are written; the low byte to the even register and the higher byte to the odd register of the pair. If only one bit is set then the register corresponding then the bit set in **WE** defines the register to be written (even bit = even register, odd bit = odd register) and the value to be written is in the lower byte of **DIN**:

```

46      process(I_CLK)
47      begin
48          if (rising_edge(I_CLK)) then
49              if (I_WE(1) = '1') then
50                  L(15 downto 8)      <= I_D(15 downto 8);
51              end if;
52              if (I_WE(0) = '1') then
53                  L( 7 downto 0)      <= I_D( 7 downto 0);
54              end if;
55          end if;
56      end process;
```

src/reg_16.vhd

6.1.2 The Status Register

The status register is an 8-bit register. This register can be updated by writing to address 0x5F. Primarily it is updated, however, as a side effect of the execution of ALU operations. If, for example, an arithmetic/logic instruction produces a result of 0, then the zero flag (the second bit in the status register) is set. An arithmetic overflow in an ADD instruction causes the carry bit to be set, and so on. The status register is declared as:

```

32      entity status_reg is
33          port (
34              I_CLK           : in  std_logic;
35              I_COND          : in  std_logic_vector ( 3 downto 0);
36              I_DIN           : in  std_logic_vector ( 7 downto 0);
37              I_FLAGS          : in  std_logic_vector ( 7 downto 0);
38              I_WE_F           : in  std_logic;
39              I_WE_SR          : in  std_logic;
40
41              Q               : out std_logic_vector ( 7 downto 0);
42              Q_CC            : out std_logic);
43      end status_reg;
```

src/status_reg.vhd

If **WE_FLAGS** is '1' then the status register is updated as a result of an ALU operation; the new value of the status register is provided on the **FLAGS** input which comes from the ALU.

If **WE_SR** is '1' then the status register is updated as a result of an I/O write operation (like **OUT** or **STS**); the new value of the status register is provided on the **DIN** input.

The output **Q** of the status register holds the current value of the register. In addition there is a **CC** output that is '1' when the condition indicated by the **COND** input is fulfilled. This is used for conditional branch instructions. **COND** comes directly from the opcode for a branch instruction (bit 10 of the opcode for the "polarity" and bits 2-0 of the opcode for the bit of the status register that is being tested).

6.1.3 Register File Components

The register file consists of 16 general purpose register pairs **r00** to **r30**, a stack pointer **sp**, and an 8-bit status register **sr**:

```

131      r00: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 1 downto 0), I_D => I_DIN, Q => R
132      r02: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 3 downto 2), I_D => I_DIN, Q => R
133      r04: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 5 downto 4), I_D => I_DIN, Q => R
134      r06: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 7 downto 6), I_D => I_DIN, Q => R
135      r08: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 9 downto 8), I_D => I_DIN, Q => R
136      r10: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(11 downto 10), I_D => I_DIN, Q => R
```

6 DATA PATH

```

137      r12: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(13 downto 12), I_D => I_DIN, Q => R
138      r14: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(15 downto 14), I_D => I_DIN, Q => R
139      r16: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(17 downto 16), I_D => I_DIN, Q => R
140      r18: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(19 downto 18), I_D => I_DIN, Q => R
141      r20: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(21 downto 20), I_D => I_DIN, Q => R
142      r22: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(23 downto 22), I_D => I_DIN, Q => R
143      r24: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(25 downto 24), I_D => I_DIN, Q => R
144      r26: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(27 downto 26), I_D => L_DX, Q => R
145      r28: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(29 downto 28), I_D => L_DY, Q => R
146      r30: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(31 downto 30), I_D => L_DZ, Q => R

```

src/register_file.vhd

```
147      sp: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE_SP,
```

```
I_D => L_DSP, Q => R
```

src/register_file.vhd

```

149      sr: status_reg
150      port map(  I_CLK      => I_CLK,
151                  I_COND     => I_COND,
152                  I_DIN      => I_DIN(7 downto 0),
153                  I_FLAGS    => I_FLAGS,
154                  I_WE_F    => I_WE_F,
155                  I_WE_SR   => L_WE_SR,
156                  Q          => S_FLAGS,
157                  Q_CC       => Q_CC);

```

src/register_file.vhd

Each register pair drives a 16-bit signal according to the (even) number of the register pair in the register file:

```

71      signal R_R00           : std_logic_vector(15 downto 0);
72      signal R_R02           : std_logic_vector(15 downto 0);
73      signal R_R04           : std_logic_vector(15 downto 0);
74      signal R_R06           : std_logic_vector(15 downto 0);
75      signal R_R08           : std_logic_vector(15 downto 0);
76      signal R_R10           : std_logic_vector(15 downto 0);
77      signal R_R12           : std_logic_vector(15 downto 0);
78      signal R_R14           : std_logic_vector(15 downto 0);
79      signal R_R16           : std_logic_vector(15 downto 0);
80      signal R_R18           : std_logic_vector(15 downto 0);
81      signal R_R20           : std_logic_vector(15 downto 0);
82      signal R_R22           : std_logic_vector(15 downto 0);
83      signal R_R24           : std_logic_vector(15 downto 0);
84      signal R_R26           : std_logic_vector(15 downto 0);
85      signal R_R28           : std_logic_vector(15 downto 0);
86      signal R_R30           : std_logic_vector(15 downto 0);      -- stack pointer
87      signal R_SP            : std_logic_vector(15 downto 0);

```

src/register_file.vhd

6.1.4 Addressing of General Purpose Registers

We address individual general purpose registers by a 5-bit value. Normally an opcode using an individual general purpose 8-bit register has a 5 bit field which is the address of the register. The opcode decoder transfers this field to its **DDDDD** or **RRRRR** output. For some opcodes not all 32 registers can be used, but only 16 (e.g. **ANDI**) or 8 (e.g. **MUL**). In these cases the register field in the opcode is smaller and the opcode decoder fills in the missing bits. Some opcodes imply particular registers (e.g. some **LPM** variant), and again the opcode decoder fills in the implied register number.

An opcode may address no, one, two, or three registers or pairs. If one register is addressed, then the number of that register is encoded in the **DDDDD** signal.

If two (or more) registers are used, then one (normally the destination register) is encoded in the **DDDDD** signal and the other (source) is encoded in the **RRRRR** signal. Opcodes with 3 registers (e.g. **MUL**) use an implied destination register pair (register pair 0) and two source registers encoded in the **DDDDD** and **RRRRR** signals.

6.1.5 Addressing of General Purpose Register Pairs

We address register pairs by addressing the even register of the pair. The address of a register pair is therefore a 5-bit value with the lowest bit cleared. The opcode normally only has a 4-bit field for a register pair and the lowest (cleared) bit is filled in by the opcode decoder. Like for individual registers it can happen that not all 16 register pairs can be addressed (e.g. **ADIW**). This is handled in the same way as for individual registers.

In the AVR context, the register pairs **R26**, **R28**, and **R30** are also called (pointer registers) **X**, **Y**, and **Z** respectively.

6.1.6 Requirements on the Register File

If we go through the opcodes of the AVR CPU, then we see the capabilities that the register file must provide for general purpose registers (or register pairs):

Capability	Opcode (example)
Read one register, read/write another register	ADD Rd, Rr
Write one register, read/write another register	LD Rd, (X+)
Write one register, read another register	LD Rd, (X)
Read/write one register	ASR Rd
Read one register, read another register	CMP Rd, Rr
Read one register, read another register	LD Rd, Rr
Read one register	IN Rd, A
Write one register	OUT A, Rr

6.1.7 Reading Registers or Register Pairs

There are 4 cases:

- Read register or register pair addresses by **DDDDD**.
- Read register or register pair addresses by **RRRRR**.
- Read register addressed by the current I/O address.
- Read **X**, **Y**, or **Z** pointer implied by the addressing mode **AMOD**.

6 DATA PATH

- Read the **Z** pointer implied by the instruction (**IJMP** or **ICALL**).

Some of these cases can happen simultaneously. For example the **ICALL** instruction reads the **Z** register (the target address of the call) while it pushed the current PC onto the stack. Likewise, **ST** may need the **X**, **Y**, or **Z** for address calculations and a general purpose register that is to be stored in memory. For this reason we provide 5 different outputs in the register file. These outputs are addressing the general purpose registers differently (and they can be used in parallel):

- **Q_D** is the content of the register addressed by **DDDDD**.
- **Q_R** is the content of the register pair addressed by **RRRR**.
- **Q_S** is the content of the register addressed by **ADR**.
- **Q_ADR** is an address defined by **AMOD** (and may use **X**, **Y**, or **Z**).
- **Q_X** is the content of the **Z** register.

Q_D is one of the register pair signals as defined by **DDDDD**. We read the entire pair; the selection of the even/odd register within the pair is done later in the ALU based on **DDDDD(0)**:

```

189      process (R_R00, R_R02, R_R04, R_R06, R_R08, R_R10, R_R12, R_R14,
190          R_R16, R_R18, R_R20, R_R22, R_R24, R_R26, R_R28, R_R30,
191          I_DDDDD(4 downto 1))
192      begin
193          case I_DDDDD(4 downto 1) is
194              when "0000" => Q_D      <= R_R00;
195              when "0001" => Q_D      <= R_R02;
196              when "0010" => Q_D      <= R_R04;
197              when "0011" => Q_D      <= R_R06;
198              when "0100" => Q_D      <= R_R08;
199              when "0101" => Q_D      <= R_R10;
200              when "0110" => Q_D      <= R_R12;
201              when "0111" => Q_D      <= R_R14;
202              when "1000" => Q_D      <= R_R16;
203              when "1001" => Q_D      <= R_R18;
204              when "1010" => Q_D      <= R_R20;
205              when "1011" => Q_D      <= R_R22;
206              when "1100" => Q_D      <= R_R24;
207              when "1101" => Q_D      <= R_R26;
208              when "1110" => Q_D      <= R_R28;
209              when others => Q_D      <= R_R30;
210          end case;
211      end process;
```

src/register_file.vhd

Q_R is one of the register pair signals as defined by **RRRR**:

```

215      process (R_R00, R_R02, R_R04, R_R06, R_R08, R_R10, R_R12, R_R14,
216          R_R16, R_R18, R_R20, R_R22, R_R24, R_R26, R_R28, R_R30, I_RRRR)
217      begin
```

6 DATA PATH

```

218      case I_RRRR is
219          when "0000" => Q_R      <= R_R00;
220          when "0001" => Q_R      <= R_R02;
221          when "0010" => Q_R      <= R_R04;
222          when "0011" => Q_R      <= R_R06;
223          when "0100" => Q_R      <= R_R08;
224          when "0101" => Q_R      <= R_R10;
225          when "0110" => Q_R      <= R_R12;
226          when "0111" => Q_R      <= R_R14;
227          when "1000" => Q_R      <= R_R16;
228          when "1001" => Q_R      <= R_R18;
229          when "1010" => Q_R      <= R_R20;
230          when "1011" => Q_R      <= R_R22;
231          when "1100" => Q_R      <= R_R24;
232          when "1101" => Q_R      <= R_R26;
233          when "1110" => Q_R      <= R_R28;
234          when others => Q_R      <= R_R30;
235      end case;
236  end process;

```

src/register_file.vhd

The general purpose registers, but also the stack pointer and the status register, are mapped into the data memory space:

Address	Purpose
0x00 - 0x1F	general purpose CPU registers.
0x20 - 0x5C	miscellaneous I/O registers.
0x5D	stack pointer low
0x5E	stack pointer high
0x5F	status register
0x60 - 0xFFFF	data memory

If an address corresponding to a register in the register file (i.e. a general purpose register, the stack pointer, or the status register is read, then the register shall be returned.

For example, LD Rd, R22 shall give the same result as LDS Rd, 22.

The 8-bit **Q_S** output contains the register addresses by **ADR**:

```

161      process(R_R00, R_R02, R_R04, R_R06, R_R08, R_R10, R_R12, R_R14,
162                  R_R16, R_R18, R_R20, R_R22, R_R24, R_R26, R_R28, R_R30,
163                  R_SP, S_FLAGS, L_ADR(6 downto 1))
164  begin
165      case L_ADR(6 downto 1) is
166          when "000000" => L_S      <= R_R00;
167          when "000001" => L_S      <= R_R02;
168          when "000010" => L_S      <= R_R04;
169          when "000011" => L_S      <= R_R06;
170          when "000100" => L_S      <= R_R08;
171          when "000101" => L_S      <= R_R10;
172          when "000110" => L_S      <= R_R12;
173          when "000111" => L_S      <= R_R14;

```

6 DATA PATH

```

174      when "001000" => L_S      <= R_R16;
175      when "001001" => L_S      <= R_R18;
176      when "001010" => L_S      <= R_R20;
177      when "001011" => L_S      <= R_R22;
178      when "001100" => L_S      <= R_R24;
179      when "001101" => L_S      <= R_R26;
180      when "001110" => L_S      <= R_R28;
181      when "001111" => L_S      <= R_R30;
182      when "101111" => L_S      <= R_SP ( 7 downto 0) & X"00";    -- SPL
183      when others     => L_S      <= S_FLAGS & R_SP (15 downto 8);   -- SR/SPH
184      end case;
185  end process;
186

```

src/register_file.vhd

6.1.8 Writing Registers or Register Pairs

In order to write a register, we need to select the proper input (data source) and the proper **WE** signal. For most registers, the only possible data source is **DIN** which comes straight from the ALU. The pointer register pairs **X**, **Y**, and **Z**, however, can also be changed as a side effect of the post-increment (**X+**, **Y+**, **Z+**) and pre-decrement (**-X**, **-Y**, **-Z**) addressing modes of the **LDS** and **STS** instructions. The addressing modes are discussed in more detail in the next chapter; here it suffices to note that the **X**, **Y**, and #**Z** #registers get their data from **DX**, **DY**, and **DZ**, respectively rather than from **DIN**.

There is a total of 4 cases where general purpose registers are written. Three of these cases that are applicable to all general purpose registers and one case collects special cases for particular registers (the register numbers are then implied).

We compute a 32 bit write enable signal for each of the four cases and **OR** them together.

The first case is a write to an 8-bit register addressed by **DDDDD**. For this case we create the signal **WE_D**:

```

288      L_WE_D( 0)      <= I_WE_D(0) when (I_DDDDD = "00000") else '0';
289      L_WE_D( 1)      <= I_WE_D(0) when (I_DDDDD = "00001") else '0';
290      L_WE_D( 2)      <= I_WE_D(0) when (I_DDDDD = "00010") else '0';
291      L_WE_D( 3)      <= I_WE_D(0) when (I_DDDDD = "00011") else '0';
292      L_WE_D( 4)      <= I_WE_D(0) when (I_DDDDD = "00100") else '0';
293      L_WE_D( 5)      <= I_WE_D(0) when (I_DDDDD = "00101") else '0';
294      L_WE_D( 6)      <= I_WE_D(0) when (I_DDDDD = "00110") else '0';
295      L_WE_D( 7)      <= I_WE_D(0) when (I_DDDDD = "00111") else '0';
296      L_WE_D( 8)      <= I_WE_D(0) when (I_DDDDD = "01000") else '0';
297      L_WE_D( 9)      <= I_WE_D(0) when (I_DDDDD = "01001") else '0';
298      L_WE_D(10)      <= I_WE_D(0) when (I_DDDDD = "01010") else '0';
299      L_WE_D(11)      <= I_WE_D(0) when (I_DDDDD = "01011") else '0';
300      L_WE_D(12)      <= I_WE_D(0) when (I_DDDDD = "01100") else '0';
301      L_WE_D(13)      <= I_WE_D(0) when (I_DDDDD = "01101") else '0';
302      L_WE_D(14)      <= I_WE_D(0) when (I_DDDDD = "01110") else '0';
303      L_WE_D(15)      <= I_WE_D(0) when (I_DDDDD = "01111") else '0';
304      L_WE_D(16)      <= I_WE_D(0) when (I_DDDDD = "10000") else '0';
305      L_WE_D(17)      <= I_WE_D(0) when (I_DDDDD = "10001") else '0';
306      L_WE_D(18)      <= I_WE_D(0) when (I_DDDDD = "10010") else '0';

```

6 DATA PATH

```

307      L_WE_D(19)      <= I_WE_D(0) when (I_DDDDD = "10011") else '0';
308      L_WE_D(20)      <= I_WE_D(0) when (I_DDDDD = "10100") else '0';
309      L_WE_D(21)      <= I_WE_D(0) when (I_DDDDD = "10101") else '0';
310      L_WE_D(22)      <= I_WE_D(0) when (I_DDDDD = "10110") else '0';
311      L_WE_D(23)      <= I_WE_D(0) when (I_DDDDD = "10111") else '0';
312      L_WE_D(24)      <= I_WE_D(0) when (I_DDDDD = "11000") else '0';
313      L_WE_D(25)      <= I_WE_D(0) when (I_DDDDD = "11001") else '0';
314      L_WE_D(26)      <= I_WE_D(0) when (I_DDDDD = "11010") else '0';
315      L_WE_D(27)      <= I_WE_D(0) when (I_DDDDD = "11011") else '0';
316      L_WE_D(28)      <= I_WE_D(0) when (I_DDDDD = "11100") else '0';
317      L_WE_D(29)      <= I_WE_D(0) when (I_DDDDD = "11101") else '0';
318      L_WE_D(30)      <= I_WE_D(0) when (I_DDDDD = "11110") else '0';
319      L_WE_D(31)      <= I_WE_D(0) when (I_DDDDD = "11111") else '0';

```

src/register_file.vhd

The second case is a write to a 16-bit register pair addressed by **DDDD** (**DDDD** is the four upper bits of **DDDDDD**). For this case we create signal **WE_DD**:

```

326      L_DDDD      <= I_DDDDD(4 downto 1);
327      L_WE_D2      <= I_WE_D(1) & I_WE_D(1);
328      L_WE_DD( 1 downto 0)      <= L_WE_D2 when (L_DDDD = "0000") else "00";
329      L_WE_DD( 3 downto 2)      <= L_WE_D2 when (L_DDDD = "0001") else "00";
330      L_WE_DD( 5 downto 4)      <= L_WE_D2 when (L_DDDD = "0010") else "00";
331      L_WE_DD( 7 downto 6)      <= L_WE_D2 when (L_DDDD = "0011") else "00";
332      L_WE_DD( 9 downto 8)      <= L_WE_D2 when (L_DDDD = "0100") else "00";
333      L_WE_DD(11 downto 10)     <= L_WE_D2 when (L_DDDD = "0101") else "00";
334      L_WE_DD(13 downto 12)     <= L_WE_D2 when (L_DDDD = "0110") else "00";
335      L_WE_DD(15 downto 14)     <= L_WE_D2 when (L_DDDD = "0111") else "00";
336      L_WE_DD(17 downto 16)     <= L_WE_D2 when (L_DDDD = "1000") else "00";
337      L_WE_DD(19 downto 18)     <= L_WE_D2 when (L_DDDD = "1001") else "00";
338      L_WE_DD(21 downto 20)     <= L_WE_D2 when (L_DDDD = "1010") else "00";
339      L_WE_DD(23 downto 22)     <= L_WE_D2 when (L_DDDD = "1011") else "00";
340      L_WE_DD(25 downto 24)     <= L_WE_D2 when (L_DDDD = "1100") else "00";
341      L_WE_DD(27 downto 26)     <= L_WE_D2 when (L_DDDD = "1101") else "00";
342      L_WE_DD(29 downto 28)     <= L_WE_D2 when (L_DDDD = "1110") else "00";
343      L_WE_DD(31 downto 30)     <= L_WE_D2 when (L_DDDD = "1111") else "00";

```

src/register_file.vhd

The third case is writing to the memory mapped I/O space of the general purpose registers. It is similar to the first case, but now we select the register by **ADR** instead of **DDDDDD**. When reading from the I/O mapped register above we did not check if **ADR** was completely correct (and different addresses could read the same register). This was OK, since some multiplexer somewhere else would discard the value read for addresses outside the range from 0x00 to 0x1F. When writing we have to be more careful and check the range by means of **WE_A**. For the third case we use signal **WE_IO**:

6 DATA PATH

```

350      L_WE_IO( 0)      <= L_WE_A when (L_ADR(4 downto 0) = "00000") else '0';
351      L_WE_IO( 1)      <= L_WE_A when (L_ADR(4 downto 0) = "00001") else '0';
352      L_WE_IO( 2)      <= L_WE_A when (L_ADR(4 downto 0) = "00010") else '0';
353      L_WE_IO( 3)      <= L_WE_A when (L_ADR(4 downto 0) = "00011") else '0';
354      L_WE_IO( 4)      <= L_WE_A when (L_ADR(4 downto 0) = "00100") else '0';
355      L_WE_IO( 5)      <= L_WE_A when (L_ADR(4 downto 0) = "00101") else '0';
356      L_WE_IO( 6)      <= L_WE_A when (L_ADR(4 downto 0) = "00110") else '0';
357      L_WE_IO( 7)      <= L_WE_A when (L_ADR(4 downto 0) = "00111") else '0';
358      L_WE_IO( 8)      <= L_WE_A when (L_ADR(4 downto 0) = "01000") else '0';
359      L_WE_IO( 9)      <= L_WE_A when (L_ADR(4 downto 0) = "01001") else '0';
360      L_WE_IO(10)     <= L_WE_A when (L_ADR(4 downto 0) = "01010") else '0';
361      L_WE_IO(11)     <= L_WE_A when (L_ADR(4 downto 0) = "01011") else '0';
362      L_WE_IO(12)     <= L_WE_A when (L_ADR(4 downto 0) = "01100") else '0';
363      L_WE_IO(13)     <= L_WE_A when (L_ADR(4 downto 0) = "01101") else '0';
364      L_WE_IO(14)     <= L_WE_A when (L_ADR(4 downto 0) = "01110") else '0';
365      L_WE_IO(15)     <= L_WE_A when (L_ADR(4 downto 0) = "01111") else '0';
366      L_WE_IO(16)     <= L_WE_A when (L_ADR(4 downto 0) = "10000") else '0';
367      L_WE_IO(17)     <= L_WE_A when (L_ADR(4 downto 0) = "10001") else '0';
368      L_WE_IO(18)     <= L_WE_A when (L_ADR(4 downto 0) = "10010") else '0';
369      L_WE_IO(19)     <= L_WE_A when (L_ADR(4 downto 0) = "10011") else '0';
370      L_WE_IO(20)     <= L_WE_A when (L_ADR(4 downto 0) = "10100") else '0';
371      L_WE_IO(21)     <= L_WE_A when (L_ADR(4 downto 0) = "10101") else '0';
372      L_WE_IO(22)     <= L_WE_A when (L_ADR(4 downto 0) = "10110") else '0';
373      L_WE_IO(23)     <= L_WE_A when (L_ADR(4 downto 0) = "10111") else '0';
374      L_WE_IO(24)     <= L_WE_A when (L_ADR(4 downto 0) = "11000") else '0';
375      L_WE_IO(25)     <= L_WE_A when (L_ADR(4 downto 0) = "11001") else '0';
376      L_WE_IO(26)     <= L_WE_A when (L_ADR(4 downto 0) = "11010") else '0';
377      L_WE_IO(27)     <= L_WE_A when (L_ADR(4 downto 0) = "11011") else '0';
378      L_WE_IO(28)     <= L_WE_A when (L_ADR(4 downto 0) = "11100") else '0';
379      L_WE_IO(29)     <= L_WE_A when (L_ADR(4 downto 0) = "11101") else '0';
380      L_WE_IO(30)     <= L_WE_A when (L_ADR(4 downto 0) = "11110") else '0';
381      L_WE_IO(31)     <= L_WE_A when (L_ADR(4 downto 0) = "11111") else '0';

```

src/register_file.vhd

The last case for writing is handled by **WE_MISC**. The various multiplication opcodes write their result to register pair 0; this case is indicated the the **WE_01** input. Then we have the pre-decrement and post-increment addressing modes that update the **X**, **Y**, or **Z** register:

```

389      L_WE_X      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WX) else '0';
390      L_WE_Y      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WY) else '0';
391      L_WE_Z      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WZ) else '0';
392      L_WE_MISC   <= L_WE_Z & L_WE_Z &      -- -Z and Z+ address modes r30
393                      L_WE_Y & L_WE_Y &      -- -Y and Y+ address modes r28
394                      L_WE_X & L_WE_X &      -- -X and X+ address modes r26
395                      X"000000" &      -- never                  r24 - r02
396                      I_WE_01 & I_WE_01;    -- multiplication result r00

```

src/register_file.vhd

The final **WE** signal is then computed by **or**'ing the four cases above:

6 DATA PATH

```
398      L_WE      <= L_WE_D or L_WE_DD or L_WE_IO or L_WE_MISC;  
src/register_file.vhd
```

The stack pointer can be updated from two sources: from **DIN** as a memory mapped I/O or implicitly from **XYZS** by addressing modes (e.g. for **CALL**, **RET**, **PUSH**, and **POP** instructions) that write to the **SP** (**AM_WS**).

```
280      L_DSP      <= L_XYZS when (I_AMOD(3 downto 0) = AM_WS) else I_DIN;  
src/register_file.vhd
```

The status register can be written as memory mapped I/O from the **DIN** input or from the **FLAGS** input (from the ALU). The **WE_SR** input (for memory mapped I/O) and the **WE_FLAGS** input (for flags set as side effect of ALU operations) control from where the new value comes:

```
272      L_WE_SR      <= I_WE_M when (L_ADR = X"005F") else '0';  
src/register_file.vhd
```

```
152          I_DIN      => I_DIN(7 downto 0),  
153          I_FLAGS    => I_FLAGS,  
154          I_WE_F     => I_WE_F,
```

```
src/register_file.vhd
```

6.1.9 Addressing Modes

The CPU provides a number of addressing modes. An addressing mode is a way to compute an address. The address specifies a location in the program memory, the data memory, the I/O memory, or some general purpose register. Computing an address can have side effects such as incrementing or decrementing a pointer register.

The addressing mode to be used (if any) is encoded in the **AMOD** signal. The **AMOD** signal consists of two sub-fields: the address source and the address offset.

6 DATA PATH

There are 5 possible address sources:

```

84      constant AS_SP  : std_logic_vector(2 downto 0) := "000";      -- SP
85      constant AS_Z   : std_logic_vector(2 downto 0) := "001";      -- Z
86      constant AS_Y   : std_logic_vector(2 downto 0) := "010";      -- Y
87      constant AS_X   : std_logic_vector(2 downto 0) := "011";      -- X
88      constant AS_IMM : std_logic_vector(2 downto 0) := "100";      -- IMM

```

src/common.vhd

The address sources **AS_SP**, **AS_X**, **AS_Y**, and **AS_Z** are the stack pointer, the **X** register pair, the **Y** register pair, or the **Z** register pair. The **AS_IMM** source is the **IMM** input (which was computed from the opcode in the opcode decoder).

There are 6 different address offsets. An address offset can imply a side effect like incrementing or decrementing the address source. The lowest bit of the address offset indicates whether a side effect is intended or not:

```

91      constant AO_0   : std_logic_vector(5 downto 3) := "000";      -- as is
92      constant AO_Q   : std_logic_vector(5 downto 3) := "010";      -- +q
93      constant AO_i   : std_logic_vector(5 downto 3) := "001";      -- +1
94      constant AO_ii  : std_logic_vector(5 downto 3) := "011";      -- +2
95      constant AO_d   : std_logic_vector(5 downto 3) := "101";      -- -1
96      constant AO_dd  : std_logic_vector(5 downto 3) := "111";      -- -2

```

src/common.vhd

The address offset **AO_0** does nothing; the address source is not modified. Address offset **AO_Q** adds some constant **q** to the address source; the constant **q** is provided on the **IMM** input (thus derived from the opcode). Address offsets **AO_i** resp. **AO_ii** increment the address source after the operation by 1 resp. 2 bytes. The address computed is the address source. Address offsets **AO_d** resp. **AO_dd** decrement the address source before the operation by 1 resp. 2 bytes. The address computed is the address source minus 1 or 2.

The constants **AM_WX**, **AM_WY**, **AM_WZ**, and **AM_WS** respectively indicate if the **X**, **Y**, **Z**, or **SP** registers will be updated and are used to decode the **WE_XYZS** signal to the register concerned and to select the proper inputs:

```

389      L_WE_X      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WX) else '0';
390      L_WE_Y      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WY) else '0';
391      L_WE_Z      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WZ) else '0';
392      L_WE_MISC   <= L_WE_Z & L_WE_Z &           -- -Z and Z+ address modes r30
393                           L_WE_Y & L_WE_Y &           -- -Y and Y+ address modes r28

```

6 DATA PATH

```
394          L_WE_X & L_WE_X &           -- -X and X+ address modes r26
src/register_file.vhd
```

```
277      L_DX      <= L_XYZS when (L_WE_MISC(26) = '1')      else I_DIN;
278      L_DY      <= L_XYZS when (L_WE_MISC(28) = '1')      else I_DIN;
279      L_DZ      <= L_XYZS when (L_WE_MISC(30) = '1')      else I_DIN;
280      L_DSP     <= L_XYZS when (I_AMOD(3 downto 0) = AM_WS) else I_DIN;
```

```
src/register_file.vhd
```


Not all combinations of address source and address offset occur; only the following combinations are needed:

```
108      constant AMOD_ABS : std_logic_vector(5 downto 0) := AO_0 & AS_IMM; -- IMM
109      constant AMOD_X   : std_logic_vector(5 downto 0) := AO_0 & AS_X;    -- (X)
110      constant AMOD_Xq  : std_logic_vector(5 downto 0) := AO_Q & AS_X;    -- (X+q)
111      constant AMOD_Xi  : std_logic_vector(5 downto 0) := AO_i & AS_X;    -- (X++)
112      constant AMOD_dX  : std_logic_vector(5 downto 0) := AO_d & AS_X;    -- (--X)
113      constant AMOD_Y   : std_logic_vector(5 downto 0) := AO_0 & AS_Y;    -- (Y)
114      constant AMOD_Yq  : std_logic_vector(5 downto 0) := AO_Q & AS_Y;    -- (Y+q)
115      constant AMOD_Yi  : std_logic_vector(5 downto 0) := AO_i & AS_Y;    -- (Y++)
116      constant AMOD_dY  : std_logic_vector(5 downto 0) := AO_d & AS_Y;    -- (--Y)
117      constant AMOD_Z   : std_logic_vector(5 downto 0) := AO_0 & AS_Z;    -- (Z)
118      constant AMOD_Zq  : std_logic_vector(5 downto 0) := AO_Q & AS_Z;    -- (Z+q)
119      constant AMOD_Zi  : std_logic_vector(5 downto 0) := AO_i & AS_Z;    -- (Z++)
120      constant AMOD_dZ  : std_logic_vector(5 downto 0) := AO_d & AS_Z;    -- (--Z)
121      constant AMOD_SPi : std_logic_vector(5 downto 0) := AO_i & AS_SP;   -- (SP++)
122      constant AMOD_SPii: std_logic_vector(5 downto 0) := AO_ii & AS_SP;  -- (SP++)
123      constant AMOD_dSP : std_logic_vector(5 downto 0) := AO_d & AS_SP;   -- (--SP)
124      constant AMOD_ddSP: std_logic_vector(5 downto 0) := AO_dd & AS_SP;  -- (--SP)
```

```
src/common.vhd
```

The following figure shows the computation of addresses:

6 DATA PATH

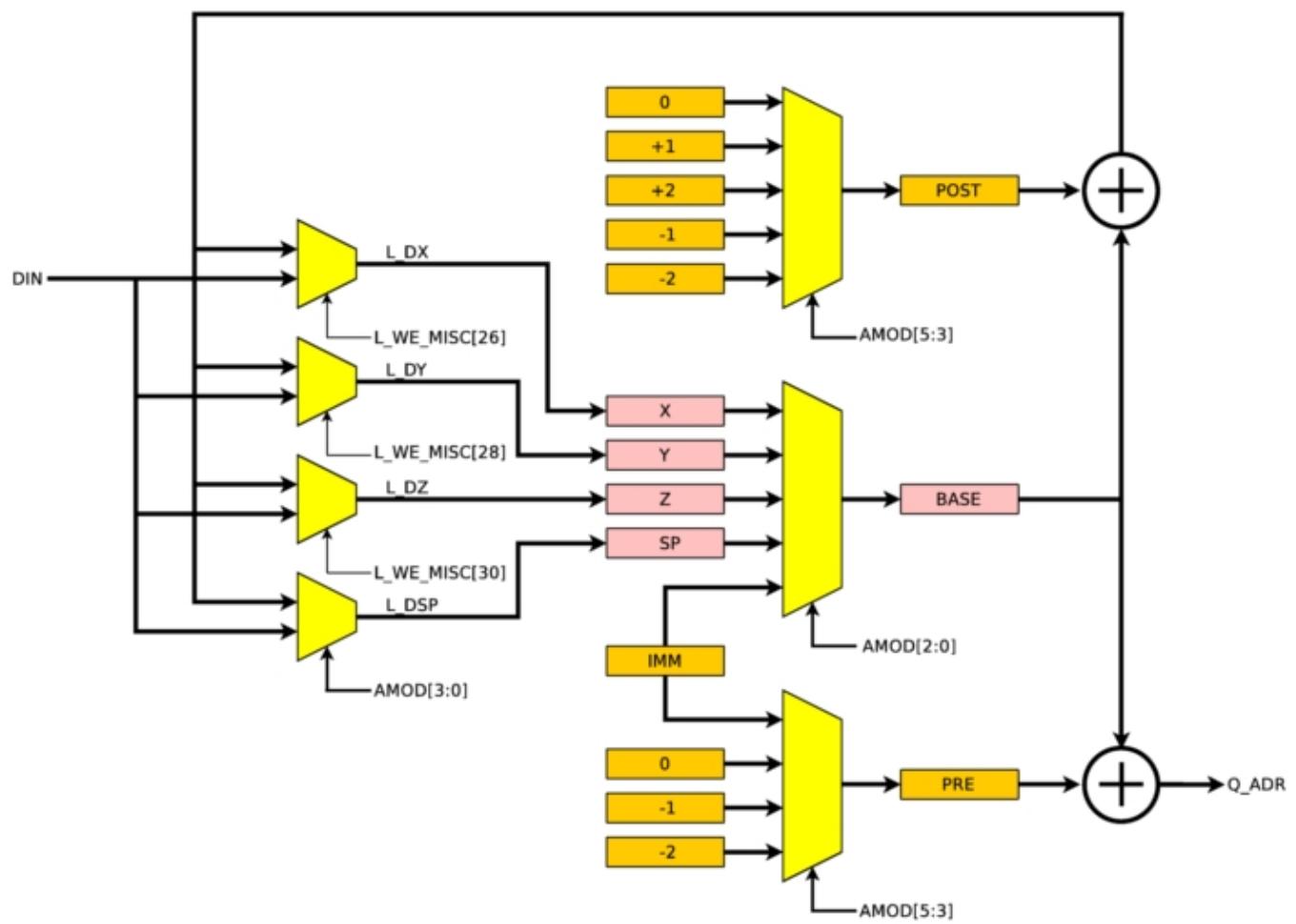

6.2 Data memory

The data memory is conceptually an 8-bit memory. However, some instructions (e.g. CALL, RET) write two bytes to consecutive memory locations. We do the same trick as for the program memory and divide the data memory into an even half and an odd half. The only new thing is a multiplexer at the input:

```
179      L_DIN_E      <= I_DIN( 7 downto 0) when (I_ADDR(0) = '0') else I_DIN(15 downto 8);
180      L_DIN_O      <= I_DIN( 7 downto 0) when (I_ADDR(0) = '1') else I_DIN(15 downto 8);

src/data_mem.vhd
```

The multiplexer is needed because the data memory is a read/write memory while the program memory was read-only. The multiplexer swaps the upper and lower bytes of **DIN** when writing to odd addresses.

6.3 Arithmetic/Logic Unit (ALU)

The most obvious component of a CPU is the ALU where all arithmetic and logic operations are computed. We do a little trick here and implement the data move instructions (**MOV**, **LD**, **ST**, etc.) as ALU operations that simply moves the data source to the output of the ALU. The data move instructions can use the same data paths as the arithmetic and logic instructions.

If we look at the instructions set of the CPU then we see that a number of instructions are quite similar. We use these similarities to reduce the number of different instructions that need to be implemented in the ALU.

- Some instructions have 8-bit and 16-bit variants (e.g. **ADD** and **ADIW**).
- Some instructions have immediate variants (e.g. **CMP** and **CMPI**).
- Some instructions differ only in whether they update the destination register or not (e.g. **CMP** and **SUB**).

The ALU is a completely combinational circuit and therefore it has no clock input. We can divide the ALU into a number of blocks that are explained in the following.

6.3.1 D Input Multiplexing.

We have seen earlier that the **D** input of the ALU is the output of the register pair addressed by **DDDDD[4:1]** and that the **D0** input of the ALU is **DDDDD[0]**:

```
178      Q_D      => F_D,
src/data_path.vhd
```

6 DATA PATH

```
146      I_D      => F_D,  
147      I_D0     => I_DDDDD(0),
```

src/data_path.vhd

If **D0** is zero, then the lower byte of the ALU operation comes from the even register regardless of the size (8-bit or 16-bit) of the operation. If **D0** is odd, then the lower byte of the ALU operation comes from the odd register of the pair (and must be an 8-bit operation since register pairs always have the lowest bit of **DDDDD** cleared).

The upper byte of the operation (if any) is always the odd register of the pair.

We can therefore compute the lower byte, called **D8**, from **D** and **D0**:

```
356      L_D8      <= I_D(15 downto 8) when (I_D0 = '1') else I_D(7 downto 0);
```

src/alu.vhd

6.3.2 **R** and **IMM** Input Multiplexing.

Multiplexing of the **R** input works like multiplexing of the **D** input. Some opcodes can have immediate operand instead of a register addressed by **RRRRR**. We compute the signal **R8** for opcodes that cannot have an immediate operand, and **RI8** for opcodes that can have an immediate operand.

This is some fine tuning of the design: the **MULT** opcodes can take a while to compute but cannot have an immediate operand. It makes therefore sense to have a path from the register addressed by **RRRRR** to the multiplier and to put the register/immediate multiplexer outside that critical path through the ALU.

```
357      L_R8      <= I_R(15 downto 8) when (I_R0 = '1') else I_R(7 downto 0);  
358      L_RI8     <= I_IMM      when (I_RSEL = RS_IMM) else L_R8;
```

src/alu.vhd

6.3.3 Arithmetic and Logic Functions

The first step in the computation of the arithmetic and logic functions is to compute a number of helper values. The reason for computing them beforehand is that we need these values several times, either for

6 DATA PATH

different but similar opcodes (e.g. **CMP** and **SUB**) but also for the result and for the flags of the same opcode.

```

360      L_ADIW_D      <= I_D + ("0000000000" & I_IMM(5 downto 0));
361      L_SBIW_D      <= I_D - ("0000000000" & I_IMM(5 downto 0));
362      L_ADD_DR      <= L_D8 + L_RI8;
363      L_ADC_DR      <= L_ADD_DR + ("0000000" & I_FLAGS(0));
364      L_ASR_D       <= L_D8(7) & L_D8(7 downto 1);
365      L_AND_DR      <= L_D8 and L_RI8;
366      L_DEC_D       <= L_D8 - X"01";
367      L_INC_D       <= L_D8 + X"01";
368      L_LSR_D       <= '0' & L_D8(7 downto 1);
369      L_NEG_D        <= X"00" - L_D8;
370      L_NOT_D        <= not L_D8;
371      L_OR_DR        <= L_D8 or L_RI8;
372      L_PROD          <= (L_SIGN_D & L_D8) * (L_SIGN_R & L_R8);
373      L_ROR_D        <= I_FLAGS(0) & L_D8(7 downto 1);
374      L_SUB_DR      <= L_D8 - L_RI8;
375      L_SBC_DR      <= L_SUB_DR - ("0000000" & I_FLAGS(0));
376      L_SIGN_D       <= L_D8(7) and I_IMM(6);
377      L_SIGN_R       <= L_R8(7) and I_IMM(5);
378      L_SWAP_D       <= L_D8(3 downto 0) & L_D8(7 downto 4);
379      L_XOR_DR      <= L_D8 xor L_R8;

```

src/alu.vhd

Most values should be obvious, but a few deserve an explanation: There is a considerable number of multiplication functions that only differ in the signedness of their operands. Instead of implementing a different 8-bit multiplier for each opcode, we use a common signed 9-bit multiplier for all opcodes. The opcode decoder sets bits 6 and/or 5 of the **IMM** input if the **D** operand and/or the **R** operand is signed. The signs of the operands are then **SIGN_D** and **SIGN_R**; they are 0 for unsigned operations. Next the signs are prepended to the operands so that each operand is 9-bit signed. If the operand was unsigned (and the sign was 0) then the new signed 9-bit operand is positive. If the operand was signed and positive (and the sign was 0 again) then the new operand is positive again. If the operand was signed and negative, then the sign was 1 and the new operand is also negative.

6.3.4 Output and Flag Multiplexing

The necessary computations in the ALU have already been made in the previous section. What remains is to select the proper result and setting the flags. The output **DOUT** and the flags are selected by **ALU_OP**. We take the first two values of **ALU_OP** as an example and leave the remaining ones as an exercise for the reader.

```

118      process (L_ADC_DR, L_ADD_DR, L_ADIW_D, I_ALU_OP, L_AND_DR, L_ASR_D,
119                  I_BIT, I_D, L_D8, L_DEC_D, I_DIN, I_FLAGS, I_IMM, L_MASK_I,
120                  L_INC_D, L_LSR_D, L_NEG_D, L_NOT_D, L_OR_DR, I_PC, L_PROD,
121                  I_R, L_RI8, L_RBIT, L_ROR_D, L_SBIW_D, L_SUB_DR, L_SBC_DR,
122                  L_SIGN_D, L_SIGN_R, L_SWAP_D, L_XOR_DR)
123      begin

```

6 DATA PATH

```

124      Q_FLAGS(9)      <= L_RBIT xor not I_BIT(3);      -- DIN[BIT] = BIT[3]
125      Q_FLAGS(8)      <= ze(L_SUB_DR);                  -- D == R for CPSE
126      Q_FLAGS(7 downto 0)    <= I_FLAGS;
127      L_DOUT        <= X"0000";
128
129      case I_ALU_OP is
130          when ALU_ADC =>
131              L_DOUT      <= L_ADC_DR & L_ADC_DR;
132              Q_FLAGS(0)  <= cy(L_D8(7), L_RI8(7), L_ADC_DR(7));  -- Carry
133              Q_FLAGS(1)  <= ze(L_ADC_DR);                      -- Zero
134              Q_FLAGS(2)  <= L_ADC_DR(7);                      -- Negative
135              Q_FLAGS(3)  <= ov(L_D8(7), L_RI8(7), L_ADC_DR(7));  -- Overflow
136              Q_FLAGS(4)  <= si(L_D8(7), L_RI8(7), L_ADC_DR(7));  -- Signed
137              Q_FLAGS(5)  <= cy(L_D8(3), L_RI8(3), L_ADC_DR(3));  -- Halfcarry
138
139          when ALU_ADD =>
140              L_DOUT      <= L_ADD_DR & L_ADD_DR;
141              Q_FLAGS(0)  <= cy(L_D8(7), L_RI8(7), L_ADD_DR(7));  -- Carry
142              Q_FLAGS(1)  <= ze(L_ADD_DR);                      -- Zero
143              Q_FLAGS(2)  <= L_ADD_DR(7);                      -- Negative
144              Q_FLAGS(3)  <= ov(L_D8(7), L_RI8(7), L_ADD_DR(7));  -- Overflow
145              Q_FLAGS(4)  <= si(L_D8(7), L_RI8(7), L_ADD_DR(7));  -- Signed
146              Q_FLAGS(5)  <= cy(L_D8(3), L_RI8(3), L_ADD_DR(3));  -- Halfcarry

```

src/alu.vhd

First of all, the default values for the flags and the ALU output are chosen. The default of **L_OUT** is 0, while the default for **O_FLAGS** is **I_FLAGS**. This means that all flags that are not explicitly changed remain the same. The upper two flag bits are set according to specific needs of certain skip instructions (CPSE, SBIC, SBIS, SBRC, and SBRS).

Then comes a big case statement for which we explain only the first two cases, **ALU_ADC** and **ALU_ADD**.

The expected value of **DOUT** was already computed as **L_ADC_DR** in the previous section and this value is assigned to **DOUT**.

After that the flags that can change in the execution of the **ADC** opcode are computed. The computation of flags is very similar for a number of different opcodes. We have therefore defined functions **cy()**, **ze()**, **ov()**, and **si()** for the usual way of computing these flags:

The half-carry flags is computed like the carry flag but on bits 3 rather than bits 7 of the operands and result.

The next example is **ADD**. It is similar to **ADC**, but now **L_ADD_DR** is used instead of **L_ADC_DR**.

6.3.5 Individual ALU Operations

The following table briefly describes how the **DOUT** output of the ALU is computed for the different **ALU_OP** values.

ALU_OP	DOUT	Size
ALU_ADC	D + R + Carry	8-bit
ALU_ADD	D + R	8-bit

6 DATA PATH

ALUADIW	D + IMM	16-bit
ALUAND	D and R	8-bit
ALUASR	D >> 1	8-bit
ALUBLD	T-flag << IMM	8-bit
ALUBST	(set T-flag)	8-bit
ALUCOM	not D	8-bit
ALUDEC	D - 1	8-bit
ALUEOR	D xor R	8-bit
ALUIN	DIN	8-bit
ALUINC	D + 1	8-bit
ALULSR	D >> 1	8-bit
ALUDMOVQD	D	16-bit
ALURMOVQR	R	16-bit
ALUMULT	D * R	16-bit
ALUNEG	0 - D	8-bit
ALUOR	A or R	8-bit
ALUPC	PC	16-bit
ALUPC_1	PC + 1	16-bit
ALUPC_2	PC + 2	16-bit
ALUROR	D rotated right	8-bit
ALUSBC	D - R - Carry	8-bit
ALUSBIW	D - IMM	16-bit
ALUSREG	(set a flag)	8-bit
ALUSUB	D - R	8-bit
ALU_SWAP	D[3:0] & D[7:4]	8-bit

For all 8-bit computations, the result is placed onto the upper and onto the lower byte of **L_DOUT**. This saves a multiplexer at the inputs of the registers.

The final result of the ALU is obtained by multiplexing the local result **L_DOUT** and **DIN** based on **I_RSEL**.

```
381          Q_DOUT      <= (I_DIN & I_DIN) when (I_RSEL = RS_DIN) else L_DOUT;
src/alu.vhd
```

We could have placed this multiplexer at the **R** input (combined with the multiplexer for the **DIN** input) or at the **DOUT** output. Placing it at the output gives a better timing, since the opcodes using the **DIN** input do not perform ALU operations.

6.3.5 Temporary Z and T Flags

There are two opcodes that use the value of the **Z** flag (**CPSE**) or the #T flag (**SBIC**, **SBIS**) without setting them. For timing reasons, they are executed in two cycles - one cycle for performing a comparison or a bit access and a second cycle for actually making the decision to skip the next instruction or not.

For this reason we have introduced copies of the **Z** and **T** flags and called them **FLAGS_98**. They store the values of these flags within an instruction, but without updating the status register. The two flags are computed in the ALU:

```
124      Q_FLAGS(9)      <= L_RBIT xor not I_BIT(3);      -- DIN[BIT] = BIT[3]
125      Q_FLAGS(8)      <= ze(L_SUB_DR);                  -- D == R for CPSE
src/alu.vhd
```

The result is stored in the data path:

```
195      flg98: process(I_CLK)
196      begin
197          if (rising_edge(I_CLK)) then
198              L_FLAGS_98      <= A_FLAGS(9 downto 8);
199          end if;
200      end process;
```

src/data_path.vhd

6.4 Other Functions

Most of the data path is contained in its components **alu**, **register_file**, and **data_mem**. A few things are written directly in VHDL and shall be explained here.

Some output signals are driven directly from inputs or from instantiated components:

```
231      Q_ADR      <= F_ADR;
232      Q_DOUT     <= A_DOUT(7 downto 0);
233      Q_INT_ENA   <= A_FLAGS(7);
234      Q_OPC       <= I_OPC;
235      Q_PC        <= I_PC;
```

src/data_path.vhd

6 DATA PATH

The address space of the data memory is spread over the register file (general purpose registers, stack pointer, and status register), the data RAM, and the external I/O registers outside of the data path. The external I/O registers reach from 0x20 to 0x5C (including) and the data RAM starts at 0x60. We generate write enable signals for these address ranges, and a read strobe for external I/O registers. We also control the multiplexer at the input of the ALU by the address output of the register file:

```

237      Q_RD_IO      <= '0'                                when (F_ADR <X"20")
238      else (I_RD_M and not I_PMS) when (F_ADR        <X"5D")
239      else '0';
240      Q_WE_IO      <= '0'                                when (F_ADR <X"20")
241      else I_WE_M(0)       when (F_ADR        <X"5D")
242      else '0';
243      L_WE_SRAM    <= "00"     when (F_ADR <X"0060") else I_WE_M;
244      L_DIN        <= I_DIN     when (I_PMS = '1')
245      else F_S      when (F_ADR        <X"0020")
246      else I_DIN    when (F_ADR        <X"005D")
247      else F_S      when (F_ADR        <X"0060")
248      else M_DOUT(7 downto 0);

```

src/data_path.vhd

Most instructions that modify the program counter (other than incrementing it) use addresses that are being provided on the **IMM** input (from the opcode decoder).

The two exceptions are the **IJMP** instruction where the new **PC** value is the value of the **Z** register pair, and the **RET** and **RETI** instructions where the new **PC** value is popped from the stack. The new value of the **PC** (if any) is therefore:

```

252      Q_NEW_PC    <= F_Z      when I_PC_OP = PC_LD_Z      -- IJMP, ICALL
253      else M_DOUT when I_PC_OP = PC_LD_S      -- RET, RETI
254      else I_JADR;                          -- JMP adr

```

src/data_path.vhd

Conditional branches use the **CC** output of the register file in order to decide whether the branch shall be taken or not. The opcode decoder drives the **COND** input according to the relevant bit in the status register (**I_COND[2:0]**) and according to the expected value (**COND[3]**) of that bit.

The **LOAD_PC** output is therefore '1' for unconditional branches and **CC** for conditional branches:

```
205      process(I_PC_OP, F_CC)
```

6 DATA PATH

```

206      begin
207          case I_PC_OP is
208              when PC_BCC => Q_LOAD_PC      <= F_CC;      -- maybe (PC on I_JADR)
209              when PC_LD_I => Q_LOAD_PC      <= '1';      -- yes: new PC on I_JADR
210              when PC_LD_Z => Q_LOAD_PC      <= '1';      -- yes: new PC in Z
211              when PC_LD_S => Q_LOAD_PC      <= '1';      -- yes: new PC on stack
212              when others   => Q_LOAD_PC      <= '0';      -- no.
213          end case;
214      end process;

```

src/data_path.vhd

When a branch is taken (in the execution stage of the pipeline), then the next instruction after the branch is about to be decoded in the opcode decoder stage. This instruction must not be executed, however, and we therefore invalidate it by asserting the **SKIP** output. Another case where instructions need to be invalidated are skip instructions (**CPSE**, **SBIC**, **SBIS**, **SBRC**, and **SBRS**). These instructions do not modify the **PC**, but they nevertheless cause the next instruction to be invalidated:

```

218      process(I_PC_OP, L_FLAGS_98, F_CC)
219      begin
220          case I_PC_OP is
221              when PC_BCC => Q_SKIP      <= F_CC;      -- if cond met
222              when PC_LD_I => Q_SKIP      <= '1';      -- yes
223              when PC_LD_Z => Q_SKIP      <= '1';      -- yes
224              when PC_LD_S => Q_SKIP      <= '1';      -- yes
225              when PC_SKIP_Z => Q_SKIP      <= L_FLAGS_98(8); -- if Z set
226              when PC_SKIP_T => Q_SKIP      <= L_FLAGS_98(9); -- if T set
227              when others   => Q_SKIP      <= '0';      -- no.
228          end case;
229      end process;

```

src/data_path.vhd

This concludes the discussion of the data path. We have now installed the environment that is needed to execute opcodes.

7 OPCODE DECODER

In this lesson we will describe the opcode decoder. We will also learn how the different instructions provided by the CPU will be implemented. We will not describe every opcode, but rather groups of instructions whose individual instructions are rather similar.

The opcode decoder is the middle state of our CPU pipeline. Therefore its inputs are defined by the outputs of the previous stage and its outputs are defined by the inputs of the next stage.

7.1 Inputs of the Opcode Decoder

- **CLK** is the clock signal. The opcode decoder is a pure pipeline stage so that no internal state is kept between clock cycles. The output of the opcode decoder is a pure function of its inputs.
- **OPC** is the opcode being decoded.
- **PC** is the program counter (the address in the program memory from which OPC was fetched).
- **T0** is '1' in the first cycle of the execution of the opcode. This allows for output signals of two-cycle instructions that are different in the first and the second cycle.

7.2 Outputs of the Opcode Decoder

Most data buses of the CPU are contained in the data path. In contrast, most control signals are generated in the opcode decoder. We start with a complete list of these control signals and their purpose. There are two groups of signals: select signals and write enable signals. Select signals are used earlier in the execution of the opcode for controlling multiplexers. The write enable signals are used at the end of the execution to determine where results shall be stored. Select signals are generally more time-critical than write enable signals.

The select signals are:

- **ALU_OP** defines which particular ALU operation (like **ADD**, **ADC**, **AND**, ...) the ALU shall perform.
- **AMOD** defines which addressing mode (like **absolute**, **Z+**, **-SP**, etc.) shall be used for data memory accesses.
- **BIT** is a bit value (0 or 1) and a bit number used in bit instructions.
- **DDDDDD** defines the destination register or register pair (if any) for storing the result of an operation. It also defines the first source register or register pair of a dyadic instructions.
- **IMM** defines an immediate value or branch address that is computed from the opcode.
- **JADR** is a branch address.
- **OPC** is the opcode being decoded, or 0 if the opcode was invalidated by means of **SKIP**.
- **PC** is the **PC** from which **OPC** was fetched.
- **PC_OP** defines an operation to be performed on the **PC** (such as branching).
- **PMS** is set when the address defined by **AMOD** is a program memory address rather than a data memory address.
- **RD_M** is set for reads from the data memory.
- **RRRRR** defines the second register or register pair of a dyadic instruction.
- **RSEL** selects the source of the second operand in the ALU. This can be a register (on the **R** input), an immediate value (on the **IMM** input), or data from memory or I/O (on the **DIN** input).

The write enable signals are:

7 OPCODE DECODER

- **WE_01** is set when register pair 0 shall be written. This is used for multiplication instructions that store the multiplication product in register pair 0.
- **WE_D** is set when the register or register pair **DDDDD** shall be written. If both bits are set then the entire pair shall be written and **DDDDD[0]** is 0. Otherwise **WE_D[1]** is 0, and one of the registers (as defined by **DDDDD[0]**) shall be written,
- **WE_F** is set when the status register (flags) shall be written.
- **WE_M** is set when the memory (including memory mapped general purpose registers and I/O registers) shall be written. If set, then the **AMOD** output defines how to compute the memory address.
- **WE_XYZS** is set when the stack pointer or one of the pointer register pairs **X**, **Y**, or **Z** shall be written. Which of these register is meant is encoded in **AMOD**.

7.3 Structure of the Opcode Decoder

The VHDL code of the opcode decoder consists essentially of a huge case statement. At the beginning of the case statement there is a section assigning a default value to each output. Then follows a case statement that decodes the upper 6 bits of the opcode:

```
66      process (I_CLK)
67      begin
68          if (rising_edge(I_CLK)) then
69              --
70              -- set the most common settings as default.
71              --
72              Q_ALU_OP      <= ALU_D_MV_Q;
73              Q_AMOD        <= AMOD_ABS;
74              Q_BIT         <= I_OPC(10) & I_OPC(2 downto 0);
75              Q_DDDDD       <= I_OPC(8 downto 4);
76              Q_IMM         <= X"0000";
77              Q_JADR        <= I_OPC(31 downto 16);
78              Q_OPC         <= I_OPC(15 downto 0);
79              Q_PC          <= I_PC;
80              Q_PC_OP       <= PC_NEXT;
81              Q_PMS         <= '0';
82              Q_RD_M        <= '0';
83              Q_RRRRR       <= I_OPC(9) & I_OPC(3 downto 0);
84              Q_RSEL        <= RS_REG;
85              Q_WE_D        <= "00";
86              Q_WE_01       <= '0';
87              Q_WE_F        <= '0';
88              Q_WE_M        <= "00";
89              Q_WE_XYZS    <= '0';
90
91          case I_OPC(15 downto 10) is
92              when "000000" =>
93
94                  when others =>
95          end case;
96      end if;
```

```
656      end process;

src/opc_deco.vhd
```

7.4 Default Values for the Outputs

The opcode decoder generates quite a few outputs. A typical instruction, however, only sets a small fraction of them. For this reason we provide a default value for all outputs before the top level case statement, as shown above.

For each instruction we then only need to specify those outputs that differ from the default value.

Every default value is either constant or a function of an input. Therefore the opcode decoder is a typical "stateless" pipeline stage. The default values are chosen so that they do not change anything in the other stages (except incrementing the PC, of course). In particular, the default values for all write enable signals are '0'.

7.5 Checklist for the Design of an Opcode.

Designing an opcode starts with asking a number of questions. The answers are found in the specification of the opcode. The answers identify the outputs that need to be set other than their default values. While the instructions are quite different, the questions are always the same:

1. What operation shall the ALU perform? Set **ALU_OP** and **Q_WE_F** accordingly.
2. Is a destination register or destination register pair used? If so, set **DDDDD** (and **WE_D** if written).
3. Is a second register or register pair involved? If so, set **RRRRR**.
4. Does the opcode access the memory? If so, set **AMOD**, **PMS**, **RSEL**, **RD_M**, **WE_M**, and **WE_XYZS** accordingly.
5. Is an immediate or implied operand used? If so, set **IMM** and **RSEL**.
6. Is the program counter modified (other than incrementing it)? If so, set **PC_OP** and **SKIP**.
7. Is a bit number specified in the opcode ? If so, set **BIT**.
8. Are instructions skipped? If so, set **SKIP**.

Equipped with this checklist we can implement all instructions. We start with the simplest instructions and proceed to the more complex instructions.

7.6 Opcode Implementations

7.6.1 The NOP instruction

The simplest instruction is the NOP instruction which does - nothing. The default values set for all outputs do nothing either so there is no extra VHDL code needed for this instruction.

7.6.2 8-bit Monadic Instructions

We call an instruction **monadic** if its opcode contains one register number and if the instruction reads the register before computing a new value for it.

7 OPCODE DECODER

Only items 1. and 2. in our checklist apply. The default value for **DDDDD** is already correct. Thus only **ALU_OP**, **WE_D**, and **WE_F** need to be set. We take the **DEC Rd** instruction as an example:

```
465      --
466      -- 1001 010d dddd 1010 - DEC
467      --
468      Q_ALU_OP      <= ALU_DEC;
469      Q_WE_D       <= "01";
470      Q_WE_F       <= '1';
```

src/opc_deco.vhd

All monadic arithmetic/logic instructions are implemented in the same way; they differ by their **ALU_OP**.

7.6.3 8-bit Dyadic Instructions, Register/Register

We call an instruction **dyadic** if its opcode contains two data sources (a data source being a register number or an immediate operand). As a consequence of the two data sources, dyadic instructions occupy a larger fraction of the opcode space than monadic functions.

We take the **ADD Rd, Rr** opcode as an example.


Compared to the monadic functions now item 3. in the checklist applies as well. This would mean we have to set **RRRRR** but by chance the default value is already correct. Therefore:

```
165      --
166      -- 0000 11rd dddd rrrr - ADD
167      --
168      Q_ALU_OP      <= ALU_ADD;
169      Q_WE_D       <= "01";
170      Q_WE_F       <= '1';
```

src/opc_deco.vhd

The dyadic instructions do not use the I/O address space and therefore they completely execute inside the data path. The following figure shows the signals in the data path that are used by the **ADD Rd, Rr** instruction:

7 OPCODE DECODER

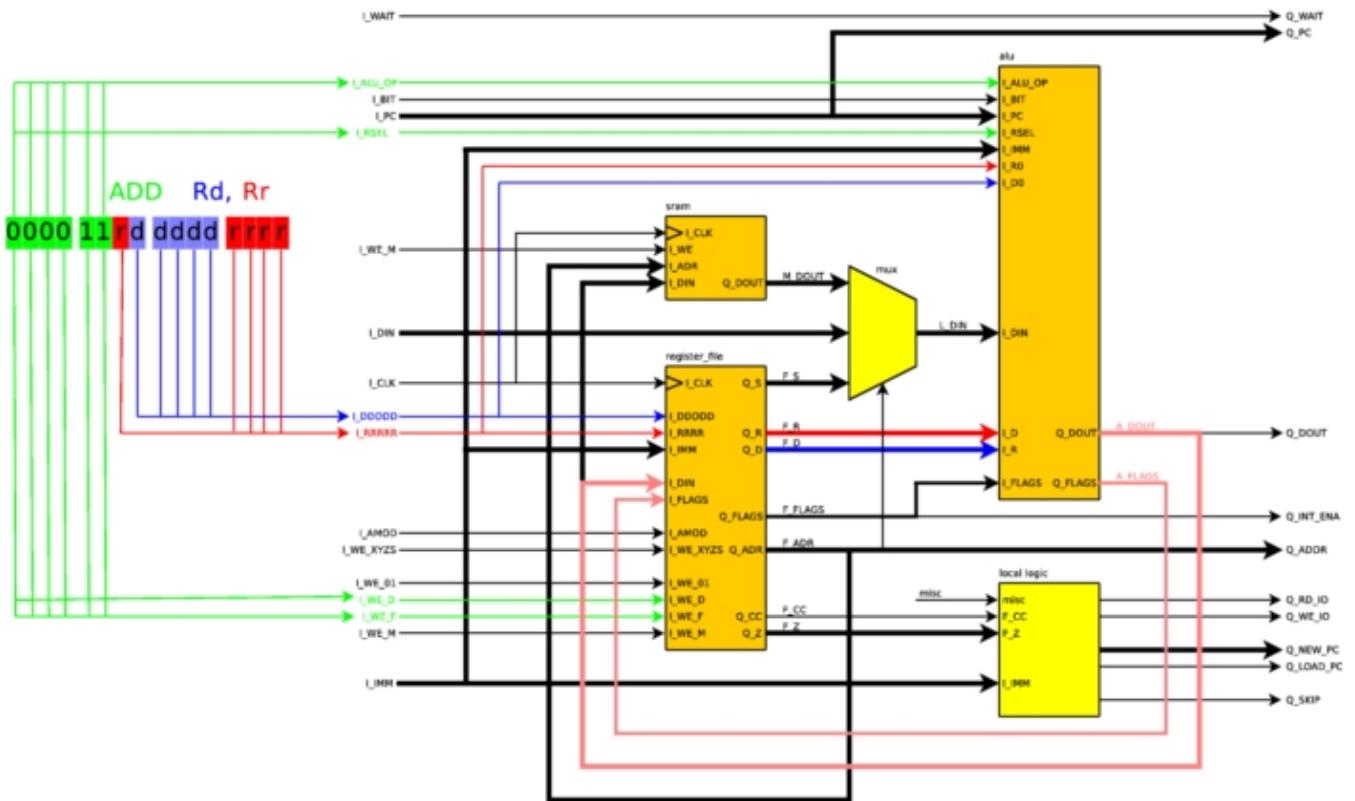

7 OPCODE DECODER

The opcode for **ADD Rd, Rr** is **0000 11rd dddd rrrr**. The opcode decoder extracts the 'd' bits into the **DDDDD** signal (blue), the 'r' bits into the **RRRRR** signal (red), and computes **ALU_OP**, **WE_D**, and **WE_F** from the remaining bits (green) as above.

The register file converts the register numbers **Rd** and **Rr** that are encoded in the **DDDDD** and **RRRRR** signals to the contents of the register pairs at its **D** and **R** outputs. The lowest bit of the **DDDDD** and **RRRRR** signals also go to the ALU (inputs **D0** and **R0**) where the odd/even register selection from the two register pairs is performed.

The decoder also selects the proper **ALU_OP** from the opcode, which is **ALU_ADD** in this example. With this input, the ALU computes the sum of the its **D** and **R** inputs and drives its **DOUT** (pink) with the sum. It also computes the flags as defined for the **ADD** opcode.

The decoder sets the **WE_D** and **WE_F** inputs of the register file so that the **DOUT** and **FLAGS** outputs of the ALU are written back to the register file.

All this happens within a single clock cycle, so that the next instruction can be performed in the next clock cycle.

The other dyadic instructions are implemented similarly. Two instructions, **CMP** and **CPC**, deviate a little since they do not set **WE_D**. Only the flags are set as a result of the comparison. Apart from that, **CMP** and **CPC** are identical to the **SUB** and **SBC**; they don't have their own **ALU_OP** but use those of the **SUB** and **SBC** instructions.

The **MOV Rd, Rr** instruction is implemented as a dyadic function. It ignores its first argument and does not set any flags.

7.6.4 8-bit Dyadic Instructions, Register/Immediate

Some of the dyadic instructions have an immediate operand (i.e. the operand is contained in the opcode) rather than using a second register. For such instructions, for example **ANDI**, we extract the immediate operand from the opcode and set **RSEL**. Since the immediate operand takes quite some space in the opcode, the register range was restricted a little and hence the default **DDDDD** value needs a modification.

```
263      --
264      -- 0111 KKKK dddd KKKK - ANDI
265      --
266      Q_ALU_OP      <= ALU_AND;
267      Q_IMM(7 downto 0)    <= I_OPC(11 downto 8) & I_OPC(3 downto 0);
268      Q_RSEL        <= RS_IMM;
269      Q_DDDDD(4)     <= '1';      -- Rd = 16...31
270      Q_WE_D        <= "01";
271      Q_WE_F        <= '1';
```

src/opc_deco.vhd

7.6.5 16-bit Dyadic Instructions

Some of the dyadic 8-bit instructions have 16-bit variants, for example **ADIW**. The second operand of these 16-bit variants can be another register pair or an immediate operand.

```

499      --
500      -- 1001 0110 KKdd KKKK - ADIW
501      -- 1001 0111 KKdd KKKK - SBIW
502      --
503      if (I_OPCODE(8) = '0') then      Q_ALU_OP      <= ALU_ADIW;
504      else                           Q_ALU_OP      <= ALU_SBIW;
505      end if;
506      Q_IMM(5 downto 4)           <= I_OPCODE(7 downto 6);
507      Q_IMM(3 downto 0)           <= I_OPCODE(3 downto 0);
508      Q_RSEL                  <= RS_IMM;
509      Q_DDDDD                 <= "11" & I_OPCODE(5 downto 4) & "0";
510
511      Q_WE_D                  <= "11";
512      Q_WE_F                  <= '1';

```

src/opc_deco.vhd

These instructions are implemented similar to their 8-bit relatives, but in contrast to them both **WE_D** bits are set. This causes the entire register pair to be updated. **LDI** and **MOVW** are also implemented as 16-bit dyadic instruction.

7.6.6 Bit Instructions

There are some instructions that are very similar to monadic functions (in that they refer to only one register) but have a small immediate operand that addresses a bit in that register. Unlike dyadic functions with immediate operands, these bit instructions do not use the register/immediate multiplexer in the ALU (they don't have a register counterpart for the immediate operand). Instead, the bit number from the instruction is provided on the **BIT** output of the opcode decoder. The **BIT** output has 4 bits; in addition to the (lower) 3 bits needed to address the bit concerned, the fourth (upper) bit indicates the value (bit set or bit cleared) of the bit for those instructions that need it.

The ALU operations related to these bit instructions are **ALU_BLD** and **ALU_BIT_CS**.

ALU_BLD stores the T bit of the status register into a bit in a general purpose register; this is used to implement the **BLD** instruction.

ALU_BIT_CS is a dual-purpose function.

The first purpose is to copy a bit in a general purpose register into the **T** flag of the status register. This use of **ALU_BIT_CS** is selected by setting (only) the **WE_F** signal so that the status register is updated with the new **T** flag. The **BST** instruction is implemented this way. The the bit value in **BIT[3]** is ignored.

7 OPCODE DECODER

The second purpose is to set or clear a bit in an I/O register. The ALU first computes a bitmask where only the bit indicated by **BIT[2:0]** is set. Depending on **BIT[3]** the register is then **or'ed** with the mask or **and'ed** with the complement of the mask. This sets or clears the bit in the current value of the register. This use of **ALU_BIT_CS** is selected by **WE_M** so the I/O register is updated with the new value. The **CBI** and **SBI** instructions are implemented this way.

ALU_BIT_CS is also used by the skip instructions **SBRC** and **SBRC** that are described in the section about branching.

7.6.7 Multiplication Instructions

There is a zoo of multiplication instructions that differ in the signedness of their operands (**MUL**, **MULS**, **MULSU**) and in whether the final result is shifted (**FMUL**, **FMULS**, and **FMULSU**) or not. The opcode decoder sets certain bits in the IMM signal to indicate the type of multiplication:

IMM(7) = 1 shift (FMULxx)

IMM(6) = 1 Rd is signed

IMM(5) = 1 Rr is signed

We also set the **WE_01** instead of the **WE_D** signal because the multiplication result is stored in register pair 0 rather than in the Rd register of the opcode.

```
129          --
130          -- 0000 0011 0ddd 0rrr - _MULSU  SU "010"
131          -- 0000 0011 0ddd 1rrr - FMUL      UU "100"
132          -- 0000 0011 1ddd 0rrr - FMULS     SS "111"
133          -- 0000 0011 1ddd 1rrr - FMULSU   SU "110"
134          --
135          Q_DDDDD(4 downto 3)      <= "10";    -- regs 16 to 23
136          Q_RRRRR(4 downto 3)      <= "10";    -- regs 16 to 23
137          Q_ALU_OP           <= ALU_MULT;
138          if I_OPC(7) = '0' then
139              if I_OPC(3) = '0' then
140                  Q_IMM(7 downto 5)        <= MULT_SU;
141              else
142                  Q_IMM(7 downto 5)        <= MULT_FUU;
143              end if;
144          else
145              if I_OPC(3) = '0' then
146                  Q_IMM(7 downto 5)        <= MULT_FSS;
147              else
148                  Q_IMM(7 downto 5)        <= MULT_FSU;
149              end if;
150          end if;
151          Q_WE_01      <= '1';
152          Q_WE_F       <= '1';
```

src/opc_deco.vhd

7.6.8 Instructions Writing To Memory or I/O

Instructions that write to memory or I/O registers need to set **AMOD**. **AMOD** selects the pointer register involved (**X**, **Y**, **Z**, **SP**, or none). If the addressing mode involves a pointer register and updates it, then **WE_XYZS** needs to be set as well.

The following code fragment shows a number of store functions and how **AMOD** is computed:

```

333
334          --
335          -- 1001 00-1r rrrr 0000 - STS
336          -- 1001 00-1r rrrr 0001 - ST Z+. Rr
337          -- 1001 00-1r rrrr 0010 - ST -Z. Rr
338          -- 1001 00-1r rrrr 1000 - ST Y. Rr
339          -- 1001 00-1r rrrr 1001 - ST Y+. Rr
340          -- 1001 00-1r rrrr 1010 - ST -Y. Rr
341          -- 1001 00-1r rrrr 1100 - ST X. Rr
342          -- 1001 00-1r rrrr 1101 - ST X+. Rr
343          -- 1001 00-1r rrrr 1110 - ST -X. Rr
344          -- 1001 00-1r rrrr 1111 - PUSH Rr
345
346          Q_ALU_OP      <= ALU_D_MV_Q;
347          Q_WE_M       <= "01";
348          Q_WE_XYZS    <= '1';
349          case I_OPC(3 downto 0) is
350              when "0000" => Q_AMOD      <= AMOD_ABS;   Q_WE_XYZS <= '0';
351              when "0001" => Q_AMOD      <= AMOD_Zi;
352              when "0010" => Q_AMOD      <= AMOD_dZ;
353              when "1001" => Q_AMOD      <= AMOD_Yi;
354              when "1010" => Q_AMOD      <= AMOD_dY;
355              when "1100" => Q_AMOD      <= AMOD_X;      Q_WE_XYZS <= '0';
356              when "1101" => Q_AMOD      <= AMOD_Xi;
357              when "1110" => Q_AMOD      <= AMOD_dX;
358              when "1111" => Q_AMOD      <= AMOD_dSP;
359          end case;

```

src/opc_deco.vhd

ALU_OP is set to **ALU_D_MOV_Q**. This causes the source register indicated by **DDDDD** to be switched through the ALU unchanged so that it shows up at the input of the data memory and of the I/O block. We set **WE_M** so that the value of the source register will be written.

Write instructions to memory execute in a single cycle.

7.6.9 Instructions Reading From Memory or I/O

Instructions that read from memory set **AMOD** and possibly **WE_XYZS** in the same way as instructions writing to memory.

The following code fragment shows a number of load functions:

7 OPCODE DECODER

```

297      Q_IMM      <= I_OPCODE(31 downto 16);    -- absolute address for LDS/STS
298      if (I_OPCODE(9) = '0') then           -- LDD / POP
299          --
300          -- 1001 00-0d dddd 0000 - LDS
301          -- 1001 00-0d dddd 0001 - LD Rd, Z+
302          -- 1001 00-0d dddd 0010 - LD Rd, -Z
303          -- 1001 00-0d dddd 0100 - (ii) LPM Rd, (Z)
304          -- 1001 00-0d dddd 0101 - (iii) LPM Rd, (Z+)
305          -- 1001 00-0d dddd 0110 - ELPMD Z      --- not mega8
306          -- 1001 00-0d dddd 0111 - ELPMD Z+     --- not mega8
307          -- 1001 00-0d dddd 1001 - LD Rd, Y+
308          -- 1001 00-0d dddd 1010 - LD Rd, -Y
309          -- 1001 00-0d dddd 1100 - LD Rd, X
310          -- 1001 00-0d dddd 1101 - LD Rd, X+
311          -- 1001 00-0d dddd 1110 - LD Rd, -X
312          -- 1001 00-0d dddd 1111 - POP Rd
313          --
314      Q_RSEL      <= RS_DIN;
315      Q_RD_M      <= I_T0;
316      Q_WE_D      <= '0' & not I_T0;
317      Q_WE_XYZS   <= not I_T0;
318      Q_PMS       <= (not I_OPCODE(3)) and I_OPCODE(2) and (not I_OPCODE(1));
319      case I_OPCODE(3 downto 0) is
320          when "0000" => Q_AMOD      <= AMOD_ABS;   Q_WE_XYZS <= '0';
321          when "0001" => Q_AMOD      <= AMOD_Zi;
322          when "0100" => Q_AMOD      <= AMOD_Z;      Q_WE_XYZS <= '0';
323          when "0101" => Q_AMOD      <= AMOD_Zi;
324          when "1001" => Q_AMOD      <= AMOD_Yi;
325          when "1010" => Q_AMOD      <= AMOD_dY;
326          when "1100" => Q_AMOD      <= AMOD_X;      Q_WE_XYZS <= '0';
327          when "1101" => Q_AMOD      <= AMOD_Xi;
328          when "1110" => Q_AMOD      <= AMOD_dX;
329          when "1111" => Q_AMOD      <= AMOD_SPi;
330          when others =>           Q_WE_XYZS      <= '0';
331      end case;

```

src/opc_deco.vhd

The data read from memory now comes from the **DIN** input. We therefore set **RSEL** to **RS_DIN**. The data read from the memory is again switched through the ALU unchanged, but we use **ALU_R_MOV_Q** instead of **ALU_D_MOV_Q** because the data from memory is now routed via the multiplexer for **R8** rather than via the multiplexer for **D8**. We generate **RD_M** instead of **WE_M** since we are now reading and not writing. The result is stored in the register indicated by **DDDDD**, so we set **WE_D**.

One of the load instructions is **LPM** which reads from program store rather than from the data memory. For this instruction we set **PMS**.

Unlike store instructions, load instructions execute in two cycles. The reason is the internal memory modules which need one clock cycle to produce a result. We therefore generate the **WE_D** and **WE_XYZS** only on the second of the two cycles.

7.6.10 Jump and Call Instructions

7.6.10.1 Unconditional Jump to Absolute Address

The simplest case of a jump instruction is **JMP**, an unconditional jump to an absolute address:

The target address of the jump follows after the instruction. Due to our odd/even trick with the program memory, the target address is provided on the upper 16 bits of the opcode and we need not wait for it. We copy the target address from the upper 16 bits of the opcode to the **IMM** output. Then we set **PC_OP** to **PC_LD_I**:

```
478          --
479          -- 1001 010k kkkk 110k - JMP (k = 0 for 16 bit)
480          -- kkkk kkkk kkkk kkkk
481          --
482          Q_PC_OP      <= PC_LD_I;
```

`src/opc_deco.vhd`

The execution stage will then cause the **PC** to be loaded from its **JADR** input:

```
209          when PC_LD_I => Q_LOAD_PC      <= '1';           -- yes: new PC on I_JADR
src/data_path.vhd
```

The next opcode after the **JMP** is already in the pipeline and would be executed next. We invalidate the next opcode so that it will not be executed:

```
222          when PC_LD_I    => Q_SKIP      <= '1';           -- yes
src/data_path.vhd
```

An instruction similar to **JMP** is **IJMP**. The difference is that the target address of the jump is not provided as an immediate address following the opcode, but is the content of the **Z** register. This case is handled by a different **PC_OP**:

7 OPCODE DECODER

```
450          --
451          -- 1001 0100 0000 1001 IJMP
452          -- 1001 0100 0001 1001 EIJMP  -- not mega8
453          -- 1001 0101 0000 1001 ICALL
454          -- 1001 0101 0001 1001 EICALL -- not mega8
455          --
456          Q_PC_OP      <= PC_LD_Z;
```

src/opc_deco.vhd

The execution stage, which contains the **Z** register, performs the selection of the target address, as we have already seen in the discussion of the data path.

7.6.10.2 Unconditional Jump to Relative Address

The **RJMP** instruction is similar to the **JMP** instruction. The target address of the jump is, however, an address relative to the current **PC** (plus 1). We sign-extend the relative address (by replicating **OPC(11)** until a 16-bit value is reached) and add the current **PC**.

```
580          --
581          -- 1100 kkkk kkkk kkkk - RJMP
582          --
583          Q_JADR      <= I_PC + (I_OPC(11) & I_OPC(11) & I_OPC(11) & I_OPC(11)
584                      & I_OPC(11 downto 0)) + X"0001";
585          Q_PC_OP     <= PC_LD_I;
```

src/opc_deco.vhd

The rest of **RJMP** is the same as for **JMP**.

7.6.10.3 Conditional Jump to Relative Address

There is a number of conditional jump instructions that differ by the bit in the status register that controls whether the branch is taken or not. **BRCS** and **BRCC** branch if bit 0 (the carry flag) is set resp. cleared. **BREQ** and **BRNE** branch if bit 1 (the zero flag) is set resp. cleared, and so on.

There is also a generic form where the bit number is an operand of the opcode. **BRBS** branches if a status register flag is set while **BRBC** branches if a bit is cleared. This means that **BRCS**, **BREQ**, ... are just different names for the **BRBS** instruction, while **BRCC**, **BRNE**, ... are different name for the **BRBC** instruction.

The relative address (i.e. the offset from the PC) for **BRBC/BRBS** is shorter (7 bit) than for **RJMP** (12 bit). Therefore the sign bit of the offset is replicated more often in order to get a 16-bit signed offset that can be added to the **PC**.

7 OPCODE DECODER

```
610      --
611      -- 1111 00kk kkkk kbbb - BRBS
612      -- 1111 01kk kkkk kbbb - BRBC
613      --
614      -- v
615      -- bbb: status register bit
616      -- v: value (set/cleared) of status register bit
617      --
618      Q_JADR      <= I_PC + (I_OPC(9) & I_OPC(9) & I_OPC(9) & I_OPC(9)
619                      & I_OPC(9) & I_OPC(9) & I_OPC(9) & I_OPC(9)
620                      & I_OPC(9) & I_OPC(9 downto 3)) + X"0001";
621
622      Q_PC_OP     <= PC_BCC;
```

src/opc_deco.vhd

The decision to branch or not is taken in the execution stage, because at the time where the conditional branch is decoded, the relevant bit in the status register is not yet valid.

7.6.10.4 Call Instructions

Many unconditional jump instructions have "call" variant. The "call" variant are executed like the corresponding jump instruction. In addition (and at the same time), the **PC** after the instruction is pushed onto the stack. We take **CALL**, the brother of **JMP** as an example:

```
485      --
486      -- 1001 010k kkkk 111k - CALL (k = 0)
487      -- kkkk kkkk kkkk kkkk
488      --
489      Q_ALU_OP      <= ALU_PC_2;
490      Q_AMOD        <= AMOD_ddSP;
491      Q_PC_OP       <= PC_LD_I;
492      Q_WE_M        <= "11";      -- both PC bytes
493      Q_WE_XYZS    <= '1';
```

src/opc_deco.vhd

The new things are an **ALU_OP** of **ALU_PC_2**. The ALU adds 2 to the **PC**, since the **CALL** instructions is 2 words long. The **RCALL** instruction, which is only 1 word long would use **ALU_PC_1** instead. **AMOD** is pre-decrement of the **SP** by 2 (since the return address is 2 bytes long). Both bits of **WE_M** are set since we write 2 bytes.

7.6.10.5 Skip Instructions

Skip instructions do not modify the PC, but they invalidate the next instruction. Like for conditional branch instructions, the condition is checked in the execution stage.

We take **SBIC** as an example:

7 OPCODE DECODER

```

516      --
517      -- 1001 1000 AAAA Abbb - CBI
518      -- 1001 1001 AAAA Abbb - SBIC
519      -- 1001 1010 AAAA Abbb - SBI
520      -- 1001 1011 AAAA Abbb - SBIS
521      --
522      Q_ALU_OP      <= ALU_BIT_CS;
523      Q_AMOD       <= AMOD_ABS;
524      Q_BIT(3)     <= I_OPC(9);   -- set/clear
525
526      -- IMM = AAAAAA + 0x20
527      --
528      Q_IMM(4 downto 0)      <= I_OPC(7 downto 3);
529      Q_IMM(6 downto 5)      <= "01";
530
531      Q_RD_M      <= I_T0;
532      if ((I_OPC(8) = '0') ) then      -- CBI or SBI
533          Q_WE_M(0)      <= '1';
534      else                      -- SBIC or SBIS
535          if (I_T0 = '0') then      -- second cycle.
536              Q_PC_OP      <= PC_SKIP_T;
537          end if;
538      end if;

```

src/opc_deco.vhd

First of all, **AMOD**, **IMM**, and **RSEL** are set such that the value from the I/O register indicated by **IMM** reaches the ALU. **ALU_OP** and **BIT** are set such that the relevant bit reaches **FLAGS_98(9)** in the data path. The access of the bit followed by a skip decision would have taken too long for a single cycle. We therefore extract the bit in the first cycle and store it in the **FLAGS_98(9)** signal in the data path. In the next cycle, the decision to skip or not is taken.

The **PC_OP** of **PC_SKIP_T** causes the **SKIP** output of the execution stage to be raised if **FLAGS_98(9)** is set:

```

226      when PC_SKIP_T => Q_SKIP      <= L_FLAGS_98(9);  -- if T set

```

src/data_path.vhd

A similar instruction is CPSE, which skips the next instruction when a comparison (rather than a bit in an I/O register) indicates equality. It works like a CP instruction, but raises **SKIP** in the execution stage rather than updating the status register.

7.6.10.6 Interrupts

We have seen earlier, that the opcode fetch stage inserts "interrupt instructions" into the pipeline when an interrupt occurs. These interrupt instructions are similar to **CALL** instructions. In contrast to **CALL** instructions, however, we use **ALU_INTR** instead of **ALU_PC_2**. This copies the **PC** (rather than **PC + 2**) to the output of the ALU (due to the fact that we have overridden a valid instruction and want to continue with exactly that instruction after returning from the interrupt). Another thing that **ALU_INTR** does is to clear the **I** flag in the status register.

The interrupt opcodes are implemented as follows:

```

95          --
96          -- 0000 0000 0000 0000 - NOP
97          -- 0000 0000 001v vvvv - INTERRUPT
98          --
99          if (I_OPC(5)) = '1' then    -- interrupt
100             Q_ALU_OP      <= ALU_INTR;
101             Q_AMOD       <= AMOD_ddSP;
102             Q_JADR       <= "0000000000" & I_OPC(4 downto 0) & "0";
103             Q_PC_OP      <= PC_LD_I;
104             Q_WE_F       <= '1';
105             Q_WE_M       <= "11";
106         end if;

```

src/opc_deco.vhd

7.6.11 Instructions Not Implemented

A handful of instructions was not implemented. The reasons for not implementing them is one of the following:

1. The instruction is only available in particular devices, typically due to extended capabilities of these devices (**EICALL**, **EIJMP**, **ELPM**).
2. The instruction uses capabilities that are somewhat unusual in general (**BREAK**, **DES**, **SLEEP**, **WDR**).

These instructions are normally not generated by C/C++ compilers, but need to be generated by means of **#asm** directives. At this point the reader should have learned enough to implement these functions when needed.

7.7 Index of all Instructions

The following table lists all CPU instructions and a reference to the chapter where they are (supposed to be) described.

ADC	7.6.3 8-bit Dyadic Instructions, Register/Register
ADD	7.6.3 8-bit Dyadic Instructions, Register/Register

7 OPCODE DECODER

ADIW	7.6.5	16-bit Dyadic Instructions
AND	7.6.3	8-bit Dyadic Instructions, Register/Register
ANDI	7.6.4	8-bit Dyadic Instructions, Register/Immediate
ASR	7.6.2	8-bit Monadic Instructions
BCLR	7.6.2	8-bit Monadic Instructions
BLD	7.6.2	8-bit Monadic Instructions
BRcc	7.6.10	Jump and Call Instructions
BREAK	7.6.11	Instructions Not Implemented
BSET	7.6.2	8-bit Monadic Instructions
BST	7.6.2	8-bit Monadic Instructions
CALL	7.6.10	Jump and Call Instructions
CBI	7.6.6	Bit Instructions
CBR	-	see ANDI
CL<flag>	-	see BCLR
CLR	-	see LDI
COM	7.6.2	8-bit Monadic Instructions
CP	7.6.3	8-bit Dyadic Instructions, Register/Register
CPC	7.6.3	8-bit Dyadic Instructions, Register/Register
CPI	7.6.4	8-bit Dyadic Instructions, Register/Immediate
CPSE	7.6.10	Jump and Call Instructions
DEC	7.6.2	8-bit Monadic Instructions
DES	7.6.11	Instructions Not Implemented
EICALL	7.6.11	Instructions Not Implemented
EIJMP	7.6.11	Instructions Not Implemented
ELPM	7.6.11	Instructions Not Implemented
EOR	7.6.3	8-bit Dyadic Instructions, Register/Register
FMUL[SU]	7.6.7	Multiplication Instructions
ICALL	7.6.10	Jump and Call Instructions
IN	7.6.9	Instructions Reading From Memory or I/O
INC	7.6.2	8-bit Monadic Instructions
IJMP	7.6.10	Jump and Call Instructions
JMP	7.6.10	Jump and Call Instructions
LDD	7.6.9	Instructions Reading From Memory or I/O
LDI	7.6.5	16-bit Dyadic Instructions
LDS	7.6.9	Instructions Reading From Memory or I/O
LSL	7.6.2	8-bit Monadic Instructions
LSR	7.6.2	8-bit Monadic Instructions
MOV	7.6.3	8-bit Dyadic Instructions, Register/Register
MOVW	7.6.5	16-bit Dyadic Instructions
MUL[SU]	7.6.7	Multiplication Instructions
NEG	7.6.2	8-bit Monadic Instructions
NOP	7.6.1	The NOP instruction

7 OPCODE DECODER

NOT	7.6.2 8-bit Monadic Instructions
OR	7.6.3 8-bit Dyadic Instructions, Register/Register
ORI	7.6.4 8-bit Dyadic Instructions, Register/Immediate
OUT	7.6.8 Instructions Writing To Memory or I/O
POP	7.6.9 Instructions Reading From Memory or I/O
PUSH	7.6.8 Instructions Writing To Memory or I/O
RCALL	7.6.10 Jump and Call Instructions
RET	7.6.10 Jump and Call Instructions
RETI	7.6.10 Jump and Call Instructions
RJMP	7.6.10 Jump and Call Instructions
ROL	7.6.2 8-bit Monadic Instructions
SBC	7.6.3 8-bit Dyadic Instructions, Register/Register
SBCI	7.6.4 8-bit Dyadic Instructions, Register/Immediate
SBI	7.6.6 Bit Instructions
SBIC	7.6.10 Jump and Call Instructions
SBIS	7.6.10 Jump and Call Instructions
SBIW	7.6.5 16-bit Dyadic Instructions
SBR	- see ORI
SBRC	7.6.10 Jump and Call Instructions
SBRS	7.6.10 Jump and Call Instructions
SE<flag>	- see BSET
SER	- see LDI
SLEEP	7.6.11 Instructions Not Implemented
SPM	7.6.8 Instructions Writing To Memory or I/O
STD	7.6.8 Instructions Writing To Memory or I/O
STS	7.6.8 Instructions Writing To Memory or I/O
SUB	7.6.3 8-bit Dyadic Instructions, Register/Register
SUBI	7.6.4 8-bit Dyadic Instructions, Register/Immediate
SWAP	7.6.2 8-bit Monadic Instructions
WDR	7.6.11 Instructions Not Implemented

This concludes the discussion of the CPU. In the next lesson we will proceed with the input/output unit.

8 INPUT/OUTPUT

The last piece in the design is the input/output unit. Strictly speaking it does not belong to the CPU as such, but we discuss it briefly to see how it connects to the CPU.

8.1 Interface to the CPU

As we have already seen in the top level design, the I/O unit uses the same clock as the CPU (which greatly simplifies its design).

The interface towards the CPU consist of the following signals:

ADR_IO The number of an individual I/O register

DIN Data to an I/O register (I/O write)

RD_IO Read Strobe

WR_IO Write Strobe

DOUT Data from an I/O register (I/O read cycle).

These signals are well known from other I/O devices like UARTs, Ethernet Controllers, and the like.

The CPU supports two kinds of accesses to I/O registers: I/O reads (with the IN or LDS instructions, but also for the skip instructions SBIC and SBIS), and I/O writes (with the OUT or STS instructions, but also with the bit instructions CBI and SBI).

The skip instructions SBIC and SBIS execute in 2 cycles; in the first cycle an I/O read is performed while the skip (or not) decision is made in the second cycle. The reason for this is that the combinational delay for a single cycle would have been too long.

From the I/O unit's perspective, I/O reads and writes are performed in a single cycle (even if the CPU needs another cycle to complete an instruction).

The I/O unit generates an interrupt vector on its **INTVEC** output. The upper bit of the **INTVEC** output is set if an interrupt is pending.

8.2 CLR Signal

Some I/O components need a **CLR** signal to bring them into a defined state. The **CLR** signal of the CPU is used for this purpose.

8.3 Connection the FPGA Pins

The remaining signals into and out of the I/O unit are more or less directly connected to FPGA pins.

The **RX** input comes from an RS232 receiver/driver chip and is the serial input for an UART (active low). The **TX** output (also active low) is the serial output from that UART and goes back to the RS232 receiver/driver chip:

8 INPUT/OUTPUT

```
89          I_RX      => I_RX,  
90  
91          Q_TX      => Q_TX,
```

src/io.vhd

The **SWITCH** input comes from a DIP switch on the board. The values of the switch can be read from I/O register **PINB** (0x36).

```
132          when X"36"  => Q_DOUT      <= I_SWITCH; -- PINB
```

src/io.vhd

The **7 SEGMENT** output drives the 7 segments of a 7-segment display. This output can be set from software by writing to the **PORTB** (0x38) I/O register. The segments can also be driven by a debug function which shows the current **PC** and the current opcode of the CPU.

```
147          when X"38"  => Q_7_SEGMENT    <= I_DIN(6 downto 0); -- PORTB
```

src/io.vhd

The choice between the debug display and the software controlled display function is made by the DIP switch setting:

```
183          Q_7_SEGMENT    <= N_7_SEGMENT when (I_SWITCH(7) = '1') else S_7_SEGMENT;
```

src/avr_fpga.vhd

8.4 I/O Read

I/O read cycles are indicated by the **RD_IO** signal. If **RD_IO** is applied, then the address of the I/O register to be read is provided on the **ADR_IO** input and the value of that register is expected on **DOUT** at the next **CLK** edge.

This is accomplished by the I/O read process:

8 INPUT/OUTPUT

```
98      iord: process(I_ADDR_IO, I_SWITCH,
99                  U_RX_DATA, U_RX_READY, L_RX_INT_ENABLED,
100                 U_TX_BUSY, L_TX_INT_ENABLED)
101 begin
102     -- addresses for mega8 device (use iom8.h or #define __AVR_ATmega8__).
103     --
104     case I_ADDR_IO is
105         when X"2A" => Q_DOUT      <=          -- UCSRB:
106             L_RX_INT_ENABLED    -- Rx complete int enabled.
107             & L_TX_INT_ENABLED   -- Tx complete int enabled.
108             & L_TX_INT_ENABLED   -- Tx empty int enabled.
109             & '1'                -- Rx enabled
110             & '1'                -- Tx enabled
111             & '0'                -- 8 bits/char
112             & '0'                -- Rx bit 8
113             & '0';               -- Tx bit 8
114         when X"2B" => Q_DOUT      <=          -- UCSRA:
115             U_RX_READY        -- Rx complete
116             & not U_TX_BUSY    -- Tx complete
117             & not U_TX_BUSY    -- Tx ready
118             & '0'                -- frame error
119             & '0'                -- data overrun
120             & '0'                -- parity error
121             & '0'                -- double dpeed
122             & '0';               -- multiproc mode
123         when X"2C" => Q_DOUT      <= U_RX_DATA; -- UDR
124         when X"40" => Q_DOUT      <=          -- UCSRC
125             '1'                -- URSEL
126             & '0'                -- asynchronous
127             & "00"               -- no parity
128             & '1'                -- two stop bits
129             & "11"               -- 8 bits/char
130             & '0';               -- rising clock edge
131
132         when X"36" => Q_DOUT      <= I_SWITCH;  -- PINB
133         when others => Q_DOUT      <= X"AA";
134     end case;
135 end process;
```

src/io.vhd

I/O registers that are not implemented (i.e almost all) set **DOUT** to 0xAA as a debugging aid.

The outputs of sub-components (like the UART) are selected in the I/O read process.

8.5 I/O Write

I/O write cycles are indicated by the **WR_IO** signal. If **WR_IO** is applied, then the address of the I/O register to be written is provided on the **ADR_IO** input and the value to be written is supplied on the **DIN** input:

```
139      iowr: process(I_CLK)
140 begin
```

8 INPUT/OUTPUT

```
141      if (rising_edge(I_CLK)) then
142          if (I_CLR = '1') then
143              L_RX_INT_ENABLED      <= '0';
144              L_TX_INT_ENABLED      <= '0';
145          elsif (I_WE_IO = '1') then
146              case I_ADR_IO is
147                  when X"38" => Q_7_SEGMENT      <= I_DIN(6 downto 0);      -- PORTB
148                      L_LEDS            <= not L_LEDS;
149                  when X"40" => -- handled by uart
150                  when X"41" => -- handled by uart
151                  when X"43" => L_RX_INT_ENABLED      <= I_DIN(0);
152                      L_TX_INT_ENABLED      <= I_DIN(1);
153                  when others =>
154                      end case;
155          end if;
156      end if;
157  end process;
```

src/io.vhd

In the I/O read process the outputs of sub-component were multiplexed into the final output **DO_{UT}** and hence their register numbers (like 0x2C for the **UDR** read register) were visible, In the I/O write process, however, the inputs of sub-components (again like 0x2C for the **UDR** write register) are not visible in the write process and decoding of the **WR** (and **RD** where needed) strobes for sub components is done outside of these processes:

```
182      L_WE_UART      <= I_WE_IO when (I_ADR_IO = X"2C") else '0'; -- write UART UDR
183      L_RD_UART      <= I_RD_IO when (I_ADR_IO = X"2C") else '0'; -- read  UART UDR
184
```

src/io.vhd

8.6 Interrupts

Some I/O components raise interrupts, which are coordinated in the I/O interrupt process:

```
161      ioint: process(I_CLK)
162      begin
163          if (rising_edge(I_CLK)) then
164              if (I_CLR = '1') then
165                  L_INTVEC      <= "000000";
166              else
167                  if (L_RX_INT_ENABLED and U_RX_READY) = '1' then
168                      if (L_INTVEC(5) = '0') then      -- no interrupt pending
169                          L_INTVEC      <= "101011";      -- _VECTOR(11)
170                      end if;
171                  elsif (L_TX_INT_ENABLED and not U_TX_BUSY) = '1' then
```

8 INPUT/OUTPUT

```
172      if (L_INTVEC(5) = '0') then      -- no interrupt pending
173          L_INTVEC      <= "101100";      -- _VECTOR(12)
174      end if;
175      else                           -- no interrupt
176          L_INTVEC      <= "000000";
177      end if;
178      end if;
179  end if;
180 end process;
```

src/io.vhd

8.7 The UART

The UART is an important facility for debugging programs that are more complex than our **hello.c**. We use a fixed baud rate of 38400 Baud and a fixed data format of 8 data bits and 2 stop bits. Therefore the corresponding bits in the UART control registers of the original AVR CPU are not implemented. The fixed values are properly reported, however.

The UART consists of 3 independent sub-components: a baud rate generator, a receiver, and a transmitter.

8.7.1 The UART Baud Rate Generator

The baud rate generator is clocked with a frequency of **clock_freq** and is supposed to generate a x1 clock of **baud_rate** for the transmitter and a x16 clock of **16*baud_rate** for the receiver.

The x16 clock is generated like this:

```
54
55      baud16: process(I_CLK)
56  begin
57      if (rising_edge(I_CLK)) then
58          if (I_CLR = '1') then
59              L_COUNTER      <= X"00000000";
60          elsif (L_COUNTER >= LIMIT) then
61              L_COUNTER      <= L_COUNTER - LIMIT;
62          else
63              L_COUNTER      <= L_COUNTER + BAUD_16;
64          end if;
65      end if;
66  end process;
67
68      baud1: process(I_CLK)
```

src/baudgen.vhd

We have done a little trick here. Most baud rate generators divide the input clock by a fixed integer number (like the one shown below for the x1 clock). That is fine if the input clock is a multiple of the output clock.

8 INPUT/OUTPUT

More often than not is the CPU clock not a multiple of the baud rate. Therefore, if an integer divider is used (like in the original AVR CPU, where the integer divisor was written into the UBRR I/O register) then the error in the baud rate cumulates over all bits transmitted. This can cause transmission errors when many characters are sent back to back. An integer divider would have set **L_COUNTER** to 0 after reaching **LIMIT**, which would have caused an absolute error of **COUNTER - LIMIT**. What we do instead is to subtract **LIMIT**, which does not discard the error but makes the next cycle a little shorter instead.

Instead of using a fixed baud rate interval of N times the clock interval (as fixed integer dividers would), we have used a variable baud rate interval; the length of the interval varies slightly over time, but the total error remains bounded. The error does not cumulate as for fixed integer dividers.

If you want to make the baud rate programmable, then you can replace the generic **baud_rate** by a signal (and the trick would still work).

The x1 clock is generated by dividing the x16 clock by 16:

```
70      if (rising_edge(I_CLK)) then
71          if (I_CLR = '1') then
72              L_CNT_16      <= "0000";
73          elsif (L_CE_16 = '1') then
74              L_CNT_16      <= L_CNT_16 + "0001";
75          end if;
76      end if;
77  end process;
78
79  L_CE_16      <= '1' when (L_COUNTER >= LIMIT) else '0';
80  Q_CE_16      <= L_CE_16;
81  Q_CE_1       <= L_CE_16 when L_CNT_16 = "1111" else '0';
```

src/baudgen.vhd

8.7.2 The UART Transmitter

The UART transmitter is a shift register that is loaded with the character to be transmitted (prepended with a start bit):

```
67      elsif (L_FLAG /= I_FLAG) then           -- new byte
68          Q_TX      <= '0';                  -- start bit
69          L_BUF     <= I_DATA;                -- data bits
70          L_TODO    <= "1001";
71      end if;
```

src/uart_tx.vhd

8 INPUT/OUTPUT

The **TODO** signal holds the number of bits that remain to be shifted out. The transmitter is clocked with the x1 baud rate:

```
59      elsif (I_CE_1 = '1') then
60          if (L_TODO /= "0000") then           -- transmitting
61              Q_TX        <= L_BUF(0);          -- next bit
62              L_BUF        <= '1' & L_BUF(7 downto 1);
63              if (L_TODO = "0001") then
64                  L_FLAG      <= I_FLAG;
65              end if;
66              L_TODO      <= L_TODO - "0001";
67              elsif (L_FLAG /= I_FLAG) then       -- new byte
68                  Q_TX        <= '0';            -- start bit
69                  L_BUF        <= I_DATA;         -- data bits
70                  L_TODO      <= "1001";
71              end if;
72          end if;
```

src/uart_tx.vhd

8.7.3 The UART Receiver

The UART transmitter runs synchronously with the CPU clock; but the UART receiver does not. We therefore clock the receiver input twice in order to synchronize it with the CPU clock:

```
56      process(I_CLK)
57      begin
58          if (rising_edge(I_CLK)) then
59              if (I_CLR = '1') then
60                  L_SERIN     <= '1';
61                  L_SER_HOT   <= '1';
62              else
63                  L_SERIN     <= I_RX;
64                  L_SER_HOT   <= L_SERIN;
65              end if;
66          end if;
67      end process;
```

src/uart_rx.vhd

The key signal in the UART receiver is **POSITION** which is the current position within the received character in units of 1/16 bit time. When the receiver is idle and a start bit is received, then **POSITION** is reset to 1:

8 INPUT/OUTPUT

```
86      if (L_POSITION = X"00") then          -- uart idle
87          L_BUF      <= "1111111111";
88      if (L_SER_HOT = '0') then           -- start bit received
89          L_POSITION     <= X"01";
90      end if;
```

src/uart_rx.vhd

At every subsequent edge of the 16x baud rate, **POSITION** is incremented and the receiver input (**SER_HOT**) input is checked at the middle of each bit (i.e. when **POSITION[3:0]** = "0111"). If the start bit has disappeared at the middle of the bit, then this is considered noise on the line rather than a valid start bit:

```
93      if (L_POSITION(3 downto 0) = "0111") then      -- 1/2 bit
94          L_BUF      <= L_SER_HOT & L_BUF(9 downto 1);    -- sample data
95      --
96      -- validate start bit
97      --
98      if (START_BIT and L_SER_HOT = '1') then      -- 1/2 start bit
99          L_POSITION     <= X"00";
100     end if;
101
102     if (STOP_BIT) then                         -- 1/2 stop bit
103         Q_DATA      <= L_BUF(9 downto 2);
104     end if;
```

src/uart_rx.vhd

Reception of a byte already finishes at 3/4 of the stop bit. This is to allow for cumulated baud rate errors of 1/4 bit time (or about 2.5 % baud rate error for 10 bit (1 start, 8 data, and 1 stop bit) transmissions). The received data is stored in **DATA**:

```
105     elsif (STOP_POS) then                  -- 3/4 stop bit
106         L_FLAG      <= L_FLAG xor (L_BUF(9) and not L_BUF(0));
107         L_POSITION     <= X"00";
```

src/uart_rx.vhd

If a greater tolerance against baud rate errors is needed, then one can decrease **STOP_POS** a little, but generally it would be safer to use 2 stop bits on the sender side.

This finalizes the description of the FPGA. We will proceed with the design flow in the next lesson.


9 TOOLCHAIN SETUP

In this lesson we will learn how to set up a toolchain on a Linux box. We will not describe, however, how the tools are downloaded and installed. The installation of a tools is normally described in the documentation that comes with the tool.

Places from where tools can be downloaded were already presented in the first lecture.

The following figure gives an overview of the entire flow. We show source files in yellow, temporary files in white and tools in green.

9 TOOLCHAIN SETUP

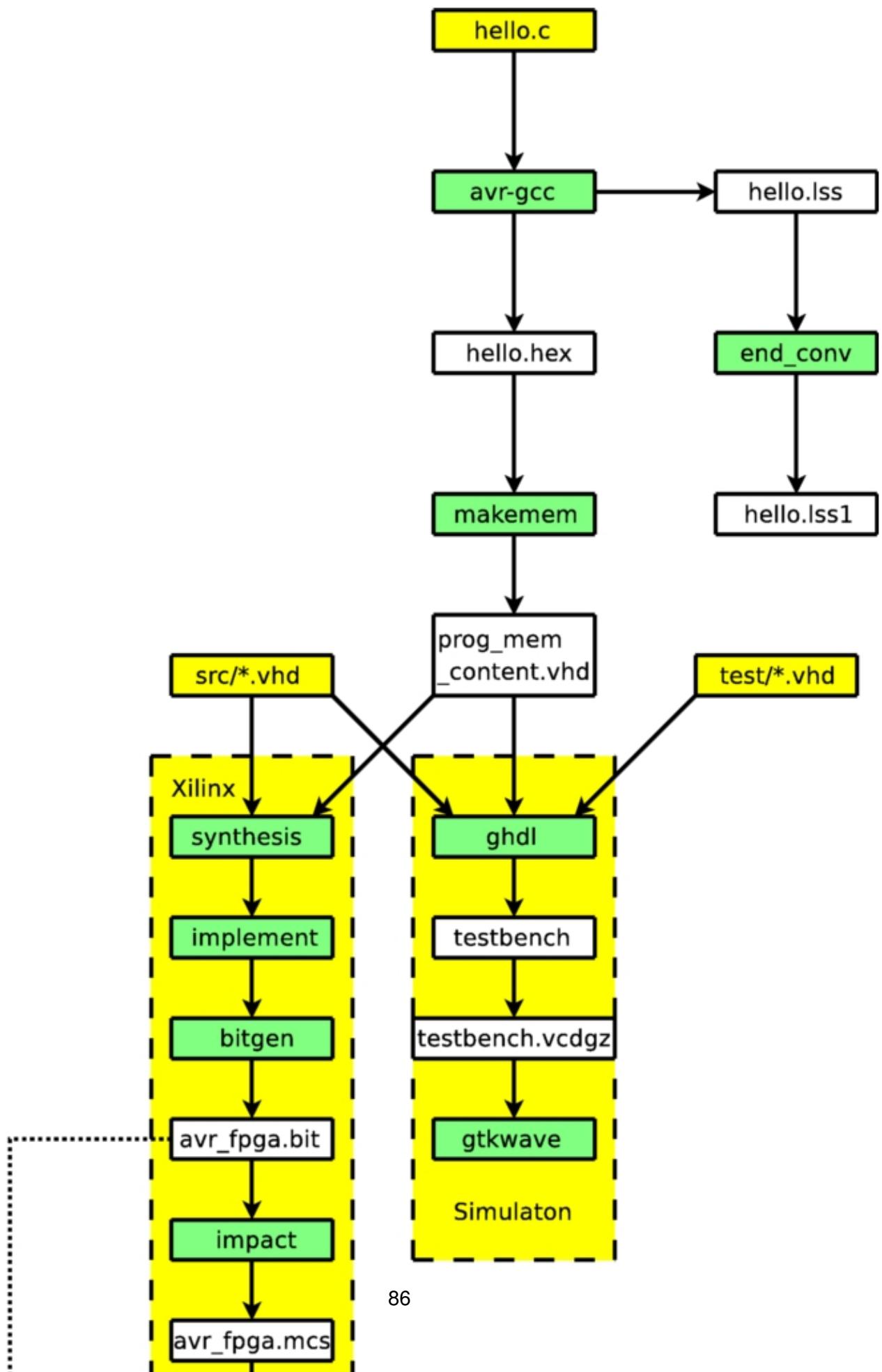

We start with a C source file **hello.c**. This file is compiled with **avr-gcc**, a **gcc** variant that generates opcodes for the AVR CPU. The compilation produces 2 output files: **hello.iss** and **hello.hex**.

hello.iss is a listing file and may optionally be post-processed by the tool **end_conv** which converts the little-endian format of **hello.iss** into a slightly different format that is more in line with the way **gtkwave** shows the hex values of signals.

The main purpose of the compilation is to produce **hello.hex**. **hello.hex** contains the opcodes produced from **hello.c** in Intel-Hex format.

hello.hex is then fed into **make_mem**. **make_mem** is a tool that converts the Intel-Hex format into VHDL constants. These constants are used to initialize the block RAM modules of the program memory. The output of **make_mem** is **memory_content.vhd** (which, as you certainly remember, was included by **prog_mem.vhd**).

At this point, there are two possible ways to proceed. You could do a functional simulation or a timing simulation.

8.1 Functional Simulation

Initially you will be concerned mostly with the functional simulation. On this branch you debug the VHDL code until it looks functionally OK. In order to perform the functional simulation, you need 3 sorts of VHDL files:


1. The VHDL source files that were discussed in the previous lessons,
2. the **memory_content.vhd** just described, and
3. a testbench that mimics the board containing the FPGA to be (**test_tb.vhd**, and a VHDL implementation of device specific components used (in our case this is only **RAMB4_S4_S4.vhd**). Both files are provided in the directory called **test**.

All these VHDL files are then processed by **ghdl**. **ghdl** produces a single output file **testbench** in directory **simu**. **testbench** is an executable file. **testbench** is then run in order to produce a gzip'ed **vcd** (value change dump) file called **testbench.vcdgz**.

The last step is visualize **testbench.vcdgz** by means of the tool **gtkwave**. **gtkwave** is similar to the **ModelSim** provided by Xilinx, but it has two advantages: it does not bother the user with licence installations (even in the "free" versions provided by Xilinx) and it runs under Linux. There are actually more advantages of the **ghdl/gtkwave** combination; after having used both tools in the past the author definitely prefers **ghdl/gtkwave**.

An example output of the functional simulation that shows the operation of our CPU:

9 TOOLCHAIN SETUP

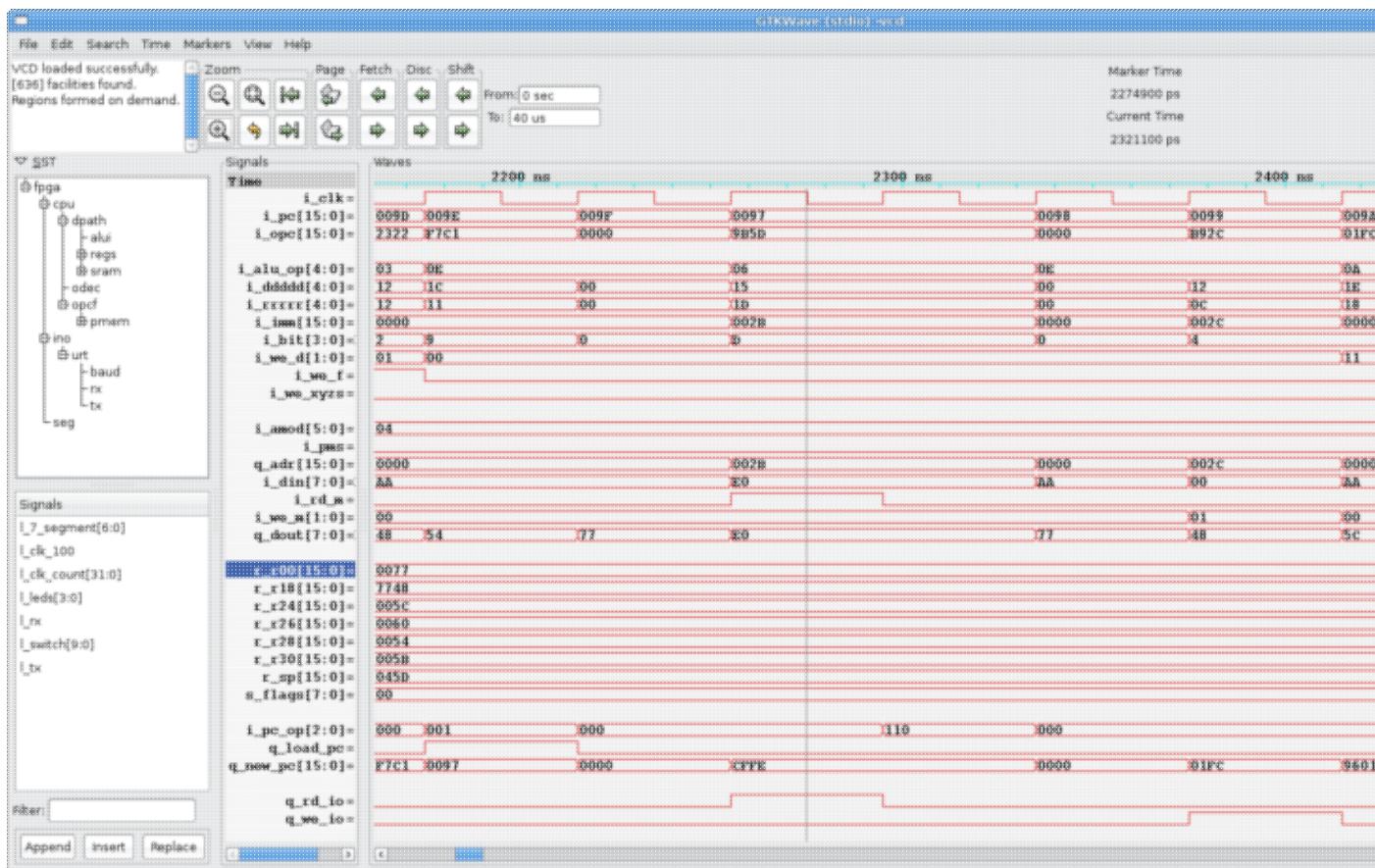

We can compare the CPU signals shown with the assembler code being executed. The CPU is executing inside the C function `uart_puts()`:

```

156      00000095: (uart_puts):
157      95: 01AC          movw    r20, r24
158      96: C003          rjmp   0x9A           ; 0x134
159      97: 9B5D          sbis   0x0b, 5 ; 11
160      98: CFFE          rjmp   0x97           ; 0x12e
161      99: B92C          out    0x0c, r18 ; 12
162     9A: 01FC          movw    r30, r24
163     9B: 9601          adiw   r24, 0x01 ; 1
164     9C: 9124          lpm    r18, z
165     9D: 2322          and    r18, r18
166     9E: F7C1          brne   0x97           ; 0x12e
167     9F: 1B84          sub    r24, r20
168     A0: 0B95          sbc    r25, r21
169     A1: 9701          sbiw   r24, 0x01 ; 1
170     A2: 9508          ret

```

app/hello.ls1

8.2 Timing Simulation and FPGA Configuration

After the CPU functions correctly, the design can be fed into the Xilinx toolchain. This toolchain is better described in the documentation that comes with it, so we don't go to too much detail here.

We used Webpack 10.1, which can be downloaded from Xilinx.

The first step is to set up a project in the ISE project navigator with the proper target device. Then the VHDL files in the `src` directory are added to the project. Next the **Synthesize** and **Implementation** steps of the design flow are run.

If this is successful, then we can generate a programming file. There are a number of ways to configure Xilinx FPGAs, and the type of programming file needed depends on the particular way of configuring the device. The board we used for testing the CPU had a serial PROM and therefore we generated a programming file for the serial PROM on the board. The FPGA would then load from the PROM on start-up. Other ways of configuring the device are via JTAG, which is also quite handy during debugging.

The entire build process is a little lengthy (and the devil is known to hide in the details). We therefore go through the entire design flow in a step-by-step fashion.

8.3 Downloading and Building the Tools

- Download and install **ghdl**.
- Download and install **gtkwave**.
- Download and install the Xilinx toolchain.

9 TOOLCHAIN SETUP

- Build the **make_mem** tool. The source is this:

```
1  #include "assert.h"
2  #include "stdio.h"
3  #include "stdint.h"
4  #include "string.h"
5
6  const char * hex_file = 0;
7  const char * vhdl_file = 0;
8
9  uint8_t buffer[0x10000];
10
11 //-----
12 uint32_t
13 get_byte(const char * cp)
14 {
15     uint32_t value;
16     const char cc[3] = { cp[0], cp[1], 0 };
17     const int cnt = sscanf(cc, "%X", &value);
18     assert(cnt == 1);
19     return value;
20 }
21
22 void
23 read_file(FILE * in)
24 {
25     memset(buffer, 0xFF, sizeof(buffer));
26     char line[200];
27     for (;;)
28     {
29         const char * s = fgets(line, sizeof(line) - 2, in);
30         if (s == 0)    return;
31         assert(*s++ == ':');
32         const uint32_t len      = get_byte(s);
33         const uint32_t ah       = get_byte(s + 2);
34         const uint32_t al       = get_byte(s + 4);
35         const uint32_t rectype = get_byte(s + 6);
36         const char * d = s + 8;
37         const uint32_t addr = ah      <<8 | al;
38
39         uint32_t csum = len + ah + al + rectype;
40         assert((addr + len)      <= 0x10000);
41         for (uint32_t l = 0; l      <len; ++l)
42         {
43             const uint32_t byte = get_byte(d);
44             d += 2;
45             buffer[addr + l] = byte;
46             csum += byte;
47         }
48
49         csum = 0xFF & -csum;
50         const uint32_t sum = get_byte(d);
51         assert(sum == csum);
52     }
53 }
54
55 void
56 write_vector(FILE * out, bool odd, uint32_t mem, uint32_t v)
```

9 TOOLCHAIN SETUP

```
57  {
58      const uint8_t * base = buffer;
59
60      // total memory is 2 even bytes, 2 odd bytes, 2 even bytes, ...
61      //
62      if (odd)    base += 2;
63
64      // total memory is 4 kByte organized into 8 memories.
65      // thus each of the 16 vectors covers 256 bytes.
66      //
67      base += v*256;
68
69      // memories 0 and 1 are the low byte of the opcode while
70      // memories 2 and 3 are the high byte.
71      //
72      if (mem >= 2)    ++base;
73
74      const char * px = odd ? "po" : "pe";
75      fprintf(out, "constant %s_%u_%.2X : BIT_VECTOR := X\"", px, mem, v);
76      for (int32_t d = 63; d >= 0; --d)
77      {
78          uint32_t q = base[4*d];
79          if (mem & 1)    q >>= 4;        // high nibble
80          else           q &= 0x0F;     // low nibble
81          fprintf(out, "%X", q);
82      }
83
84      fprintf(out, "\\\";\r\n");
85  }
86 //-----
87 void
88 write_mem(FILE * out, bool odd, uint32_t mem)
89 {
90     const char * px = odd ? "po" : "pe";
91
92     fprintf(out, "-- content of %s_%u -----"
93             "-----\r\n", px, mem);
94
95     for (uint32_t v = 0; v < 16; ++v)
96         write_vector(out, odd, mem, v);
97
98     fprintf(out, "\r\n");
99 }
100 //-----
101 void
102 write_file(FILE * out)
103 {
104     fprintf(out,
105     "\r\n"
106     "library IEEE;\r\n"
107     "use IEEE.STD_LOGIC_1164.all;\r\n"
108     "\r\n"
109     "package prog_mem_content is\r\n"
110     "\r\n");
111
112     for (uint32_t m = 0; m < 4; ++m)
113         write_mem(out, false, m);
114
115     for (uint32_t m = 0; m < 4; ++m)
116         write_mem(out, true, m);
117
118     fprintf(out,
```

9 TOOLCHAIN SETUP

```
119     "end prog_mem_content;\r\n"
120     "\r\n");
121 }
122 //-----
123 int
124 main(int argc, char * argv[])
125 {
126     if (argc > 1)    hex_file = argv[1];
127     if (argc > 2)    vhdl_file = argv[2];
128
129     FILE * in = stdin;
130     if (hex_file)   in = fopen(hex_file, "r");
131     assert(in);
132     read_file(in);
133     fclose(in);
134
135     FILE * out = stdout;
136     if (vhdl_file)  out = fopen(vhdl_file, "w");
137     write_file(out);
138     assert(out);
139 }
140 //-----
```

tools/make_mem.cc

The command to build the tool is:

```
# Build makemem.
g++ -o make_mem make_mem.cc
```

- Build the **end_conv** tool. The source is this:

```
1 #include "assert.h"
2 #include "ctype.h"
3 #include "stdio.h"
4 #include "string.h"
5
6 //-----
7 int
8 main(int argc, const char * argv)
9 {
10     char buffer[2000];
11     int pc, val, val2;
12
13     for (;;)
14     {
15         char * s = fgets(buffer, sizeof(buffer) - 2, stdin);
16         if (s == 0)    return 0;
```

9 TOOLCHAIN SETUP

```
17 // map lines ' xx:' and 'xxxxxxxx; to 2* the hex value.
18 // 
19 if (
20     (isxdigit(s[0]) || s[0] == ' ') &&
21     (isxdigit(s[1]) || s[1] == ' ') &&
22     (isxdigit(s[2]) || s[2] == ' ') &&
23     isxdigit(s[3]) && s[4] == ':')    // ' xx:'
24 {
25     assert(1 == sscanf(s, "%x:", &pc));
26     if (pc & 1)      printf("%4X+", pc/2);
27     else            printf("%4X:", pc/2);
28     s += 5;
29 }
30 else if (isxdigit(s[0]) && isxdigit(s[1]) && isxdigit(s[2]) &&
31     isxdigit(s[3]) && isxdigit(s[4]) && isxdigit(s[5]) &&
32     isxdigit(s[6]) && isxdigit(s[7]))           // 'xxxxxxxx'
33 {
34     assert(1 == sscanf(s, "%x", &pc));
35     if (pc & 1)  printf("%8.8X+", pc/2);
36     else          printf("%8.8X:", pc/2);
37     s += 8;
38 }
39 else                                // other: copy verbatim
40 {
41     printf("%s", s);
42     continue;
43 }
44
45 while (isblank(*s))    printf("%c", *s++);
46
47 // endian swap.
48 //
49 while (isxdigit(s[0]) &&
50     isxdigit(s[1]) &&
51         s[2] == ' ' &&
52         isxdigit(s[3]) &&
53         isxdigit(s[4]) &&
54             s[5] == ' ')
55 {
56     assert(2 == sscanf(s, "%x %x ", &val, &val2));
57     printf("%2.2X%2.2X ", val2, val);
58     s += 6;
59 }
60
61 char * s1 = strstr(s, ".+");
62 char * s2 = strstr(s, "-.");
63 if (s1)
64 {
65     assert(1 == sscanf(s1 + 2, "%d", &val));
66     assert((val & 1) == 0);
67     sprintf(s1, " 0x%X", (pc + val)/2 + 1);
68     printf(s);
69     s = s1 + strlen(s1) + 1;
70 }
71 else if (s2)
72 {
73     assert(1 == sscanf(s2 + 2, "%d", &val));
74     assert((val & 1) == 0);
75     sprintf(s2, " 0x%X", (pc - val)/2 + 1);
76     printf(s);
77     s = s2 + strlen(s2) + 1;
78 }
```

9 TOOLCHAIN SETUP

```
79         }
80         printf("%s", s);
81     }
82 }
83 //-----
84 tools/end_conv.cc
```

The command to build the tool is:

```
# Build end_conv.
g++ -o end_conv end_conv.cc
```

8.4 Preparing the Memory Content

We write a program **hello.c** that prints "Hello World" to the serial line.

The source is this:

```
1  #include "stdint.h"
2  #include "avr/io.h"
3  #include "avr/pgmspace.h"
4
5  #undef F_CPU
6  #define F_CPU 25000000UL
7  #include "util/delay.h"
8
9
10 //-----//
11 //-----//
12 //      print char cc on UART.          //
13 //      return number of chars printed (i.e. 1).  //
14 //-----//
15 //-----////
16 uint8_t
17 uart_putchar(uint8_t cc)
18 {
19     while ((UCSRA & (1      <<UDRE)) == 0)      ;
20     UDR = cc;
21     return 1;
22 }
23 //-----//
24 //-----//
25 //      print char cc on 7 segment display.      //
26 //-----//
```

9 TOOLCHAIN SETUP

```
27      //      return number of chars printed (i.e. 1).          //
28      //      //
29  //-----//  
30 // The segments of the display are encoded like this:  
31 //  
32 //  
33 //      segment      PORT B  
34 //      name        Bit number  
35 //      ----A----  ----0----  
36 //      |          |  |          |  
37 //      F          B  5          1  
38 //      |          |  |          |  
39 //      ----G----  ----6----  
40 //      |          |  |          |  
41 //      E          C  4          2  
42 //      |          |  |          |  
43 //      ----D----  ----3----  
44 //  
45 //-----//  
46  
47 #define SEG7(G, F, E, D, C, B, A)    (~G      <  
app/hello.c
```

The commands to create **hello.hex** and **hello.css** are:

```
# Compile and link hello.c.  
avr-gcc -Wall -Os -fpack-struct -fshort-enums -funsigned-char -funsigned-bitfields -mmcu=atmega8  
    -DF_CPU=3333333UL -MMD -MP -MF"main.d" -MT"main.d" -c -o"main.o" "main.c"  
avr-gcc -Wl,-Map,AVR_FPGA.map -mmcu=atmega8 -o"AVR_FPGA.elf" ./main.o  
  
# Create an opcode listing.  
avr-objdump -h -S AVR_FPGA.elf >"AVR_FPGA.lss"  
  
# Create intel hex file.  
avr-objcopy -R .eeprom -O ihex AVR_FPGA.elf "AVR_FPGA.hex"
```

Create **hello.css1**, a better readable from of **hello.css**:

```
# Create hello.css1.  
.end_conv <hello.css > hello.css1
```

Create **prog_mem_content.vhd**.

```
# Create prog_mem_content.vhd.
./make_mem <hello.hex > src/prog_mem_content.vhd
```

8.5 Performing the Functional Simulation

8.5.1 Preparing a Testbench

We prepare a testbench in which we instantiate the top-level FPGA design of the CPU. The test bench provides a clock signal and a reset signal for the CPU:

```

1  -----
2  --
3  -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann
4  --
5  -- This code is free software: you can redistribute it and/or modify
6  -- it under the terms of the GNU General Public License as published by
7  -- the Free Software Foundation, either version 3 of the License, or
8  -- (at your option) any later version.
9  --
10 -- This code is distributed in the hope that it will be useful,
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
13 -- GNU General Public License for more details.
14 --
15 -- You should have received a copy of the GNU General Public License
16 -- along with this code (see the file named COPYING).
17 -- If not, see http://www.gnu.org/licenses/.
18 --
19 -----
20 -----
21 --
22 -- Module Name:      alu - Behavioral
23 -- Create Date:     16:47:24 12/29/2009
24 -- Description:    arithmetic logic unit of a CPU
25 --
26 -----
27 --
28 library IEEE;
29 use IEEE.STD_LOGIC_1164.ALL;
30 use IEEE.STD_LOGIC_ARITH.ALL;
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;
32 --
33 entity testbench is
34 end testbench;
35 --
36 architecture Behavioral of testbench is
37 --
38 component avr_fpga
39     port ( I_CLK_100      : in  std_logic;
40             I_SWITCH      : in  std_logic_vector(9 downto 0);
41             I_RX          : in  std_logic;
```

9 TOOLCHAIN SETUP

```
43      Q_7_SEGMENT : out std_logic_vector(6 downto 0);
44      Q_LEDS      : out std_logic_vector(3 downto 0);
45      Q_TX        : out std_logic;
46  end component;
47
48  signal L_CLK_100          : std_logic;
49  signal L_LEDS            : std_logic_vector(3 downto 0);
50  signal L_7_SEGMENT       : std_logic_vector(6 downto 0);
51  signal L_RX              : std_logic;
52  signal L_SWITCH          : std_logic_vector(9 downto 0);
53  signal L_TX              : std_logic;
54
55  signal L_CLK_COUNT       : integer := 0;
56
57 begin
58
59     fpga: avr_fpga
60     port map(    I_CLK_100    => L_CLK_100,
61                I_SWITCH     => L_SWITCH,
62                I_RX         => L_RX,
63
64                Q_LEDS       => L_LEDS,
65                Q_7_SEGMENT  => L_7_SEGMENT,
66                Q_TX         => L_TX);
67
68 process -- clock process for CLK_100,
69 begin
70     clock_loop : loop
71         L_CLK_100      <= transport '0';
72         wait for 5 ns;
73
74         L_CLK_100      <= transport '1';
75         wait for 5 ns;
76     end loop clock_loop;
77 end process;
78
79 process(L_CLK_100)
80 begin
81     if (rising_edge(L_CLK_100)) then
82         case L_CLK_COUNT is
83             when 0 => L_SWITCH      <= "0011100000";  L_RX <= '0';
84             when 2 => L_SWITCH(9 downto 8)      <= "11";
85             when others =>
86                 end case;
87             L_CLK_COUNT      <= L_CLK_COUNT + 1;
88         end if;
89     end process;
90 end Behavioral;
```

test/test_tb.vhd

8.5.2 Defining Memory Modules

We also need a VHDL file that implements the Xilinx primitives that we use. This is only one: the memory module RAMB4_S4_S4:

9 TOOLCHAIN SETUP

```
1 -----
2 --
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann
4 --
5 -- This code is free software: you can redistribute it and/or modify
6 -- it under the terms of the GNU General Public License as published by
7 -- the Free Software Foundation, either version 3 of the License, or
8 -- (at your option) any later version.
9 --
10 -- This code is distributed in the hope that it will be useful,
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
13 -- GNU General Public License for more details.
14 --
15 -- You should have received a copy of the GNU General Public License
16 -- along with this code (see the file named COPYING).
17 -- If not, see http://www.gnu.org/licenses/.
18 --
19 -----
20 -----
21 --
22 -- Module Name:      prog_mem - Behavioral
23 -- Create Date:     14:09:04 10/30/2009
24 -- Description:    a block memory module
25 --
26 -----
27 
28 library IEEE;
29 use IEEE.STD_LOGIC_1164.ALL;
30 use IEEE.STD_LOGIC_ARITH.ALL;
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;
32 
33 entity RAMB4_S4_S4 is
34     generic(INIT_00 : bit_vector := X"00000000000000000000000000000000"
35                               & "00000000000000000000000000000000";
36         INIT_01 : bit_vector := X"00000000000000000000000000000000"
37                               & X"00000000000000000000000000000000";
38         INIT_02 : bit_vector := X"00000000000000000000000000000000"
39                               & X"00000000000000000000000000000000";
40         INIT_03 : bit_vector := X"00000000000000000000000000000000"
41                               & X"00000000000000000000000000000000";
42         INIT_04 : bit_vector := X"00000000000000000000000000000000"
43                               & X"00000000000000000000000000000000";
44         INIT_05 : bit_vector := X"00000000000000000000000000000000"
45                               & X"00000000000000000000000000000000";
46         INIT_06 : bit_vector := X"00000000000000000000000000000000"
47                               & X"00000000000000000000000000000000";
48         INIT_07 : bit_vector := X"00000000000000000000000000000000"
49                               & X"00000000000000000000000000000000";
50         INIT_08 : bit_vector := X"00000000000000000000000000000000"
51                               & X"00000000000000000000000000000000";
52         INIT_09 : bit_vector := X"00000000000000000000000000000000"
53                               & X"00000000000000000000000000000000";
54         INIT_0A : bit_vector := X"00000000000000000000000000000000"
55                               & X"00000000000000000000000000000000";
56         INIT_0B : bit_vector := X"00000000000000000000000000000000"
57                               & X"00000000000000000000000000000000";
58         INIT_0C : bit_vector := X"00000000000000000000000000000000"
59                               & X"00000000000000000000000000000000";
60         INIT_0D : bit_vector := X"00000000000000000000000000000000"
61                               & X"00000000000000000000000000000000";
```

9 TOOLCHAIN SETUP

```

62      INIT_0E : bit_vector := X"0000000000000000000000000000000000000000000000000000000000000000";
63      & X"0000000000000000000000000000000000000000000000000000000000000000";
64      INIT_0F : bit_vector := X"0000000000000000000000000000000000000000000000000000000000000000";
65      & X"0000000000000000000000000000000000000000000000000000000000000000");
66
67      port( ADDR_A : in std_logic_vector(9 downto 0);
68             ADDR_B : in std_logic_vector(9 downto 0);
69             CLK_A : in std_ulogic;
70             CLK_B : in std_ulogic;
71             DIA : in std_logic_vector(3 downto 0);
72             DIB : in std_logic_vector(3 downto 0);
73             ENA : in std_ulogic;
74             ENB : in std_ulogic;
75             RSTA : in std_ulogic;
76             RSTB : in std_ulogic;
77             WEA : in std_ulogic;
78             WEB : in std_ulogic;
79
80             DOA : out std_logic_vector(3 downto 0);
81             DOB : out std_logic_vector(3 downto 0));
82 end RAMB4_S4_S4;
83
84 architecture Behavioral of RAMB4_S4_S4 is
85
86     function cv(A : bit) return std_logic is
87 begin
88     if (A = '1') then return '1';
89     else               return '0';
90     end if;
91 end;
92
93     function cv1(A : std_logic) return bit is
94 begin
95     if (A = '1') then return '1';
96     else               return '0';
97     end if;
98 end;
99
100    signal DATA : bit_vector(4095 downto 0) :=
101        INIT_0F & INIT_0E & INIT_0D & INIT_0C & INIT_0B & INIT_0A & INIT_09 & INIT_08 &
102        INIT_07 & INIT_06 & INIT_05 & INIT_04 & INIT_03 & INIT_02 & INIT_01 & INIT_00;
103
104 begin
105
106     process(CLKA, CLK_B)
107 begin
108     if (rising_edge(CLKA)) then
109         if (ENA = '1') then
110             DOA(3)      <= cv(DATA(conv_integer(ADDR_A & "11")));
111             DOA(2)      <= cv(DATA(conv_integer(ADDR_A & "10")));
112             DOA(1)      <= cv(DATA(conv_integer(ADDR_A & "01")));
113             DOA(0)      <= cv(DATA(conv_integer(ADDR_A & "00")));
114
115         if (WEA = '1') then
116             DATA(conv_integer(ADDR_A & "11"))      <= cv1(DIA(3));
117             DATA(conv_integer(ADDR_A & "10"))      <= cv1(DIA(2));
118             DATA(conv_integer(ADDR_A & "01"))      <= cv1(DIA(1));
119             DATA(conv_integer(ADDR_A & "00"))      <= cv1(DIA(0));
120
121         end if;
122     end if;
123
124     if (rising_edge(CLKB)) then

```

9 TOOLCHAIN SETUP

```
124      if (ENB = '1') then
125          DOB(3)      <= cv(DATA(conv_integer(ADDRB & "11")));
126          DOB(2)      <= cv(DATA(conv_integer(ADDRB & "10")));
127          DOB(1)      <= cv(DATA(conv_integer(ADDRB & "01")));
128          DOB(0)      <= cv(DATA(conv_integer(ADDRB & "00")));
129      if (WEB = '1') then
130          DATA(conv_integer(ADDRB & "11"))      <= cv1(DIB(3));
131          DATA(conv_integer(ADDRB & "10"))      <= cv1(DIB(2));
132          DATA(conv_integer(ADDRB & "01"))      <= cv1(DIB(1));
133          DATA(conv_integer(ADDRB & "00"))      <= cv1(DIB(0));
134      end if;
135      end if;
136      end if;
137  end process;
138
139 end Behavioral;
140
```

test/RAMB4_S4_S4.vhd

8.5.3 Creating the testbench executable

We assume the following file structure:

- a **test** directory that contains the testbench (**test_tb.vhd**) and the memory module (**RAMB4_S4_S4.vhd**).
- a **src** directory that contains all other VHDL files.
- a **simu** directory (empty).
- A **Makefile** like this:

```
1 PROJECT=avr_core
2
3 # the vhdl source files (except testbench)
4 #
5 FILES      += src/*.vhd
6
7 # the testbench sources and binary.
8 #
9 SIMFILES    = test/test_tb.vhd
10 SIMFILES   += test/RAMB4_S4_S4.vhd
11 SIMFILES   += test/RAM32X1S.vhd
12 SIMTOP     = testbench
13
14 # When to stop the simulation
15 #
16 # GHDL_SIM_OPT  = --assert-level=error
17 GHDL_SIM_OPT = --stop-time=40us
18
19 SIMDIR     = simu
20
21 FLAGS       = --ieee=synopsys --warn-no-vital-generic -fexplicit --std=93c
22
23 all:
```

9 TOOLCHAIN SETUP

```
24          make compile
25          make run 2>& 1 | grep -v std_logic_arith
26          make view
27
28      compile:
29          @mkdir -p simu
30          @echo -----
31          ghdl -i $(FLAGS) --workdir=simu --work=work $(SIMFILES) $(FILES)
32          @echo -----
33          @echo -----
34          ghdl -m $(FLAGS) --workdir=simu --work=work $(SIMTOP)
35          @echo
36          @mv $(SIMTOP) simu/$(SIMTOP)
37
38      run:
39          @$(SIMDIR)/$(SIMTOP) $(GHDL_SIM_OPT) --vcdgz=$(SIMDIR)/$(SIMTOP).vcdgz
40
41      view:
42          gunzip --stdout $(SIMDIR)/$(SIMTOP).vcdgz | gtkwave --vcd gtkwave.save
43
44      clean:
45          ghdl --clean --workdir=simu
46
```

Makefile

Then

```
# Run the functional simulation.
make
```

It will take a moment, but then a **gtkwave** window like the one shown earlier in this lesson will appear. It may look a little different due to different default settings (like background color). In that window you can add new signals from the design that you would like to investigate, remove signals you are not interested in, and so on. At the first time, no signals will be shown; you can add some by selecting a component instance at the right, selecting a signal in that component, and then pushing the **append** button on the right.

The **make** command has actually made 3 things:

- make compile (compile the VHDL files)
- make run (run the simulation), and
- make view

The first two steps (which took most of the total time) need only be run after changes to the VHDL files.

8.6 Building the Design

When the functional simulation looks OK, it is time to implement the design and check the timing. We describe this only briefly, since the Xilinx documentation of the Xilinx toolchain is a much better source of information.

8.6.1 Creating an UCF file

Before implementing the design, we need an **UCF** file. That file describes timing requirements, pin properties (like pull-ups for our DIP switch), and pin-to-signal mappings:

```

1      NET      I_CLK_100          PERIOD = 10 ns;
2      NET      L_CLK            PERIOD = 45 ns;
3
4      NET      I_CLK_100          TNM_NET = I_CLK_100;
5      NET      L_CLK            TNM_NET = L_CLK;
6
7      NET      I_CLK_100          LOC = AA12;
8      NET      I_RX              LOC = M3;
9      NET      Q_TX              LOC = M4;
10
11     # 7 segment LED display
12     #
13    NET      Q_7_SEGMENT        LOC = V3;
14    NET      Q_7_SEGMENT        LOC = V4;
15    NET      Q_7_SEGMENT        LOC = W3;
16    NET      Q_7_SEGMENT        LOC = T4;
17    NET      Q_7_SEGMENT        LOC = T3;
18    NET      Q_7_SEGMENT        LOC = U3;
19    NET      Q_7_SEGMENT        LOC = U4;
20
21     # single LEDs
22     #
23    NET      Q_LEDS             LOC = N1;
24    NET      Q_LEDS             LOC = N2;
25    NET      Q_LEDS             LOC = P1;
26    NET      Q_LEDS             LOC = P2;
27
28     # DIP switch(0 ... 7) and two pushbuttons (8, 9)
29     #
30    NET      I_SWITCH           LOC = H2;
31    NET      I_SWITCH           LOC = H1;
32    NET      I_SWITCH           LOC = J2;
33    NET      I_SWITCH           LOC = J1;
34    NET      I_SWITCH           LOC = K2;
35    NET      I_SWITCH           LOC = K1;
36    NET      I_SWITCH           LOC = L2;
37    NET      I_SWITCH           LOC = L1;
38    NET      I_SWITCH           LOC = R1;
39    NET      I_SWITCH           LOC = R2;
40
41    NET      I_SWITCH           PULLUP;
42

```

src/avr_fpga.ucf

8.6.2 Synthesis and Implementation

- Start the ISE project manager and open a new project with the desired FPGA device.
- Add the VHDL files and the **UCF** file in the **src** directory to the project (Project->Add Source).
- Synthesize and implement the design (Process->Implement top Module).

This generates a number of reports, netlists, and other files. There should be no errors. There will be warnings though, including timing constraints that are not met.

It is important to understand the reason for each warning. Warnings often point to faults in the design.

The next thing to check is the timing reports. We were lucky:

```
#Timing report fragment:
=====
Timing constraint: NET "L_CLK" PERIOD = 35 ns HIGH 50%;
676756190 paths analyzed, 2342 endpoints analyzed, 0 failing endpoints
0 timing errors detected. (0 setup errors, 0 hold errors)
Minimum period is 34.981ns.
-----
=====
Timing constraint: NET "I_CLK_100_BUFGP/IBUFG" PERIOD = 10 ns HIGH 50%;
19 paths analyzed, 11 endpoints analyzed, 0 failing endpoints
0 timing errors detected. (0 setup errors, 0 hold errors)
Minimum period is 3.751ns.
```

All constraints were met.

This tells us that we have enough slack on the crystal CLK_100 signal (8.048ns would allow for up to 124 MHz). We had specified a period of 35 ns irequirement for the CPU clock:

```
2      NET      L_CLK          PERIOD = 45 ns;
src/avr_fpga.ucf
```

The CPU runs at 25 MHz, or 40 ns. The 35 ns come from the 40 ms minus a slack of 5 ns. With some tweaking of optimization options, we could have reached 33 MHz, but then the slack would have been pretty

small.

However, we rather stay on the safe side.

8.7 Creating a Programming File

Next we double-click "Generate Programming file" in the ISE project navigator. This generates a file **avr_fpga.bit** in the project directory. This can also be run from a Makefile or from the command line (the command is **bitgen**).

8.8 Configuring the FPGA

At this point, we have the choice between configuring the FPGA directly via JTAG, or flashing an EEPROM and then loading the FPGA from the EEPROM.

8.8.1 Configuring the FPGA via JTAG Boundary Scan

Configuring the FPGA can be done with the Xilinx tool called **impact**. The file needed by **impact** is **avr_fpga.bit** from above. The configuration loaded via JTAG will be lost when the FPGA loses power.

Choose "Boundary Scan" in **impact**, select the FPGA and follow the instructions.

8.8.2 Flashing PROMs

In theory this can also be done from ISE. In practice it could (and actually did) happen that the programming cable (I use an old parallel 3 cable) is not detected by impact.

Before flashing the PROM, the **avr_fpga.bit** from the previous step needs to be translated into a format suitable for the PROM. My PROM is of the serial variety, so I start **impact**, choose "PROM File Formatter" and follow the instructions.

After converting **avr_fpga.bit** into, for example, **avr_fpga.mcs**, the PROM can be flashed. Like before choose "Boundary Scan" in **#impact**. This time, however, you select the PROM and not the FPGA, and follow the instructions.

This concludes the description of the design flow and also of the CPU. The remaining lessons contain the complete listings of all sources files discussed in this lectures.

Thank you very much for your attention.

10 LISTING OF alu.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      alu - Behavioral  
23 -- Create Date:     13:51:24 11/07/2009  
24 -- Description:    arithmetic logic unit of a CPU  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.std_logic_1164.ALL;  
30 use IEEE.std_logic_ARITH.ALL;  
31 use IEEE.std_logic_UNSIGNED.ALL;  
32  
33 use work.common.ALL;  
34  
35 entity alu is  
36     port ( I_ALU_OP      : in  std_logic_vector( 4 downto 0);  
37             I_BIT        : in  std_logic_vector( 3 downto 0);  
38             I_D          : in  std_logic_vector(15 downto 0);  
39             I_D0         : in  std_logic;  
40             I_DIN        : in  std_logic_vector( 7 downto 0);  
41             I_FLAGS       : in  std_logic_vector( 7 downto 0);  
42             I_IMM         : in  std_logic_vector( 7 downto 0);  
43             I_PC          : in  std_logic_vector(15 downto 0);  
44             I_R           : in  std_logic_vector(15 downto 0);  
45             I_R0          : in  std_logic;  
46             I_RSEL        : in  std_logic_vector( 1 downto 0);  
47             Q_FLAGS       : out std_logic_vector( 9 downto 0);  
48             Q_DOUT        : out std_logic_vector(15 downto 0));  
49  
50 end alu;  
51  
52 architecture Behavioral of alu is  
53  
54 function ze(A: std_logic_vector(7 downto 0)) return std_logic is  
55 begin  
56     return not (A(0) or A(1) or A(2) or A(3) or  
57                  A(4) or A(5) or A(6) or A(7));  
58 end;
```

10 LISTING OF alu.vhd

```

59
60     function cy(D, R, S: std_logic) return std_logic is
61     begin
62         return (D and R) or (D and not S) or (R and not S);
63     end;
64
65     function ov(D, R, S: std_logic) return std_logic is
66     begin
67         return (D and R and (not S)) or ((not D) and (not R) and S);
68     end;
69
70     function si(D, R, S: std_logic) return std_logic is
71     begin
72         return S xor ov(D, R, S);
73     end;
74
75     signal L_ADC_DR      : std_logic_vector( 7 downto 0);      -- D + R + Carry
76     signal L_ADD_DR      : std_logic_vector( 7 downto 0);      -- D + R
77     signal LADIW_D       : std_logic_vector(15 downto 0);      -- D + IMM
78     signal L_AND_DR      : std_logic_vector( 7 downto 0);      -- D and R
79     signal L_ASRL_D      : std_logic_vector( 7 downto 0);      -- (signed D) >> 1
80     signal L_D8           : std_logic_vector( 7 downto 0);      -- D(7 downto 0)
81     signal L_DEC_D       : std_logic_vector( 7 downto 0);      -- D - 1
82     signal L_DOUT          : std_logic_vector(15 downto 0);      -- D + 1
83     signal L_INC_D       : std_logic_vector( 7 downto 0);      -- (unsigned) D >> 1
84     signal L_LSR_D       : std_logic_vector( 7 downto 0);      -- 1      <<IMM
85     signal L_MASK_I       : std_logic_vector( 7 downto 0);      -- 0 - D
86     signal L_NEG_D        : std_logic_vector( 7 downto 0);      -- 0 not D
87     signal L_NOT_D        : std_logic_vector( 7 downto 0);      -- D or R
88     signal L_OR_DR        : std_logic_vector( 7 downto 0);      -- D * R
89     signal L_PROD          : std_logic_vector(17 downto 0);      -- odd or even R
90     signal L_R8           : std_logic_vector( 7 downto 0);      -- R8 or IMM
91     signal L_RI8          : std_logic_vector( 7 downto 0);      -- R8 or IMM
92     signal L_RBIT          : std_logic;                          -- D - IMM
93     signal L_SBIW_D       : std_logic_vector(15 downto 0);      -- D rotated right
94     signal L_ROR_D        : std_logic_vector( 7 downto 0);      -- D - R - Carry
95     signal L_SBC_DR       : std_logic_vector( 7 downto 0);      -- D - R
96     signal L_SIGN_D       : std_logic;
97     signal L_SIGN_R       : std_logic;
98     signal L_SUB_DR       : std_logic_vector( 7 downto 0);      -- D - R
99     signal L_SWAP_D       : std_logic_vector( 7 downto 0);      -- D swapped
100    signal L_XOR_DR       : std_logic_vector( 7 downto 0);      -- D xor R
101
102    begin
103
104        dinbit: process(I_DIN, I_BIT(2 downto 0))
105        begin
106            case I_BIT(2 downto 0) is
107                when "000"  => L_RBIT      <= I_DIN(0);  L_MASK_I <= "00000001";
108                when "001"  => L_RBIT      <= I_DIN(1);  L_MASK_I <= "00000010";
109                when "010"  => L_RBIT      <= I_DIN(2);  L_MASK_I <= "00000100";
110                when "011"  => L_RBIT      <= I_DIN(3);  L_MASK_I <= "00001000";
111                when "100"  => L_RBIT      <= I_DIN(4);  L_MASK_I <= "00010000";
112                when "101"  => L_RBIT      <= I_DIN(5);  L_MASK_I <= "00100000";
113                when "110"  => L_RBIT      <= I_DIN(6);  L_MASK_I <= "01000000";
114                when others => L_RBIT      <= I_DIN(7);  L_MASK_I <= "10000000";
115            end case;
116        end process;
117
118        process(L_ADC_DR, L_ADD_DR, LADIW_D, I_ALU_OP, L_AND_DR, L_ASRL_D,
119                  I_BIT, I_D, L_D8, L_DEC_D, I_DIN, I_FLAGS, I_IMM, L_MASK_I,
120                  L_INC_D, L_LSR_D, L_NEG_D, L_NOT_D, L_OR_DR, I_PC, L_PROD,

```

10 LISTING OF alu.vhd

```

121          I_R, L_RI8, L_RBIT, L_ROR_D, L_SBIW_D, L_SUB_DR, L_SBC_DR,
122          L_SIGN_D, L_SIGN_R, L_SWAP_D, L_XOR_DR)
123      begin
124          Q_FLAGS(9)      <= L_RBIT xor not I_BIT(3);           -- DIN[BIT] = BIT[3]
125          Q_FLAGS(8)      <= ze(L_SUB_DR);                      -- D == R for CPSE
126          Q_FLAGS(7 downto 0)    <= I_FLAGS;
127          L_DOUT        <= X"0000";
128
129      case I_ALU_OP is
130          when ALU_ADC =>
131              L_DOUT      <= L_ADC_DR & L_ADC_DR;
132              Q_FLAGS(0)    <= cy(L_D8(7), L_RI8(7), L_ADC_DR(7));   -- Carry
133              Q_FLAGS(1)    <= ze(L_ADC_DR);                      -- Zero
134              Q_FLAGS(2)    <= L_ADC_DR(7);                      -- Negative
135              Q_FLAGS(3)    <= ov(L_D8(7), L_RI8(7), L_ADC_DR(7));   -- Overflow
136              Q_FLAGS(4)    <= si(L_D8(7), L_RI8(7), L_ADC_DR(7));   -- Signed
137              Q_FLAGS(5)    <= cy(L_D8(3), L_RI8(3), L_ADC_DR(3));   -- Halfcarry
138
139          when ALU_ADD =>
140              L_DOUT      <= L_ADD_DR & L_ADD_DR;
141              Q_FLAGS(0)    <= cy(L_D8(7), L_RI8(7), L_ADD_DR(7));   -- Carry
142              Q_FLAGS(1)    <= ze(L_ADD_DR);                      -- Zero
143              Q_FLAGS(2)    <= L_ADD_DR(7);                      -- Negative
144              Q_FLAGS(3)    <= ov(L_D8(7), L_RI8(7), L_ADD_DR(7));   -- Overflow
145              Q_FLAGS(4)    <= si(L_D8(7), L_RI8(7), L_ADD_DR(7));   -- Signed
146              Q_FLAGS(5)    <= cy(L_D8(3), L_RI8(3), L_ADD_DR(3));   -- Halfcarry
147
148          when ALUADIW =>
149              L_DOUT      <= L_ADIW_D;
150              Q_FLAGS(0)    <= L_ADIW_D(15) and not I_D(15);       -- Carry
151              Q_FLAGS(1)    <= ze(L_ADIW_D(15 downto 8)) and
152                  ze(L_ADIW_D(7 downto 0));                      -- Zero
153              Q_FLAGS(2)    <= L_ADIW_D(15);                      -- Negative
154              Q_FLAGS(3)    <= I_D(15) and not L_ADIW_D(15);       -- Overflow
155              Q_FLAGS(4)    <= (L_ADIW_D(15) and not I_D(15))
156                  xor (I_D(15) and not L_ADIW_D(15));       -- Signed
157
158          when ALU_AND =>
159              L_DOUT      <= L_AND_DR & L_AND_DR;
160              Q_FLAGS(1)    <= ze(L_AND_DR);                      -- Zero
161              Q_FLAGS(2)    <= L_AND_DR(7);                      -- Negative
162              Q_FLAGS(3)    <= '0';                           -- Overflow
163              Q_FLAGS(4)    <= L_AND_DR(7);                      -- Signed
164
165          when ALU_ASR =>
166              L_DOUT      <= L_ASR_D & L_ASR_D;
167              Q_FLAGS(0)    <= L_D8(0);                         -- Carry
168              Q_FLAGS(1)    <= ze(L_ASR_D);                      -- Zero
169              Q_FLAGS(2)    <= L_D8(7);                         -- Negative
170              Q_FLAGS(3)    <= L_D8(0) xor L_D8(7);           -- Overflow
171              Q_FLAGS(4)    <= L_D8(0);                         -- Signed
172
173          when ALU_BLD =>      -- copy T flag to DOUT
174              case I_BIT(2 downto 0) is
175                  when "000"  => L_DOUT( 0)      <= I_FLAGS(6);
176                                  L_DOUT( 8)      <= I_FLAGS(6);
177                  when "001"  => L_DOUT( 1)      <= I_FLAGS(6);
178                                  L_DOUT( 9)      <= I_FLAGS(6);
179                  when "010"  => L_DOUT( 2)      <= I_FLAGS(6);
180                                  L_DOUT(10)     <= I_FLAGS(6);
181                  when "011"  => L_DOUT( 3)      <= I_FLAGS(6);
182                                  L_DOUT(11)     <= I_FLAGS(6);

```

10 LISTING OF alu.vhd

```

183      when "100"  => L_DOUT( 4)      <= I_FLAGS(6);
184                  L_DOUT(12)      <= I_FLAGS(6);
185      when "101"  => L_DOUT( 5)      <= I_FLAGS(6);
186                  L_DOUT(13)      <= I_FLAGS(6);
187      when "110"  => L_DOUT( 6)      <= I_FLAGS(6);
188                  L_DOUT(14)      <= I_FLAGS(6);
189      when others => L_DOUT( 7)      <= I_FLAGS(6);
190                  L_DOUT(15)      <= I_FLAGS(6);
191      end case;
192
193      when ALU_BIT_CS => -- copy I_DIN to T flag
194          Q_FLAGS(6)      <= L_RBIT xor not I_BIT(3);
195          if (I_BIT(3) = '0') then      -- clear
196              L_DOUT(15 downto 8)      <= I_DIN and not L_MASK_I;
197              L_DOUT( 7 downto 0)      <= I_DIN and not L_MASK_I;
198          else                      -- set
199              L_DOUT(15 downto 8)      <= I_DIN or L_MASK_I;
200              L_DOUT( 7 downto 0)      <= I_DIN or L_MASK_I;
201          end if;
202
203      when ALU_COM =>
204          L_DOUT      <= L_NOT_D & L_NOT_D;
205          Q_FLAGS(0)      <= '1';           -- Carry
206          Q_FLAGS(1)      <= ze(not L_D8);   -- Zero
207          Q_FLAGS(2)      <= not L_D8(7);    -- Negative
208          Q_FLAGS(3)      <= '0';           -- Overflow
209          Q_FLAGS(4)      <= not L_D8(7);    -- Signed
210
211      when ALU_DEC =>
212          L_DOUT      <= L_DEC_D & L_DEC_D;
213          Q_FLAGS(1)      <= ze(L_DEC_D);   -- Zero
214          Q_FLAGS(2)      <= L_DEC_D(7);    -- Negative
215          if (L_D8 = X"80") then
216              Q_FLAGS(3)      <= '1';           -- Overflow
217              Q_FLAGS(4)      <= not L_DEC_D(7);  -- Signed
218          else
219              Q_FLAGS(3)      <= '0';           -- Overflow
220              Q_FLAGS(4)      <= L_DEC_D(7);    -- Signed
221          end if;
222
223      when ALU_EOR =>
224          L_DOUT      <= L_XOR_DR & L_XOR_DR;
225          Q_FLAGS(1)      <= ze(L_XOR_DR);  -- Zero
226          Q_FLAGS(2)      <= L_XOR_DR(7);   -- Negative
227          Q_FLAGS(3)      <= '0';           -- Overflow
228          Q_FLAGS(4)      <= L_XOR_DR(7);   -- Signed
229
230      when ALU_INC =>
231          L_DOUT      <= L_INC_D & L_INC_D;
232          Q_FLAGS(1)      <= ze(L_INC_D);   -- Zero
233          Q_FLAGS(2)      <= L_INC_D(7);   -- Negative
234          if (L_D8 = X"7F") then
235              Q_FLAGS(3)      <= '1';           -- Overflow
236              Q_FLAGS(4)      <= not L_INC_D(7);  -- Signed
237          else
238              Q_FLAGS(3)      <= '0';           -- Overflow
239              Q_FLAGS(4)      <= L_INC_D(7);   -- Signed
240          end if;
241
242      when ALU_INTR =>
243          L_DOUT      <= I_PC;
244          Q_FLAGS(7)      <= I_IMM(6);      -- ena/disable interrupts

```

10 LISTING OF alu.vhd

```

245
246      when ALU_LSR  =>
247          L_DOUT      <= L_LSR_D & L_LSR_D;
248          Q_FLAGS(0)    <= L_D8(0);
249          Q_FLAGS(1)    <= ze(L_LSR_D);
250          Q_FLAGS(2)    <= '0';
251          Q_FLAGS(3)    <= L_D8(0);
252          Q_FLAGS(4)    <= L_D8(0);
253
254      when ALU_D_MV_Q =>
255          L_DOUT      <= L_D8 & L_D8;
256
257      when ALU_R_MV_Q =>
258          L_DOUT      <= L_RI8 & L_RI8;
259
260      when ALU_MV_16 =>
261          L_DOUT      <= I_R(15 downto 8) & L_RI8;
262
263      when ALU_MULT =>
264          Q_FLAGS(0)      <= L_PROD(15);                                -- Carry
265          if I_IMM(7) = '0' then                                         -- MUL
266              L_DOUT      <= L_PROD(15 downto 0);
267              Q_FLAGS(1)      <= ze(L_PROD(15 downto 8))                -- Zero
268                  and ze(L_PROD( 7 downto 0));
269          else
270              L_DOUT      <= L_PROD(14 downto 0) & "0";                   -- FMUL
271              Q_FLAGS(1)      <= ze(L_PROD(14 downto 7))                -- Zero
272                  and ze(L_PROD( 6 downto 0) & "0");
273          end if;
274
275      when ALU_NEG =>
276          L_DOUT      <= L_NEG_D & L_NEG_D;
277          Q_FLAGS(0)      <= not ze(L_D8);                            -- Carry
278          Q_FLAGS(1)      <= ze(L_NEG_D);                            -- Zero
279          Q_FLAGS(2)      <= L_NEG_D(7);                            -- Negative
280          if (L_D8 = X"80") then
281              Q_FLAGS(3)      <= '1';                                -- Overflow
282              Q_FLAGS(4)      <= not L_NEG_D(7);                         -- Signed
283          else
284              Q_FLAGS(3)      <= '0';                                -- Overflow
285              Q_FLAGS(4)      <= L_NEG_D(7);                         -- Signed
286          end if;
287          Q_FLAGS(5)      <= L_D8(3) or L_NEG_D(3);                      -- Halfcarry
288
289      when ALU_OR =>
290          L_DOUT      <= L_OR_DR & L_OR_DR;
291          Q_FLAGS(1)      <= ze(L_OR_DR);                            -- Zero
292          Q_FLAGS(2)      <= L_OR_DR(7);                            -- Negative
293          Q_FLAGS(3)      <= '0';                                -- Overflow
294          Q_FLAGS(4)      <= L_OR_DR(7);                            -- Signed
295
296      when ALU_PC_1 =>      -- ICALL, RCALL
297          L_DOUT      <= I_PC + X"0001";
298
299      when ALU_PC_2 =>      -- CALL
300          L_DOUT      <= I_PC + X"0002";
301
302      when ALU_ROR =>
303          L_DOUT      <= L_ROR_D & L_ROR_D;
304          Q_FLAGS(1)      <= ze(L_ROR_D);                            -- Zero
305          Q_FLAGS(2)      <= I_FLAGS(0);                            -- Negative
306          Q_FLAGS(3)      <= I_FLAGS(0) xor L_D8(0);                      -- Overflow

```

10 LISTING OF alu.vhd

```

307          Q_FLAGS(4)      <= I_FLAGS(0);                                -- Signed
308
309      when ALU_SBC =>
310          L_DOUT      <= L_SBC_DR & L_SBC_DR;
311          Q_FLAGS(0)    <= cy(L_SBC_DR(7), L_RI8(7), L_D8(7));    -- Carry
312          Q_FLAGS(1)    <= ze(L_SBC_DR) and I_FLAGS(1);           -- Zero
313          Q_FLAGS(2)    <= L_SBC_DR(7);                           -- Negative
314          Q_FLAGS(3)    <= ov(L_SBC_DR(7), L_RI8(7), L_D8(7));    -- Overflow
315          Q_FLAGS(4)    <= si(L_SBC_DR(7), L_RI8(7), L_D8(7));    -- Signed
316          Q_FLAGS(5)    <= cy(L_SBC_DR(3), L_RI8(3), L_D8(3));    -- Halfcarry
317
318      when ALU_SBIW =>
319          L_DOUT      <= L_SBIW_D;
320          Q_FLAGS(0)    <= L_SBIW_D(15) and not I_D(15);           -- Carry
321          Q_FLAGS(1)    <= ze(L_SBIW_D(15 downto 8)) and
322              ze(L_SBIW_D(7 downto 0));                          -- Zero
323          Q_FLAGS(2)    <= L_SBIW_D(15);                           -- Negative
324          Q_FLAGS(3)    <= I_D(15) and not L_SBIW_D(15);           -- Overflow
325          Q_FLAGS(4)    <= (L_SBIW_D(15) and not I_D(15))
326              xor (I_D(15) and not L_SBIW_D(15));           -- Signed
327
328      when ALU_SREG =>
329          case I_BIT(2 downto 0) is
330              when "000"  => Q_FLAGS(0)      <= I_BIT(3);
331              when "001"  => Q_FLAGS(1)      <= I_BIT(3);
332              when "010"  => Q_FLAGS(2)      <= I_BIT(3);
333              when "011"  => Q_FLAGS(3)      <= I_BIT(3);
334              when "100"  => Q_FLAGS(4)      <= I_BIT(3);
335              when "101"  => Q_FLAGS(5)      <= I_BIT(3);
336              when "110"  => Q_FLAGS(6)      <= I_BIT(3);
337              when others => Q_FLAGS(7)      <= I_BIT(3);
338          end case;
339
340      when ALU_SUB =>
341          L_DOUT      <= L_SUB_DR & L_SUB_DR;
342          Q_FLAGS(0)    <= cy(L_SUB_DR(7), L_RI8(7), L_D8(7));    -- Carry
343          Q_FLAGS(1)    <= ze(L_SUB_DR);                         -- Zero
344          Q_FLAGS(2)    <= L_SUB_DR(7);                           -- Negative
345          Q_FLAGS(3)    <= ov(L_SUB_DR(7), L_RI8(7), L_D8(7));    -- Overflow
346          Q_FLAGS(4)    <= si(L_SUB_DR(7), L_RI8(7), L_D8(7));    -- Signed
347          Q_FLAGS(5)    <= cy(L_SUB_DR(3), L_RI8(3), L_D8(3));    -- Halfcarry
348
349      when ALU_SWAP =>
350          L_DOUT      <= L_SWAP_D & L_SWAP_D;
351
352          when others =>
353      end case;
354  end process;
355
356  L_D8      <= I_D(15 downto 8) when (I_D0 = '1') else I_D(7 downto 0);
357  L_R8      <= I_R(15 downto 8) when (I_R0 = '1') else I_R(7 downto 0);
358  L_RI8     <= I_IMM        when (I_RSEL = RS_IMM) else L_R8;
359
360  L_ADIW_D  <= I_D + ("0000000000" & I_IMM(5 downto 0));
361  L_SBIW_D  <= I_D - ("0000000000" & I_IMM(5 downto 0));
362  L_ADD_DR  <= L_D8 + L_RI8;
363  L_ADC_DR  <= L_ADD_DR + ("0000000" & I_FLAGS(0));
364  L_ASR_D   <= L_D8(7) & L_D8(7 downto 1);
365  L_AND_DR  <= L_D8 and L_RI8;
366  L_DEC_D   <= L_D8 - X"01";
367  L_INC_D   <= L_D8 + X"01";
368  L_LSR_D   <= '0' & L_D8(7 downto 1);

```

10 LISTING OF alu.vhd

```
369      L_NEG_D      <= X"00" - L_D8;
370      L_NOT_D      <= not L_D8;
371      L_OR_DR      <= L_D8 or L_RI8;
372      L_PROD        <= (L_SIGN_D & L_D8) * (L_SIGN_R & L_R8);
373      L_ROR_D       <= I_FLAGS(0) & L_D8(7 downto 1);
374      L_SUB_DR      <= L_D8 - L_RI8;
375      L_SBC_DR      <= L_SUB_DR - ("0000000" & I_FLAGS(0));
376      L_SIGN_D      <= L_D8(7) and I_IMM(6);
377      L_SIGN_R      <= L_R8(7) and I_IMM(5);
378      L_SWAP_D      <= L_D8(3 downto 0) & L_D8(7 downto 4);
379      L_XOR_DR      <= L_D8 xor L_R8;
380
381      Q_DOUT        <= (I_DIN & I_DIN) when (I_RSEL = RS_DIN) else L_DOUT;
382
383  end Behavioral;
384
```

src/alu.vhd

11 LISTING OF avr_fpga.vhd

```
1 -----
2 --
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann
4 --
5 -- This code is free software: you can redistribute it and/or modify
6 -- it under the terms of the GNU General Public License as published by
7 -- the Free Software Foundation, either version 3 of the License, or
8 -- (at your option) any later version.
9 --
10 -- This code is distributed in the hope that it will be useful,
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the
13 -- GNU General Public License for more details.
14 --
15 -- You should have received a copy of the GNU General Public License
16 -- along with this code (see the file named COPYING).
17 -- If not, see http://www.gnu.org/licenses/.
18 --
19 -----
20 -----
21 --
22 -- Module Name:      avr_fpga - Behavioral
23 -- Create Date:     13:51:24 11/07/2009
24 -- Description:    top level of a CPU
25 --
26 -----
27 
28 library IEEE;
29 use IEEE.STD_LOGIC_1164.ALL;
30 use IEEE.STD_LOGIC_ARITH.ALL;
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;
32 
33 entity avr_fpga is
34     port (  I_CLK_100      : in  std_logic;
35             I_SWITCH       : in  std_logic_vector(9 downto 0);
36             I_RX           : in  std_logic;
37 
38             Q_7_SEGMENT   : out std_logic_vector(6 downto 0);
39             Q_LEDs         : out std_logic_vector(3 downto 0);
40             Q_TX           : out std_logic);
41 end avr_fpga;
42 
43 architecture Behavioral of avr_fpga is
44 
45 component cpu_core
46     port (  I_CLK          : in  std_logic;
47             I_CLR          : in  std_logic;
48             I_INTVEC      : in  std_logic_vector( 5 downto 0);
49             I_DIN          : in  std_logic_vector( 7 downto 0);
50 
51             Q_OPC          : out std_logic_vector(15 downto 0);
52             Q_PC           : out std_logic_vector(15 downto 0);
53             Q_DOUT         : out std_logic_vector( 7 downto 0);
54             Q_ADR_IO       : out std_logic_vector( 7 downto 0);
55             Q_RD_IO        : out std_logic;
56             Q_WE_IO        : out std_logic);
57 end component;
58
```

11 LISTING OF avr_fpga.vhd

```

59      signal C_PC          : std_logic_vector(15 downto 0);
60      signal C_OPC         : std_logic_vector(15 downto 0);
61      signal C_ADR_IO      : std_logic_vector( 7 downto 0);
62      signal C_DOUT        : std_logic_vector( 7 downto 0);
63      signal C_RD_IO       : std_logic;
64      signal C_WE_IO       : std_logic;
65
66      component io
67          port ( I_CLK       : in  std_logic;
68                  I_CLR       : in  std_logic;
69                  I_ADR_IO    : in  std_logic_vector( 7 downto 0);
70                  I_DIN       : in  std_logic_vector( 7 downto 0);
71                  I_RD_IO     : in  std_logic;
72                  I_WE_IO     : in  std_logic;
73                  I_SWITCH   : in  std_logic_vector( 7 downto 0);
74                  I_RX        : in  std_logic;
75
76                  Q_7_SEGMENT : out std_logic_vector( 6 downto 0);
77                  Q_DOUT      : out std_logic_vector( 7 downto 0);
78                  Q_INTVEC   : out std_logic_vector(5 downto 0);
79                  Q_LEDS      : out std_logic_vector( 1 downto 0);
80                  Q_TX        : out std_logic);
81      end component;
82
83      signal N_INTVEC      : std_logic_vector( 5 downto 0);
84      signal N_DOUT        : std_logic_vector( 7 downto 0);
85      signal N_TX          : std_logic;
86      signal N_7_SEGMENT   : std_logic_vector( 6 downto 0);
87
88      component segment7
89          port ( I_CLK       : in  std_logic;
90
91                  I_CLR       : in  std_logic;
92                  I_OPC       : in  std_logic_vector(15 downto 0);
93                  I_PC        : in  std_logic_vector(15 downto 0);
94
95                  Q_7_SEGMENT : out std_logic_vector( 6 downto 0));
96      end component;
97
98      signal S_7_SEGMENT   : std_logic_vector( 6 downto 0);
99
100     signal L_CLK          : std_logic := '0';
101     signal L_CLK_CNT     : std_logic_vector( 2 downto 0) := "000";
102     signal L_CLR          : std_logic;           -- reset, active low
103     signal L_CLR_N        : std_logic := '0';      -- reset, active low
104     signal L_C1_N         : std_logic := '0';      -- switch debounce, active low
105     signal L_C2_N         : std_logic := '0';      -- switch debounce, active low
106
107     begin
108
109         cpu : cpu_core
110         port map( I_CLK       => L_CLK,
111                     I_CLR       => L_CLR,
112                     I_DIN       => N_DOUT,
113                     I_INTVEC   => N_INTVEC,
114
115                     Q_ADR_IO    => C_ADR_IO,
116                     Q_DOUT      => C_DOUT,
117                     Q_OPC       => C_OPC,
118                     Q_PC        => C_PC,
119                     Q_RD_IO     => C_RD_IO,
120                     Q_WE_IO     => C_WE_IO);

```

11 LISTING OF avr_fpga.vhd

```

121
122     ino : io
123     port map(  I_CLK      => L_CLK,
124                  I_CLR      => L_CLR,
125                  I_ADDR_IO  => C_ADDR_IO,
126                  I_DIN      => C_DOUT,
127                  I_RD_IO    => C_RD_IO,
128                  I_RX       => I_RX,
129                  I_SWITCH   => I_SWITCH(7 downto 0),
130                  I_WE_IO    => C_WE_IO,
131
132                  Q_7_SEGMENT => N_7_SEGMENT,
133                  Q_DOUT     => N_DOUT,
134                  Q_INTVEC   => N_INTVEC,
135                  Q_LEDS     => Q_LEDS(1 downto 0),
136                  Q_TX       => N_TX);
137
138     seg : segment7
139     port map(  I_CLK      => L_CLK,
140                  I_CLR      => L_CLR,
141                  I_OPC      => C_OPC,
142                  I_PC       => C_PC,
143
144                  Q_7_SEGMENT => S_7_SEGMENT);
145
146 -- input clock scaler
147 --
148 clk_div : process(I_CLK_100)
149 begin
150     if (rising_edge(I_CLK_100)) then
151         L_CLK_CNT    <= L_CLK_CNT + "001";
152         if (L_CLK_CNT = "001") then
153             L_CLK        <= '1';
154         elsif (L_CLK_CNT = "100") then
155             L_CLK        <= '0';
156             L_CLK_CNT    <= "000";
157         end if;
158     end if;
159 end process;
160
161 -- reset button debounce process
162 --
163 deb : process(L_CLK)
164 begin
165     if (rising_edge(L_CLK)) then
166         -- switch debounce
167         if ((I_SWITCH(8) = '0') or (I_SWITCH(9) = '0')) then      -- pushed
168             L_CLR_N      <= '0';
169             L_C2_N       <= '0';
170             L_C1_N       <= '0';
171         else                                     -- released
172             L_CLR_N      <= L_C2_N;
173             L_C2_N       <= L_C1_N;
174             L_C1_N       <= '1';
175         end if;
176     end if;
177 end process;
178
179     L_CLR      <= not L_CLR_N;
180
181     Q_LEDS(2)      <= I_RX;
182     Q_LEDS(3)      <= N_TX;

```

11 LISTING OF avr_fpga.vhd

```
183      Q_7_SEGMENT      <= N_7_SEGMENT when (I_SWITCH(7) = '1') else S_7_SEGMENT;
184      Q_TX        <= N_TX;
185
186  end Behavioral;
187
```

src/avr_fpga.vhd

12 LISTING OF baudgen.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      baudgen - Behavioral  
23 -- Create Date:     13:51:24 11/07/2009  
24 -- Description:    fixed baud rate generator  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity baudgen is  
34     generic(clock_freq : std_logic_vector(31 downto 0);  
35                 baud_rate  : std_logic_vector(27 downto 0));  
36     port(  I_CLK       : in  std_logic;  
37             I_CLR       : in  std_logic;  
38             Q_CE_1      : out std_logic;      -- baud x 1 clock enable  
39             Q_CE_16     : out std_logic);      -- baud x 16 clock enable  
40 end baudgen;  
41  
42  
43 architecture Behavioral of baudgen is  
44  
45 constant BAUD_16          : std_logic_vector(31 downto 0) := baud_rate & "0000";  
46 constant LIMIT            : std_logic_vector(31 downto 0) := clock_freq - BAUD_16;  
47  
48 signal L_CE_16           : std_logic;  
49 signal L_CNT_16          : std_logic_vector( 3 downto 0);  
50 signal L_COUNTER         : std_logic_vector(31 downto 0);  
51  
52 begin  
53  
54     baud16: process(I_CLK)  
55     begin  
56         if (rising_edge(I_CLK)) then  
57             if (I_CLR = '1') then
```

12 LISTING OF baudgen.vhd

```
59      L_COUNTER      <= X"00000000";
60      elsif (L_COUNTER >= LIMIT) then
61          L_COUNTER      <= L_COUNTER - LIMIT;
62      else
63          L_COUNTER      <= L_COUNTER + BAUD_16;
64      end if;
65      end if;
66  end process;
67
68  baud1: process(I_CLK)
69 begin
70      if (rising_edge(I_CLK)) then
71          if (I_CLR = '1') then
72              L_CNT_16      <= "0000";
73          elsif (L_CE_16 = '1') then
74              L_CNT_16      <= L_CNT_16 + "0001";
75          end if;
76      end if;
77  end process;
78
79      L_CE_16      <= '1' when (L_COUNTER >= LIMIT) else '0';
80      Q_CE_16      <= L_CE_16;
81      Q_CE_1       <= L_CE_16 when L_CNT_16 = "1111" else '0';
82
83  end behavioral;
84
```

src/baudgen.vhd

13 LISTING OF common.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name: common  
23 -- Create Date: 13:51:24 11/07/2009  
24 -- Description: constants shared by different modules.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.all;  
30  
31 package common is  
32  
33 -----  
34  
35 -- ALU operations  
36 --  
37 constant ALU_ADC : std_logic_vector(4 downto 0) := "00000";  
38 constant ALU_ADD : std_logic_vector(4 downto 0) := "00001";  
39 constant ALUADIW : std_logic_vector(4 downto 0) := "00010";  
40 constant ALU_AND : std_logic_vector(4 downto 0) := "00011";  
41 constant ALU_ASR : std_logic_vector(4 downto 0) := "00100";  
42 constant ALU_BLD : std_logic_vector(4 downto 0) := "00101";  
43 constant ALU_BIT_CS : std_logic_vector(4 downto 0) := "00110";  
44 constant ALU_COM : std_logic_vector(4 downto 0) := "00111";  
45 constant ALU_DEC : std_logic_vector(4 downto 0) := "01000";  
46 constant ALU_EOR : std_logic_vector(4 downto 0) := "01001";  
47 constant ALU_MV_16 : std_logic_vector(4 downto 0) := "01010";  
48 constant ALU_INC : std_logic_vector(4 downto 0) := "01011";  
49 constant ALU_INTR : std_logic_vector(4 downto 0) := "01100";  
50 constant ALU_LSR : std_logic_vector(4 downto 0) := "01101";  
51 constant ALU_D_MV_Q : std_logic_vector(4 downto 0) := "01110";  
52 constant ALU_R_MV_Q : std_logic_vector(4 downto 0) := "01111";  
53 constant ALU_MULT : std_logic_vector(4 downto 0) := "10000";  
54 constant ALU_NEG : std_logic_vector(4 downto 0) := "10001";  
55 constant ALU_OR : std_logic_vector(4 downto 0) := "10010";  
56 constant ALU_PC_1 : std_logic_vector(4 downto 0) := "10011";  
57 constant ALU_PC_2 : std_logic_vector(4 downto 0) := "10100";  
58 constant ALU_ROR : std_logic_vector(4 downto 0) := "10101";
```

13 LISTING OF common.vhd

```

59      constant ALU_SBC      : std_logic_vector(4 downto 0) := "10110";
60      constant ALU_SBIW     : std_logic_vector(4 downto 0) := "10111";
61      constant ALU_SREG      : std_logic_vector(4 downto 0) := "11000";
62      constant ALU_SUB       : std_logic_vector(4 downto 0) := "11001";
63      constant ALU_SWAP      : std_logic_vector(4 downto 0) := "11010";
64
65 -----
66 --
67 -- PC manipulations
68 --
69      constant PC_NEXT      : std_logic_vector(2 downto 0) := "000";      -- PC += 1
70      constant PC_BCC        : std_logic_vector(2 downto 0) := "001";      -- PC ?= IMM
71      constant PC_LD_I       : std_logic_vector(2 downto 0) := "010";      -- PC = IMM
72      constant PC_LD_Z       : std_logic_vector(2 downto 0) := "011";      -- PC = Z
73      constant PC_LD_S       : std_logic_vector(2 downto 0) := "100";      -- PC = (SP)
74      constant PC_SKIP_Z     : std_logic_vector(2 downto 0) := "101";      -- SKIP if Z
75      constant PC_SKIP_T     : std_logic_vector(2 downto 0) := "110";      -- SKIP if T
76
77 -----
78 --
79 -- Addressing modes. An address mode consists of two sub-fields,
80 -- which are the source of the address and an offset from the source.
81 -- Bit 3 indicates if the address will be modified.
82
83 -- address source
84      constant AS_SP         : std_logic_vector(2 downto 0) := "000";      -- SP
85      constant AS_Z          : std_logic_vector(2 downto 0) := "001";      -- Z
86      constant AS_Y          : std_logic_vector(2 downto 0) := "010";      -- Y
87      constant AS_X          : std_logic_vector(2 downto 0) := "011";      -- X
88      constant AS_IMM        : std_logic_vector(2 downto 0) := "100";      -- IMM
89
90 -- address offset
91      constant AO_0          : std_logic_vector(5 downto 3) := "000";      -- as is
92      constant AO_Q          : std_logic_vector(5 downto 3) := "010";      -- +q
93      constant AO_i          : std_logic_vector(5 downto 3) := "001";      -- +1
94      constant AO_ii         : std_logic_vector(5 downto 3) := "011";      -- +2
95      constant AO_d          : std_logic_vector(5 downto 3) := "101";      -- -1
96      constant AO_dd         : std_logic_vector(5 downto 3) := "111";      -- -2
97      --
98      --+
99 -- address updated ?
100      -- v
101      constant AM_WX         : std_logic_vector(3 downto 0) := '1' & AS_X;  -- X ++ or --
102      constant AM_WY         : std_logic_vector(3 downto 0) := '1' & AS_Y;  -- Y ++ or --
103      constant AM_WZ         : std_logic_vector(3 downto 0) := '1' & AS_Z;  -- Z ++ or --
104      constant AM_WS         : std_logic_vector(3 downto 0) := '1' & AS_SP; -- SP ++/--
105
106 -- address modes used
107 --
108      constant AMOD_ABS       : std_logic_vector(5 downto 0) := AO_0 & AS_IMM; -- IMM
109      constant AMOD_X         : std_logic_vector(5 downto 0) := AO_0 & AS_X;   -- (X)
110      constant AMOD_Xq        : std_logic_vector(5 downto 0) := AO_Q & AS_X;   -- (X+q)
111      constant AMOD_Xi        : std_logic_vector(5 downto 0) := AO_i & AS_X;   -- (X++)
112      constant AMOD_dX        : std_logic_vector(5 downto 0) := AO_d & AS_X;   -- (--X)
113      constant AMOD_Y         : std_logic_vector(5 downto 0) := AO_0 & AS_Y;   -- (Y)
114      constant AMOD_Yq        : std_logic_vector(5 downto 0) := AO_Q & AS_Y;   -- (Y+q)
115      constant AMOD_Yi        : std_logic_vector(5 downto 0) := AO_i & AS_Y;   -- (Y++)
116      constant AMOD_dY        : std_logic_vector(5 downto 0) := AO_d & AS_Y;   -- (--Y)
117      constant AMOD_Z         : std_logic_vector(5 downto 0) := AO_0 & AS_Z;   -- (Z)
118      constant AMOD_Zq        : std_logic_vector(5 downto 0) := AO_Q & AS_Z;   -- (Z+q)
119      constant AMOD_Zi        : std_logic_vector(5 downto 0) := AO_i & AS_Z;   -- (Z++)
120      constant AMOD_dZ        : std_logic_vector(5 downto 0) := AO_d & AS_Z;   -- (--Z)

```

13 LISTING OF common.vhd

```
121      constant AMOD_SPi : std_logic_vector(5 downto 0) := AO_i & AS_SP; -- (SP++)
122      constant AMOD_SPi: std_logic_vector(5 downto 0) := AO_ii & AS_SP; -- (SP++)
123      constant AMOD_dSP : std_logic_vector(5 downto 0) := AO_d & AS_SP; -- (--SP)
124      constant AMOD_ddSP: std_logic_vector(5 downto 0) := AO_dd & AS_SP; -- (--SP)
125
126 -----
127
128      -- Stack pointer manipulations.
129      --
130      constant SP_NOP : std_logic_vector(2 downto 0) := "000";
131      constant SP_ADD1: std_logic_vector(2 downto 0) := "001";
132      constant SP_ADD2: std_logic_vector(2 downto 0) := "010";
133      constant SP_SUB1: std_logic_vector(2 downto 0) := "011";
134      constant SP_SUB2: std_logic_vector(2 downto 0) := "100";
135
136 -----
137      --
138      -- ALU multiplexers.
139      --
140      constant RS_REG : std_logic_vector(1 downto 0) := "00";
141      constant RS_IMM : std_logic_vector(1 downto 0) := "01";
142      constant RS_DIN : std_logic_vector(1 downto 0) := "10";
143
144 -----
145      --
146      -- Multiplier variants. F means FMULT (as opposed to MULT).
147      -- S and U means signed vs. unsigned operands.
148      --
149      constant MULT_UU : std_logic_vector(2 downto 0) := "000";
150      constant MULT_SU : std_logic_vector(2 downto 0) := "010";
151      constant MULT_SS : std_logic_vector(2 downto 0) := "011";
152      constant MULT_FUU: std_logic_vector(2 downto 0) := "100";
153      constant MULT_FSU : std_logic_vector(2 downto 0) := "110";
154      constant MULT_FSS : std_logic_vector(2 downto 0) := "111";
155
156 -----
157
158      end common;
159
```

src/common.vhd

14 LISTING OF cpu_core.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      cpu_core - Behavioral  
23 -- Create Date:     13:51:24 11/07/2009  
24 -- Description:    the instruction set implementation of a CPU.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity cpu_core is  
34     port (  I_CLK          : in  std_logic;  
35             I_CLR          : in  std_logic;  
36             I_INTVEC       : in  std_logic_vector( 5 downto 0);  
37             I_DIN          : in  std_logic_vector( 7 downto 0);  
38  
39             Q_OPC          : out std_logic_vector(15 downto 0);  
40             Q_PC           : out std_logic_vector(15 downto 0);  
41             Q_DOUT         : out std_logic_vector( 7 downto 0);  
42             Q_ADR_IO        : out std_logic_vector( 7 downto 0);  
43             Q_RD_IO         : out std_logic;  
44             Q_WE_IO         : out std_logic);  
45 end cpu_core;  
46  
47 architecture Behavioral of cpu_core is  
48  
49 component opc_fetch  
50     port(  I_CLK          : in  std_logic;  
51  
52             I_CLR          : in  std_logic;  
53             I_INTVEC       : in  std_logic_vector( 5 downto 0);  
54             I_NEW_PC        : in  std_logic_vector(15 downto 0);  
55             I_LOAD_PC       : in  std_logic;  
56             I_PM_ADR        : in  std_logic_vector(11 downto 0);  
57             I_SKIP          : in  std_logic;  
58
```

14 LISTING OF cpu_core.vhd

```

59      Q_OPC      : out std_logic_vector(31 downto 0);
60      Q_PC       : out std_logic_vector(15 downto 0);
61      Q_PM_DOUT  : out std_logic_vector( 7 downto 0);
62      Q_T0        : out std_logic);
63 end component;
64
65 signal F_PC       : std_logic_vector(15 downto 0);
66 signal F_OPC      : std_logic_vector(31 downto 0);
67 signal F_PM_DOUT  : std_logic_vector( 7 downto 0);
68 signal F_T0        : std_logic;
69
70 component opc_deco is
71   port ( I_CLK      : in  std_logic;
72
73     I_OPC      : in  std_logic_vector(31 downto 0);
74     I_PC       : in  std_logic_vector(15 downto 0);
75     I_T0        : in  std_logic;
76
77     Q_ALU_OP    : out std_logic_vector( 4 downto 0);
78     Q_AMOD      : out std_logic_vector( 5 downto 0);
79     Q_BIT       : out std_logic_vector( 3 downto 0);
80     Q_DDDDD     : out std_logic_vector( 4 downto 0);
81     Q_IMM       : out std_logic_vector(15 downto 0);
82     Q_JADR      : out std_logic_vector(15 downto 0);
83     Q_OPC       : out std_logic_vector(15 downto 0);
84     Q_PC        : out std_logic_vector(15 downto 0);
85     Q_PC_OP     : out std_logic_vector( 2 downto 0);
86     Q_PMS       : out std_logic; -- program memory select
87     Q_RD_M      : out std_logic;
88     Q_RRRRR     : out std_logic_vector( 4 downto 0);
89     Q_RSEL      : out std_logic_vector( 1 downto 0);
90     Q_WE_01     : out std_logic;
91     Q_WE_D      : out std_logic_vector( 1 downto 0);
92     Q_WE_F      : out std_logic;
93     Q_WE_M      : out std_logic_vector( 1 downto 0);
94     Q_WE_XYZS  : out std_logic);
95 end component;
96
97 signal D_ALU_OP   : std_logic_vector( 4 downto 0);
98 signal D_AMOD     : std_logic_vector( 5 downto 0);
99 signal D_BIT       : std_logic_vector( 3 downto 0);
100 signal D_DDDDD    : std_logic_vector( 4 downto 0);
101 signal D_IMM      : std_logic_vector(15 downto 0);
102 signal D_JADR     : std_logic_vector(15 downto 0);
103 signal D_OPC      : std_logic_vector(15 downto 0);
104 signal D_PC       : std_logic_vector(15 downto 0);
105 signal D_PC_OP    : std_logic_vector( 2 downto 0);
106 signal D_PMS      : std_logic;
107 signal D_RD_M     : std_logic;
108 signal D_RRRRR    : std_logic_vector( 4 downto 0);
109 signal D_RSEL     : std_logic_vector( 1 downto 0);
110 signal D_WE_01    : std_logic;
111 signal D_WE_D     : std_logic_vector( 1 downto 0);
112 signal D_WE_F     : std_logic;
113 signal D_WE_M     : std_logic_vector( 1 downto 0);
114 signal D_WE_XYZS : std_logic;
115
116 component data_path
117   port( I_CLK      : in  std_logic;
118
119     I_ALU_OP    : in  std_logic_vector( 4 downto 0);
120     I_AMOD      : in  std_logic_vector( 5 downto 0);

```

14 LISTING OF cpu_core.vhd

```

121      I_BIT          : in  std_logic_vector( 3 downto 0);
122      I_DDDDD        : in  std_logic_vector( 4 downto 0);
123      I_DIN          : in  std_logic_vector( 7 downto 0);
124      I_IMM          : in  std_logic_vector(15 downto 0);
125      I_JADR         : in  std_logic_vector(15 downto 0);
126      I_PC_OP        : in  std_logic_vector( 2 downto 0);
127      I_OPC          : in  std_logic_vector(15 downto 0);
128      I_PC           : in  std_logic_vector(15 downto 0);
129      I_PMS          : in  std_logic;  -- program memory select
130      I_RD_M          : in  std_logic;
131      I_RRRRR        : in  std_logic_vector( 4 downto 0);
132      I_RSEL          : in  std_logic_vector( 1 downto 0);
133      I_WE_01         : in  std_logic;
134      I_WE_D          : in  std_logic_vector( 1 downto 0);
135      I_WE_F          : in  std_logic;
136      I_WE_M          : in  std_logic_vector( 1 downto 0);
137      I_WE_XYZS       : in  std_logic;
138
139      Q_ADR          : out std_logic_vector(15 downto 0);
140      Q_DOUT         : out std_logic_vector( 7 downto 0);
141      Q_INT_ENA       : out std_logic;
142      Q_LOAD_PC       : out std_logic;
143      Q_NEW_PC        : out std_logic_vector(15 downto 0);
144      Q_OPC           : out std_logic_vector(15 downto 0);
145      Q_PC            : out std_logic_vector(15 downto 0);
146      Q_RD_IO          : out std_logic;
147      Q_SKIP          : out std_logic;
148      Q_WE_IO          : out std_logic);
149 end component;
150
151 signal R_INT_ENA       : std_logic;
152 signal R_NEW_PC        : std_logic_vector(15 downto 0);
153 signal R_LOAD_PC       : std_logic;
154 signal R_SKIP          : std_logic;
155 signal R_ADR           : std_logic_vector(15 downto 0);
156
157 -- local signals
158 --
159 signal L_DIN           : std_logic_vector( 7 downto 0);
160 signal L_INTVEC_5       : std_logic;
161
162 begin
163
164     opcf : opc_fetch
165     port map(   I_CLK        => I_CLK,
166
167                 I_CLR        => I_CLR,
168                 I_INTVEC(5)  => L_INTVEC_5,
169                 I_INTVEC(4 downto 0) => I_INTVEC(4 downto 0),
170                 I_LOAD_PC    => R_LOAD_PC,
171                 I_NEW_PC     => R_NEW_PC,
172                 I_PM_ADR     => R_ADR(11 downto 0),
173                 I_SKIP        => R_SKIP,
174
175                 Q_PC          => F_PC,
176                 Q_OPC         => F_OPC,
177                 Q_T0          => F_T0,
178                 Q_PM_DOUT    => F_PM_DOUT);
179
180     odec : opc_deco
181     port map(   I_CLK        => I_CLK,
182

```

14 LISTING OF cpu_core.vhd

```

183      I_OPC      => F_OPC,
184      I_PC       => F_PC,
185      I_T0       => F_T0,
186
187      Q_ALU_OP   => D_ALU_OP,
188      Q_AMOD     => D_AMOD,
189      Q_BIT       => D_BIT,
190      Q_DDDDD    => D_DDDDD,
191      Q_IMM      => D_IMM,
192      Q_JADR     => D_JADR,
193      Q_OPC      => D_OPC,
194      Q_PC       => D_PC,
195      Q_PC_OP    => D_PC_OP,
196      Q_PMS      => D_PMS,
197      Q_RD_M     => D_RD_M,
198      Q_RRRRR    => D_RRRRR,
199      Q_RSEL     => D_RSEL,
200      Q_WE_01    => D_WE_01,
201      Q_WE_D     => D_WE_D,
202      Q_WE_F     => D_WE_F,
203      Q_WE_M     => D_WE_M,
204      Q_WE_XYZS  => D_WE_XYZS);
205
206      dpath : data_path
207      port map(  I_CLK      => I_CLK,
208
209          I_ALU_OP   => D_ALU_OP,
210          I_AMOD     => D_AMOD,
211          I_BIT      => D_BIT,
212          I_DDDDD    => D_DDDDD,
213          I_DIN      => L_DIN,
214          I_IMM      => D_IMM,
215          I_JADR     => D_JADR,
216          I_OPC      => D_OPC,
217          I_PC       => D_PC,
218          I_PC_OP    => D_PC_OP,
219          I_PMS      => D_PMS,
220          I_RD_M     => D_RD_M,
221          I_RRRRR    => D_RRRRR,
222          I_RSEL     => D_RSEL,
223          I_WE_01    => D_WE_01,
224          I_WE_D     => D_WE_D,
225          I_WE_F     => D_WE_F,
226          I_WE_M     => D_WE_M,
227          I_WE_XYZS  => D_WE_XYZS,
228
229          Q_ADR      => R_ADR,
230          Q_DOUT     => Q_DOUT,
231          Q_INT_ENA  => R_INT_ENA,
232          Q_NEW_PC   => R_NEW_PC,
233          Q_OPC      => Q_OPC,
234          Q_PC       => Q_PC,
235          Q_LOAD_PC  => R_LOAD_PC,
236          Q_RD_IO    => Q_RD_IO,
237          Q_SKIP      => R_SKIP,
238          Q_WE_IO    => Q_WE_IO);
239
240      L_DIN      <= F_PM_DOUT when (D_PMS = '1') else I_DIN(7 downto 0);
241      L_INTVEC_5 <= I_INTVEC(5) and R_INT_ENA;
242      Q_ADR_IO   <= R_ADR(7 downto 0);
243
244 end Behavioral;

```

14 LISTING OF cpu_core.vhd

245

src/cpu_core.vhd

15 LISTING OF data_mem.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      data_mem - Behavioral  
23 -- Create Date:     14:09:04 10/30/2009  
24 -- Description:    the data mempry of a CPU.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity data_mem is  
34     port (  I_CLK       : in  std_logic;  
35             IADR        : in  std_logic_vector(10 downto 0);  
36             IDIN        : in  std_logic_vector(15 downto 0);  
37             IWE         : in  std_logic_vector( 1 downto 0);  
38             QDOUT       : out std_logic_vector(15 downto 0));  
39 end data_mem;  
40  
41 architecture Behavioral of data_mem is  
42  
43 constant zero_256 : bit_vector := X"00000000000000000000000000000000"  
44                 & X"00000000000000000000000000000000";  
45 constant nine_256 : bit_vector := X"99999999999999999999999999999999"  
46                 & X"99999999999999999999999999999999";  
47  
48 component RAM1024X4  
49     generic(INIT_00 : bit_vector := zero_256;  
50               INIT_01 : bit_vector := zero_256;  
51               INIT_02 : bit_vector := zero_256;  
52               INIT_03 : bit_vector := zero_256;  
53               INIT_04 : bit_vector := zero_256;  
54               INIT_05 : bit_vector := zero_256;  
55               INIT_06 : bit_vector := zero_256;  
56               INIT_07 : bit_vector := zero_256;
```

15 LISTING OF data_mem.vhd

```

59      INIT_08 : bit_vector := zero_256;
60      INIT_09 : bit_vector := zero_256;
61      INIT_0A : bit_vector := zero_256;
62      INIT_0B : bit_vector := zero_256;
63      INIT_0C : bit_vector := zero_256;
64      INIT_0D : bit_vector := zero_256;
65      INIT_0E : bit_vector := zero_256;
66      INIT_0F : bit_vector := zero_256);
67
68      port ( DOA      : out std_logic_vector(3 downto 0);
69              DOB      : out std_logic_vector(3 downto 0);
70              ADDRA   : in  std_logic_vector(9 downto 0);
71              ADDRDB  : in  std_logic_vector(9 downto 0);
72              CLKA     : in  std_ulogic;
73              CLKB     : in  std_ulogic;
74              DIA      : in  std_logic_vector(3 downto 0);
75              DIB      : in  std_logic_vector(3 downto 0);
76              ENA      : in  std_ulogic;
77              ENB      : in  std_ulogic;
78              RSTA    : in  std_ulogic;
79              RSTB    : in  std_ulogic;
80              WEA     : in  std_ulogic;
81              WEB     : in  std_ulogic);
82      end component;
83
84      signal L_ADDR_0      : std_logic;
85      signal L_ADDR_E      : std_logic_vector(10 downto 1);
86      signal L_ADDR_O      : std_logic_vector(10 downto 1);
87      signal L_DIN_E       : std_logic_vector( 7 downto 0);
88      signal L_DIN_O       : std_logic_vector( 7 downto 0);
89      signal L_DOUT_E      : std_logic_vector( 7 downto 0);
90      signal L_DOUT_O      : std_logic_vector( 7 downto 0);
91      signal L_WE_E        : std_logic;
92      signal L_WE_O        : std_logic;
93
94      begin
95
96          sr_0 : RAM1024X4 -----
97          generic map(INIT_00 => nine_256, INIT_01 => nine_256, INIT_02 => nine_256,
98                      INIT_03 => nine_256, INIT_04 => nine_256, INIT_05 => nine_256,
99                      INIT_06 => nine_256, INIT_07 => nine_256, INIT_08 => nine_256,
100                     INIT_09 => nine_256, INIT_0A => nine_256, INIT_0B => nine_256,
101                     INIT_0C => nine_256, INIT_0D => nine_256, INIT_0E => nine_256,
102                     INIT_0F => nine_256)
103
104         port map( ADDRA => L_ADDR_E,                               ADDRDB => "0000000000",
105                  CLKA  => I_CLK,                                CLKB  => I_CLK,
106                  DIA   => L_DIN_E(3 downto 0),                DIB   => "0000",
107                  ENA   => '1',                                 ENB   => '0',
108                  RSTA  => '0',                                 RSTB  => '0',
109                  WEA   => L_WE_E,                             WEB   => '0',
110                  DOA   => L_DOUT_E(3 downto 0),               DOB   => open);
111
112         sr_1 : RAM1024X4 -----
113         generic map(INIT_00 => nine_256, INIT_01 => nine_256, INIT_02 => nine_256,
114                     INIT_03 => nine_256, INIT_04 => nine_256, INIT_05 => nine_256,
115                     INIT_06 => nine_256, INIT_07 => nine_256, INIT_08 => nine_256,
116                     INIT_09 => nine_256, INIT_0A => nine_256, INIT_0B => nine_256,
117                     INIT_0C => nine_256, INIT_0D => nine_256, INIT_0E => nine_256,
118                     INIT_0F => nine_256)
119
120         port map( ADDRA => L_ADDR_E,                               ADDRDB => "0000000000",

```

15 LISTING OF data_mem.vhd

```

121      CLKA  => I_CLK,           CLKB  => I_CLK,
122      DIA   => L_DIN_E(7 downto 4), DIB   => "0000",
123      ENA   => '1',            ENB   => '0',
124      RSTA  => '0',            RSTB  => '0',
125      WEA   => L_WE_E,         WEB   => '0',
126      DOA   => L_DOUT_E(7 downto 4), DOB   => open);
127
128      sr_2 : RAM1024X4 -----
129      generic map(INIT_00 => nine_256, INIT_01 => nine_256, INIT_02 => nine_256,
130                  INIT_03 => nine_256, INIT_04 => nine_256, INIT_05 => nine_256,
131                  INIT_06 => nine_256, INIT_07 => nine_256, INIT_08 => nine_256,
132                  INIT_09 => nine_256, INIT_0A => nine_256, INIT_0B => nine_256,
133                  INIT_0C => nine_256, INIT_0D => nine_256, INIT_0E => nine_256,
134                  INIT_0F => nine_256)
135
136      port map(  ADDRA => L_ADR_O,          ADDR_B => "0000000000",
137                  CLKA  => I_CLK,           CLKB  => I_CLK,
138                  DIA   => L_DIN_O(3 downto 0), DIB   => "0000",
139                  ENA   => '1',            ENB   => '0',
140                  RSTA  => '0',            RSTB  => '0',
141                  WEA   => L_WE_O,          WEB   => '0',
142                  DOA   => L_DOUT_O(3 downto 0), DOB   => open);
143
144      sr_3 : RAM1024X4 -----
145      generic map(INIT_00 => nine_256, INIT_01 => nine_256, INIT_02 => nine_256,
146                  INIT_03 => nine_256, INIT_04 => nine_256, INIT_05 => nine_256,
147                  INIT_06 => nine_256, INIT_07 => nine_256, INIT_08 => nine_256,
148                  INIT_09 => nine_256, INIT_0A => nine_256, INIT_0B => nine_256,
149                  INIT_0C => nine_256, INIT_0D => nine_256, INIT_0E => nine_256,
150                  INIT_0F => nine_256)
151
152      port map(  ADDRA => L_ADR_O,          ADDR_B => "0000000000",
153                  CLKA  => I_CLK,           CLKB  => I_CLK,
154                  DIA   => L_DIN_O(7 downto 4), DIB   => "0000",
155                  ENA   => '1',            ENB   => '0',
156                  RSTA  => '0',            RSTB  => '0',
157                  WEA   => L_WE_O,          WEB   => '0',
158                  DOA   => L_DOUT_O(7 downto 4), DOB   => open);
159
160
161      -- remember ADR(0)
162      --
163      adr0: process(I_CLK)
164      begin
165          if (rising_edge(I_CLK)) then
166              L_ADR_0      <= I_ADR(0);
167          end if;
168      end process;
169
170      -- we use two memory blocks _E and _O (even and odd).
171      -- This gives us a memory with ADR and ADR + 1 at the same time.
172      -- The second port is currently unused, but may be used later,
173      -- e.g. for DMA.
174      --
175
176      L_ADR_O      <= I_ADR(10 downto 1);
177      L_ADR_E      <= I_ADR(10 downto 1) + ("0000000000" & I_ADR(0));
178
179      L_DIN_E      <= I_DIN( 7 downto 0) when (I_ADR(0) = '0') else I_DIN(15 downto 8);
180      L_DIN_O      <= I_DIN( 7 downto 0) when (I_ADR(0) = '1') else I_DIN(15 downto 8);
181
182      L_WE_E       <= I_WE(1) or (I_WE(0) and not I_ADR(0));

```

15 LISTING OF data_mem.vhd

```
183      L_WE_O      <= I_WE(1) or (I_WE(0) and      I_ADR(0));  
184  
185      Q_DOUT( 7 downto 0)      <= L_DOUT_E when (L_ADR_0 = '0') else L_DOUT_O;  
186      Q_DOUT(15 downto 8)      <= L_DOUT_E when (L_ADR_0 = '1') else L_DOUT_O;  
187  
188  end Behavioral;  
189
```

src/data_mem.vhd

16 LISTING OF data_path.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      data_path - Behavioral  
23 -- Create Date:     13:24:10 10/29/2009  
24 -- Description:    the data path of a CPU.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.std_logic_1164.ALL;  
30 use IEEE.std_logic_ARITH.ALL;  
31 use IEEE.std_logic_UNSIGNED.ALL;  
32  
33 use work.common.ALL;  
34  
35 entity data_path is  
36     port(  I_CLK          : in  std_logic;  
37             I_ALU_OP       : in  std_logic_vector( 4 downto 0);  
38             I_AMOD        : in  std_logic_vector( 5 downto 0);  
39             I_BIT         : in  std_logic_vector( 3 downto 0);  
40             I_DDDDD        : in  std_logic_vector( 4 downto 0);  
41             I_DIN         : in  std_logic_vector( 7 downto 0);  
42             I_IMM          : in  std_logic_vector(15 downto 0);  
43             I_JADR         : in  std_logic_vector(15 downto 0);  
44             I_OPC          : in  std_logic_vector(15 downto 0);  
45             I_PC           : in  std_logic_vector(15 downto 0);  
46             I_PC_OP        : in  std_logic_vector( 2 downto 0);  
47             I_PMS          : in  std_logic;  -- program memory select  
48             I_RD_M         : in  std_logic;  
49             I_RRRRR        : in  std_logic_vector( 4 downto 0);  
50             I_RSEL         : in  std_logic_vector( 1 downto 0);  
51             I_WE_01        : in  std_logic;  
52             I_WE_D         : in  std_logic_vector( 1 downto 0);  
53             I_WE_F         : in  std_logic;  
54             I_WE_M         : in  std_logic_vector( 1 downto 0);  
55             I_WE_XYZS      : in  std_logic;  
56             Q_ADR          : out std_logic_vector(15 downto 0);  
57
```

16 LISTING OF data_path.vhd

```

59      Q_DOUT      : out std_logic_vector( 7 downto 0);
60      Q_INT_ENA   : out std_logic;
61      Q_LOAD_PC   : out std_logic;
62      Q_NEW_PC    : out std_logic_vector(15 downto 0);
63      Q_OPC        : out std_logic_vector(15 downto 0);
64      Q_PC         : out std_logic_vector(15 downto 0);
65      Q_RD_IO     : out std_logic;
66      Q_SKIP       : out std_logic;
67      Q_WE_IO     : out std_logic);
68 end data_path;
69
70 architecture Behavioral of data_path is
71
72 component alu
73     port ( I_ALU_OP   : in  std_logic_vector( 4 downto 0);
74             I_BIT       : in  std_logic_vector( 3 downto 0);
75             I_D          : in  std_logic_vector(15 downto 0);
76             I_D0         : in  std_logic;
77             I_DIN        : in  std_logic_vector( 7 downto 0);
78             I_FLAGS      : in  std_logic_vector( 7 downto 0);
79             I_IMM        : in  std_logic_vector( 7 downto 0);
80             I_PC         : in  std_logic_vector(15 downto 0);
81             I_R          : in  std_logic_vector(15 downto 0);
82             I_R0         : in  std_logic;
83             I_RSEL       : in  std_logic_vector( 1 downto 0);
84
85             Q_FLAGS      : out std_logic_vector( 9 downto 0);
86             Q_DOUT       : out std_logic_vector(15 downto 0));
87 end component;
88
89 signal A_DOUT      : std_logic_vector(15 downto 0);
90 signal A_FLAGS      : std_logic_vector( 9 downto 0);
91
92 component register_file
93     port ( I_CLK       : in  std_logic;
94
95             I_AMOD      : in  std_logic_vector( 5 downto 0);
96             I_COND       : in  std_logic_vector( 3 downto 0);
97             I_DDDDD      : in  std_logic_vector( 4 downto 0);
98             I_DIN        : in  std_logic_vector(15 downto 0);
99             I_FLAGS      : in  std_logic_vector( 7 downto 0);
100            I_IMM        : in  std_logic_vector(15 downto 0);
101            I_RRRR       : in  std_logic_vector( 4 downto 1);
102            I_WE_01      : in  std_logic;
103            I_WE_D       : in  std_logic_vector( 1 downto 0);
104            I_WE_F       : in  std_logic;
105            I_WE_M       : in  std_logic;
106            I_WE_XYZS    : in  std_logic;
107
108            Q_ADR        : out std_logic_vector(15 downto 0);
109            Q_CC         : out std_logic;
110            Q_D          : out std_logic_vector(15 downto 0);
111            Q_FLAGS      : out std_logic_vector( 7 downto 0);
112            Q_R          : out std_logic_vector(15 downto 0);
113            Q_S          : out std_logic_vector( 7 downto 0);
114            Q_Z          : out std_logic_vector(15 downto 0));
115 end component;
116
117 signal F_ADR      : std_logic_vector(15 downto 0);
118 signal F_CC       : std_logic;
119 signal F_D        : std_logic_vector(15 downto 0);
120 signal F_FLAGS    : std_logic_vector( 7 downto 0);

```

16 LISTING OF data_path.vhd

```

121      signal F_R          : std_logic_vector(15 downto 0);
122      signal F_S          : std_logic_vector( 7 downto 0);
123      signal F_Z          : std_logic_vector(15 downto 0);
124
125      component data_mem
126          port (  I_CLK       : in  std_logic;
127                    I_ADR       : in  std_logic_vector(10 downto 0);
128                    I_DIN       : in  std_logic_vector(15 downto 0);
129                    I_WE        : in  std_logic_vector( 1 downto 0);
130
131                    Q_DOUT      : out std_logic_vector(15 downto 0));
132      end component;
133
134      signal M_DOUT        : std_logic_vector(15 downto 0);
135
136      signal L_DIN         : std_logic_vector( 7 downto 0);
137      signal L_WE_SRAM     : std_logic_vector( 1 downto 0);
138      signal L_FLAGS_98     : std_logic_vector( 9 downto 8);
139
140
141 begin
142
143     alui : alu
144     port map(  I_ALU_OP    => I_ALU_OP,
145                 I_BIT       => I_BIT,
146                 I_D         => F_D,
147                 I_D0        => I_DDDDD(0),
148                 I_DIN       => L_DIN,
149                 I_FLAGS     => F_FLAGS,
150                 I_IMM       => I_IMM(7 downto 0),
151                 I_PC        => I_PC,
152                 I_R         => F_R,
153                 I_R0        => I_RRRRR(0),
154                 I_RSEL      => I_RSEL,
155
156                 Q_FLAGS     => A_FLAGS,
157                 Q_DOUT      => A_DOUT);
158
159     regs : register_file
160     port map(  I_CLK       => I_CLK,
161
162                 I_AMOD      => I_AMOD,
163                 I_COND(3)   => I_OPC(10),
164                 I_COND(2 downto 0)=> I_OPC(2 downto 0),
165                 I_DDDDD     => I_DDDDD,
166                 I_DIN       => A_DOUT,
167                 I_FLAGS     => A_FLAGS(7 downto 0),
168                 I_IMM       => I_IMM,
169                 I_RRRR      => I_RRRRR(4 downto 1),
170                 I_WE_01     => I_WE_01,
171                 I_WE_D      => I_WE_D,
172                 I_WE_F      => I_WE_F,
173                 I_WE_M      => I_WE_M(0),
174                 I_WE_XYZS   => I_WE_XYZS,
175
176                 Q_ADR       => F_ADR,
177                 Q_CC        => F_CC,
178                 Q_D         => F_D,
179                 Q_FLAGS     => F_FLAGS,
180                 Q_R         => F_R,
181                 Q_S         => F_S,    -- Q_Rxx(F_ADR)
182                 Q_Z         => F_Z);

```

16 LISTING OF data_path.vhd

```

183
184      sram : data_mem
185      port map(    I_CLK      => I_CLK,
186
187                  I_ADR      => F_ADR(10 downto 0),
188                  I_DIN      => A_DOUT,
189                  I_WE       => L_WE_SRAM,
190
191                  Q_DOUT     => M_DOUT);
192
193      -- remember A_FLAGS(9 downto 8) (within the current instruction).
194      --
195      flg98: process(I_CLK)
196      begin
197          if (rising_edge(I_CLK)) then
198              L_FLAGS_98      <= A_FLAGS(9 downto 8);
199          end if;
200      end process;
201
202      -- whether PC shall be loaded with NEW_PC or not.
203      -- I.e. if a branch shall be taken or not.
204      --
205      process(I_PC_OP, F_CC)
206      begin
207          case I_PC_OP is
208              when PC_BCC  => Q_LOAD_PC      <= F_CC;           -- maybe (PC on I_JADR)
209              when PC_LD_I => Q_LOAD_PC      <= '1';            -- yes: new PC on I_JADR
210              when PC_LD_Z => Q_LOAD_PC      <= '1';            -- yes: new PC in Z
211              when PC_LD_S => Q_LOAD_PC      <= '1';            -- yes: new PC on stack
212              when others   => Q_LOAD_PC      <= '0';            -- no.
213          end case;
214      end process;
215
216      -- whether the next instruction shall be skipped or not.
217      --
218      process(I_PC_OP, L_FLAGS_98, F_CC)
219      begin
220          case I_PC_OP is
221              when PC_BCC  => Q_SKIP        <= F_CC;           -- if cond met
222              when PC_LD_I => Q_SKIP        <= '1';            -- yes
223              when PC_LD_Z => Q_SKIP        <= '1';            -- yes
224              when PC_LD_S => Q_SKIP        <= '1';            -- yes
225              when PC_SKIP_Z => Q_SKIP      <= L_FLAGS_98(8);  -- if Z set
226              when PC_SKIP_T => Q_SKIP      <= L_FLAGS_98(9);  -- if T set
227              when others   => Q_SKIP        <= '0';            -- no.
228          end case;
229      end process;
230
231      Q_ADR        <= F_ADR;
232      Q_DOUT       <= A_DOUT(7 downto 0);
233      Q_INT_ENA    <= A_FLAGS(7);
234      Q_OPC         <= I_OPC;
235      Q_PC          <= I_PC;
236
237      Q_RD_IO       <= '0'           when (F_ADR <X"20")
238          else (I_RD_M and not I_PMS) when (F_ADR      <X"5D")
239          else '0';
240      Q_WE_IO       <= '0'           when (F_ADR <X"20")
241          else I_WE_M(0)           when (F_ADR      <X"5D")
242          else '0';
243      L_WE_SRAM    <= "00"    when (F_ADR <X"0060") else I_WE_M;
244      L_DIN         <= I_DIN   when (I_PMS = '1')

```

16 LISTING OF data_path.vhd

```
245      else F_S      when  (F_ADR          <X"0020")
246      else I_DIN    when  (F_ADR          <X"005D")
247      else F_S      when  (F_ADR          <X"0060")
248      else M_DOUT(7 downto 0);
249
250      -- compute potential new PC value from Z, (SP), or IMM.
251      --
252      Q_NEW_PC      <= F_Z      when I_PC_OP = PC_LD_Z      -- IJMP, ICALL
253      else M_DOUT when I_PC_OP = PC_LD_S      -- RET, RETI
254      else I_JADR;                          -- JMP adr
255
256  end Behavioral;
257
```

src/data_path.vhd

17 LISTING OF io.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      io - Behavioral  
23 -- Create Date:     13:59:36 11/07/2009  
24 -- Description:    the I/O of a CPU (uart and general purpose I/O lines).  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity io is  
34     port (  I_CLK          : in  std_logic;  
35             I_CLR          : in  std_logic;  
36             I_ADDR_IO      : in  std_logic_vector( 7 downto 0);  
37             I_DIN          : in  std_logic_vector( 7 downto 0);  
38             I_SWITCH        : in  std_logic_vector( 7 downto 0);  
39             I_RD_IO         : in  std_logic;  
40             I_RX           : in  std_logic;  
41             I_WE_IO         : in  std_logic;  
42             Q_7_SEGMENT    : out std_logic_vector( 6 downto 0);  
43             Q_DOUT         : out std_logic_vector( 7 downto 0);  
44             Q_INTVEC       : out std_logic_vector( 5 downto 0);  
45             Q_LEDS         : out std_logic_vector( 1 downto 0);  
46             Q_TX           : out std_logic);  
47  
48 end io;  
49  
50  
51 architecture Behavioral of io is  
52  
53 component uart  
54     generic(CLOCK_FREQ  : std_logic_vector(31 downto 0);  
55                 BAUD_RATE   : std_logic_vector(27 downto 0));  
56     port(  I_CLK          : in  std_logic;  
57             I_CLR          : in  std_logic;  
58             I_RD           : in  std_logic;
```

17 LISTING OF io.vhd

```

59      I_WE          : in  std_logic;
60      I_RX          : in  std_logic;
61      I_TX_DATA    : in  std_logic_vector(7 downto 0);
62
63      Q_RX_DATA    : out std_logic_vector(7 downto 0);
64      Q_RX_READY   : out std_logic;
65      Q_TX          : out std_logic;
66      Q_TX_BUSY    : out std_logic);
67 end component;
68
69 signal U_RX_READY    : std_logic;
70 signal U_TX_BUSY     : std_logic;
71 signal U_RX_DATA     : std_logic_vector( 7 downto 0);
72
73 signal L_INTVEC      : std_logic_vector( 5 downto 0);
74 signal L_LEDS         : std_logic;
75 signal L_RD_UART     : std_logic;
76 signal L_RX_INT_ENABLED : std_logic;
77 signal L_TX_INT_ENABLED : std_logic;
78 signal L_WE_UART     : std_logic;
79
80 begin
81     urt: uart
82         generic map(CLOCK_FREQ  => std_logic_vector(conv_unsigned(25000000, 32)),
83                      BAUD_RATE    => std_logic_vector(conv_unsigned( 38400, 28)))
84         port map(  I_CLK        => I_CLK,
85                    I_CLR        => I_CLR,
86                    I_RD         => L_RD_UART,
87                    I_WE         => L_WE_UART,
88                    I_TX_DATA   => I_DIN(7 downto 0),
89                    I_RX         => I_RX,
90
91                    Q_TX         => Q_TX,
92                    Q_RX_DATA   => U_RX_DATA,
93                    Q_RX_READY  => U_RX_READY,
94                    Q_TX_BUSY   => U_TX_BUSY);
95
96     -- IO read process
97     --
98     iord: process(I_ADDR_IO, I_SWITCH,
99                  U_RX_DATA, U_RX_READY, L_RX_INT_ENABLED,
100                 U_TX_BUSY, L_TX_INT_ENABLED)
101 begin
102     -- addresses for mega8 device (use iom8.h or #define __AVR_ATmega8__).
103     --
104     case I_ADDR_IO is
105         when X"2A"  => Q_DOUT      <=           -- UCSRB:
106                         L_RX_INT_ENABLED  -- Rx complete int enabled.
107                         & L_TX_INT_ENABLED  -- Tx complete int enabled.
108                         & L_TX_INT_ENABLED  -- Tx empty int enabled.
109                         & '1'                -- Rx enabled
110                         & '1'                -- Tx enabled
111                         & '0'                -- 8 bits/char
112                         & '0'                -- Rx bit 8
113                         & '0';               -- Tx bit 8
114         when X"2B"  => Q_DOUT      <=           -- UCSRA:
115                         U_RX_READY       -- Rx complete
116                         & not U_TX_BUSY   -- Tx complete
117                         & not U_TX_BUSY   -- Tx ready
118                         & '0'              -- frame error
119                         & '0'              -- data overrun
120                         & '0'              -- parity error

```

17 LISTING OF io.vhd

```

121                      & '0'                  -- double dpeed
122                      & '0';                 -- multiproc mode
123      when X"2C"  => Q_DOUT      <= U_RX_DATA; -- UDR
124      when X"40"  => Q_DOUT      <=
125                      '1'                   -- URSEL
126                      & '0'                   -- asynchronous
127                      & "00"                  -- no parity
128                      & '1'                   -- two stop bits
129                      & "11"                  -- 8 bits/char
130                      & '0';                 -- rising clock edge
131
132      when X"36"  => Q_DOUT      <= I_SWITCH;  -- PINB
133      when others => Q_DOUT      <= X"AA";
134  end case;
135 end process;
136
137 -- IO write process
138 --
139 iowr: process(I_CLK)
140 begin
141     if (rising_edge(I_CLK)) then
142         if (I_CLR = '1') then
143             L_RX_INT_ENABLED      <= '0';
144             L_TX_INT_ENABLED      <= '0';
145         elsif (I_WE_IO = '1') then
146             case I_ADDR_IO is
147                 when X"38"  => Q_7_SEGMENT      <= I_DIN(6 downto 0);      -- PORTB
148                     L_LEDS            <= not L_LEDS;
149                 when X"40"  => -- handled by uart
150                 when X"41"  => -- handled by uart
151                 when X"43"  => L_RX_INT_ENABLED      <= I_DIN(0);
152                     L_TX_INT_ENABLED      <= I_DIN(1);
153                 when others =>
154             end case;
155         end if;
156     end if;
157 end process;
158
159 -- interrupt process
160 --
161 ioint: process(I_CLK)
162 begin
163     if (rising_edge(I_CLK)) then
164         if (I_CLR = '1') then
165             L_INTVEC        <= "000000";
166         else
167             if (L_RX_INT_ENABLED and U_RX_READY) = '1' then
168                 if (L_INTVEC(5) = '0') then      -- no interrupt pending
169                     L_INTVEC        <= "101011";      -- _VECTOR(11)
170                 end if;
171             elsif (L_TX_INT_ENABLED and not U_TX_BUSY) = '1' then
172                 if (L_INTVEC(5) = '0') then      -- no interrupt pending
173                     L_INTVEC        <= "101100";      -- _VECTOR(12)
174                 end if;
175             else                                -- no interrupt
176                 L_INTVEC        <= "000000";
177             end if;
178         end if;
179     end if;
180 end process;
181
182 L_WE_UART      <= I_WE_IO when (I_ADDR_IO = X"2C") else '0'; -- write UART UDR

```

17 LISTING OF io.vhd

```
183      L_RD_UART      <= I_RD_IO when (I_ADR_IO = X"2C") else '0'; -- read UART UDR
184
185      Q_LEDS(1)       <= L_LEDS;
186      Q_LEDS(0)       <= not L_LEDS;
187      Q_INTVEC        <= L_INTVEC;
188
189  end Behavioral;
190
```

src/io.vhd

18 Listing of opc_deco.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      opc_deco - Behavioral  
23 -- Create Date:      16:05:16 10/29/2009  
24 -- Description:     the opcode decoder of a CPU.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 use work.common.ALL;  
34  
35 entity opc_deco is  
36     port (  
37         I_CLK      : in  std_logic;  
38         I_OPC      : in  std_logic_vector(31 downto 0);  
39         I_PC       : in  std_logic_vector(15 downto 0);  
40         I_T0       : in  std_logic;  
41         Q_ALU_OP   : out std_logic_vector( 4 downto 0);  
42         Q_AMOD     : out std_logic_vector( 5 downto 0);  
43         Q_BIT      : out std_logic_vector( 3 downto 0);  
44         Q_DDDDD    : out std_logic_vector( 4 downto 0);  
45         Q_IMM      : out std_logic_vector(15 downto 0);  
46         Q_JADR     : out std_logic_vector(15 downto 0);  
47         Q_OPC      : out std_logic_vector(15 downto 0);  
48         Q_PC       : out std_logic_vector(15 downto 0);  
49         Q_PC_OP    : out std_logic_vector( 2 downto 0);  
50         Q_PMS      : out std_logic;  -- program memory select  
51         Q_RD_M     : out std_logic;  
52         Q_RRRRR    : out std_logic_vector( 4 downto 0);  
53         Q_RSEL     : out std_logic_vector( 1 downto 0);  
54         Q_WE_01    : out std_logic;  
55         Q_WE_D     : out std_logic_vector( 1 downto 0);  
56         Q_WE_F     : out std_logic;  
57         Q_WE_M    : out std_logic_vector( 1 downto 0);  
58     );
```

18 Listing of opc_deco.vhd

```
59          Q_WE_XYZS  : out std_logic);
60      end opc_deco;
61
62      architecture Behavioral of opc_deco is
63
64      begin
65
66          process(I_CLK)
67          begin
68              if (rising_edge(I_CLK)) then
69                  --
70                  -- set the most common settings as default.
71                  --
72                  Q_ALU_OP      <= ALU_D_MV_Q;
73                  Q_AMOD        <= AMOD_ABS;
74                  Q_BIT         <= I_OPCODE(10) & I_OPCODE(2 downto 0);
75                  Q_DDDDD       <= I_OPCODE(8 downto 4);
76                  Q_IMM         <= X"0000";
77                  Q_JADR        <= I_OPCODE(31 downto 16);
78                  Q_OPC         <= I_OPCODE(15 downto 0);
79                  Q_PC          <= I_PC;
80                  Q_PC_OP       <= PC_NEXT;
81                  Q_PMS         <= '0';
82                  Q_RD_M        <= '0';
83                  Q_RRRRR       <= I_OPCODE(9) & I_OPCODE(3 downto 0);
84                  Q_RSEL        <= RS_REG;
85                  Q_WE_D        <= "00";
86                  Q_WE_01       <= '0';
87                  Q_WE_F        <= '0';
88                  Q_WE_M        <= "00";
89                  Q_WE_XYZS    <= '0';
90
91          case I_OPCODE(15 downto 10) is
92              when "000000" =>
93                  case I_OPCODE(9 downto 8) is
94                      when "00" =>
95                          --
96                          -- 0000 0000 0000 0000 - NOP
97                          -- 0000 0000 001v vvvv - INTERRUPT
98                          --
99                      if (I_OPCODE(5)) = '1' then -- interrupt
100                          Q_ALU_OP      <= ALU_INTR;
101                          Q_AMOD        <= AMOD_ddSP;
102                          Q_JADR        <= "0000000000" & I_OPCODE(4 downto 0) & "0";
103                          Q_PC_OP       <= PC_LD_I;
104                          Q_WE_F        <= '1';
105                          Q_WE_M        <= "11";
106                      end if;
107
108                  when "01" =>
109                      --
110                      -- 0000 0001 dddd rrrr - MOVW
111                      --
112                      Q_DDDDD       <= I_OPCODE(7 downto 4) & "0";
113                      Q_RRRRR       <= I_OPCODE(3 downto 0) & "0";
114                      Q_ALU_OP      <= ALU_MV_16;
115                      Q_WE_D        <= "11";
116
117                  when "10" =>
118                      --
119                      -- 0000 0010 dddd rrrr - MULS
120                      --
```

18 Listing of opc_deco.vhd

```

121      Q_DDDDD      <= "1" & I_OPC(7 downto 4);
122      Q_RRRRR      <= "1" & I_OPC(3 downto 0);
123      Q_ALU_OP     <= ALU_MULT;
124      Q_IMM(7 downto 5)      <= MULT_SS;
125      Q_WE_01      <= '1';
126      Q_WE_F       <= '1';
127
128      when others =>
129          --
130          -- 0000 0011 0ddd 0rrr - _MULSU  SU "010"
131          -- 0000 0011 0ddd 1rrr - FMUL    UU "100"
132          -- 0000 0011 1ddd 0rrr - FMULS   SS "111"
133          -- 0000 0011 1ddd 1rrr - FMULSU  SU "110"
134          --
135          Q_DDDDD(4 downto 3)      <= "10";      -- regs 16 to 23
136          Q_RRRRR(4 downto 3)      <= "10";      -- regs 16 to 23
137          Q_ALU_OP     <= ALU_MULT;
138          if I_OPC(7) = '0' then
139              if I_OPC(3) = '0' then
140                  Q_IMM(7 downto 5)      <= MULT_SU;
141              else
142                  Q_IMM(7 downto 5)      <= MULT_FUU;
143              end if;
144          else
145              if I_OPC(3) = '0' then
146                  Q_IMM(7 downto 5)      <= MULT_FSS;
147              else
148                  Q_IMM(7 downto 5)      <= MULT_FSU;
149              end if;
150          end if;
151          Q_WE_01      <= '1';
152          Q_WE_F       <= '1';
153      end case;
154
155      when "000001" | "000010" =>
156          --
157          -- 0000 01rd dddd rrrr - CPC = SBC without Q_WE_D
158          -- 0000 10rd dddd rrrr - SBC
159          --
160          Q_ALU_OP     <= ALU_SBC;
161          Q_WE_D       <= '0' & I_OPC(11);  -- write Rd if SBC.
162          Q_WE_F       <= '1';
163
164      when "000011" =>
165          --
166          -- 0000 11rd dddd rrrr - ADD
167          --
168          Q_ALU_OP     <= ALU_ADD;
169          Q_WE_D       <= "01";
170          Q_WE_F       <= '1';
171
172      when "000100" => -- CPSE
173          Q_ALU_OP     <= ALU_SUB;
174          Q_RD_M       <= I_T0;
175          if (I_T0 = '0') then      -- second cycle.
176              Q_PC_OP      <= PC_SKIP_Z;
177          end if;
178
179      when "000101" | "000110" =>
180          --
181          -- 0001 01rd dddd rrrr - CP = SUB without Q_WE_D
182          -- 0000 10rd dddd rrrr - SUB

```

18 Listing of opc_deco.vhd

```

183      --
184      Q_ALU_OP      <= ALU_SUB;
185      Q_WE_D       <= '0' & I_OPCODE(11); -- write Rd if SUB.
186      Q_WE_F       <= '1';
187
188      when "000111" =>
189          --
190          -- 0001 11rd dddd rrrr - ADC
191          --
192          Q_ALU_OP      <= ALU_ADC;
193          Q_WE_D       <= "01";
194          Q_WE_F       <= '1';
195
196      when "001000" =>
197          --
198          -- 0010 00rd dddd rrrr - AND
199          --
200          Q_ALU_OP      <= ALU_AND;
201          Q_WE_D       <= "01";
202          Q_WE_F       <= '1';
203
204      when "001001" =>
205          --
206          -- 0010 01rd dddd rrrr - EOR
207          --
208          Q_ALU_OP      <= ALU_EOR;
209          Q_WE_D       <= "01";
210          Q_WE_F       <= '1';
211
212      when "001010" => -- OR
213          --
214          -- 0010 10rd dddd rrrr - OR
215          --
216          Q_ALU_OP      <= ALU_OR;
217          Q_WE_D       <= "01";
218          Q_WE_F       <= '1';
219
220      when "001011" =>
221          --
222          -- 0010 11rd dddd rrrr - MOV
223          --
224          Q_ALU_OP      <= ALU_R_MV_Q;
225          Q_WE_D       <= "01";
226
227      when "001100" | "001101" | "001110" | "001111"
228      | "010100" | "010101" | "010110" | "010111" =>
229          --
230          -- 0011 KKKK dddd KKKK - CPI
231          -- 0101 KKKK dddd KKKK - SUBI
232          --
233          Q_ALU_OP      <= ALU_SUB;
234          Q_IMM(7 downto 0)    <= I_OPCODE(11 downto 8) & I_OPCODE(3 downto 0);
235          Q_RSEL        <= RS_IMM;
236          Q_DDDDD(4)     <= '1';      -- Rd = 16...31
237          Q_WE_D       <= '0' & I_OPCODE(14);
238          Q_WE_F       <= '1';
239
240      when "010000" | "010001" | "010010" | "010011" =>
241          --
242          -- 0100 KKKK dddd KKKK - SBCI
243          --
244          Q_ALU_OP      <= ALU_SBC;

```

18 Listing of opc_deco.vhd

```

245          Q_IMM(7 downto 0)      <= I_OPC(11 downto 8) & I_OPC(3 downto 0);
246          Q_RSEL            <= RS_IMM;
247          Q_DDDDD(4)        <= '1';      -- Rd = 16...31
248          Q_WE_D            <= "01";
249          Q_WE_F            <= '1';
250
251      when "011000" | "011001" | "011010" | "011011" =>
252          --
253          -- 0110 KKKK dddd KKKK - ORI
254          --
255          Q_ALU_OP           <= ALU_OR;
256          Q_IMM(7 downto 0)      <= I_OPC(11 downto 8) & I_OPC(3 downto 0);
257          Q_RSEL            <= RS_IMM;
258          Q_DDDDD(4)        <= '1';      -- Rd = 16...31
259          Q_WE_D            <= "01";
260          Q_WE_F            <= '1';
261
262      when "011100" | "011101" | "011110" | "011111" =>
263          --
264          -- 0111 KKKK dddd KKKK - ANDI
265          --
266          Q_ALU_OP           <= ALU_AND;
267          Q_IMM(7 downto 0)      <= I_OPC(11 downto 8) & I_OPC(3 downto 0);
268          Q_RSEL            <= RS_IMM;
269          Q_DDDDD(4)        <= '1';      -- Rd = 16...31
270          Q_WE_D            <= "01";
271          Q_WE_F            <= '1';
272
273      when "100000" | "100001" | "100010" | "100011"
274      | "101000" | "101001" | "101010" | "101011" =>
275          --
276          -- LDD (Y + q) == LD (y) if q == 0
277          --
278          -- 10q0 qq0d dddd 1qqq  LDD (Y + q)
279          -- 10q0 qq0d dddd 0qqq  LDD (Z + q)
280          -- 10q0 qq1d dddd 1qqq  SDD (Y + q)
281          -- 10q0 qq1d dddd 0qqq  SDD (Z + q)
282          --          L/      Z/
283          --          S       Y
284          --
285          Q_IMM(5)           <= I_OPC(13);
286          Q_IMM(4 downto 3)      <= I_OPC(11 downto 10);
287          Q_IMM(2 downto 0)      <= I_OPC( 2 downto 0);
288
289      if (I_OPC(3) = '0') then    Q_AMOD      <= AMOD_Zq;
290      else                      Q_AMOD      <= AMOD_Yq;
291      end if;
292
293      Q_RD_M            <= not I_OPC(9);           -- '1'  if LDD
294      Q_WE_M            <= '0' & I_OPC(9);           -- "01" if STD
295
296      when "100100" =>
297          Q_IMM           <= I_OPC(31 downto 16);   -- absolute address for LDS/STS
298          if (I_OPC(9) = '0') then      -- LDD / POP
299              --
300              -- 1001 00-0d dddd 0000 - LDS
301              -- 1001 00-0d dddd 0001 - LD Rd, Z+
302              -- 1001 00-0d dddd 0010 - LD Rd, -Z
303              -- 1001 00-0d dddd 0100 - (ii) LPM Rd, (Z)
304              -- 1001 00-0d dddd 0101 - (iii) LPM Rd, (Z+)
305              -- 1001 00-0d dddd 0110 - ELPMD Z      --- not mega8
306              -- 1001 00-0d dddd 0111 - ELPMD Z+     --- not mega8

```

18 Listing of opc_deco.vhd

```

307      -- 1001 00-0d dddd 1001 - LD Rd, Y+
308      -- 1001 00-0d dddd 1010 - LD Rd, -Y
309      -- 1001 00-0d dddd 1100 - LD Rd, X
310      -- 1001 00-0d dddd 1101 - LD Rd, X+
311      -- 1001 00-0d dddd 1110 - LD Rd, -X
312      -- 1001 00-0d dddd 1111 - POP Rd
313      --
314      Q_RSEL      <= RS_DIN;
315      Q_RD_M      <= I_T0;
316      Q_WE_D      <= '0' & not I_T0;
317      Q_WE_XYZS   <= not I_T0;
318      Q_PMS       <= (not I_OPC(3)) and I_OPC(2) and (not I_OPC(1));
319      case I_OPC(3 downto 0) is
320          when "0000" => Q_AMOD      <= AMOD_ABS;    Q_WE_XYZS <= '0';
321          when "0001" => Q_AMOD      <= AMOD_Zi;
322          when "0100" => Q_AMOD      <= AMOD_Z;      Q_WE_XYZS <= '0';
323          when "0101" => Q_AMOD      <= AMOD_Zi;
324          when "1001" => Q_AMOD      <= AMOD_Yi;
325          when "1010" => Q_AMOD      <= AMOD_dY;
326          when "1100" => Q_AMOD      <= AMOD_X;      Q_WE_XYZS <= '0';
327          when "1101" => Q_AMOD      <= AMOD_Xi;
328          when "1110" => Q_AMOD      <= AMOD_dX;
329          when "1111" => Q_AMOD      <= AMOD_SPi;
330          when others =>           Q_WE_XYZS      <= '0';
331      end case;
332  else                                     -- STD / PUSH
333      --
334      -- 1001 00-1r rrrr 0000 - STS
335      -- 1001 00-1r rrrr 0001 - ST Z+. Rr
336      -- 1001 00-1r rrrr 0010 - ST -Z. Rr
337      -- 1001 00-1r rrrr 1000 - ST Y. Rr
338      -- 1001 00-1r rrrr 1001 - ST Y+. Rr
339      -- 1001 00-1r rrrr 1010 - ST -Y. Rr
340      -- 1001 00-1r rrrr 1100 - ST X. Rr
341      -- 1001 00-1r rrrr 1101 - ST X+. Rr
342      -- 1001 00-1r rrrr 1110 - ST -X. Rr
343      -- 1001 00-1r rrrr 1111 - PUSH Rr
344      --
345      Q_ALU_OP     <= ALU_D_MV_Q;
346      Q_WE_M       <= "01";
347      Q_WE_XYZS   <= '1';
348      case I_OPC(3 downto 0) is
349          when "0000" => Q_AMOD      <= AMOD_ABS;    Q_WE_XYZS <= '0';
350          when "0001" => Q_AMOD      <= AMOD_Zi;
351          when "0010" => Q_AMOD      <= AMOD_dZ;
352          when "1001" => Q_AMOD      <= AMOD_Yi;
353          when "1010" => Q_AMOD      <= AMOD_dY;
354          when "1100" => Q_AMOD      <= AMOD_X;      Q_WE_XYZS <= '0';
355          when "1101" => Q_AMOD      <= AMOD_Xi;
356          when "1110" => Q_AMOD      <= AMOD_dX;
357          when "1111" => Q_AMOD      <= AMOD_dSP;
358          when others =>
359      end case;
360  end if;
361
362  when "100101" =>
363      if (I_OPC(9) = '0') then
364          if (I_OPC(3) = '0') then
365              --
366              -- 1001 010d dddd 0000 - COM
367              -- 1001 010d dddd 0001 - NEG
368              -- 1001 010d dddd 0010 - SWAP

```

18 Listing of opc_deco.vhd

```

369          -- 1001 010d dddd 0011 - INC
370          -- 1001 010d dddd 0101 - ASR
371          -- 1001 010d dddd 0110 - LSR
372          -- 1001 010d dddd 0111 - ROR
373          --
374          case I_OPC(2 downto 0) is
375              when "000" => Q_ALU_OP      <= ALU_COM;
376              when "001" => Q_ALU_OP      <= ALU_NEG;
377              when "010" => Q_ALU_OP      <= ALU_SWAP;
378              when "011" => Q_ALU_OP      <= ALU_INC;
379              when "101" => Q_ALU_OP      <= ALU_ASR;
380              when "110" => Q_ALU_OP      <= ALU_LSR;
381              when "111" => Q_ALU_OP      <= ALU_ROR;
382              when others =>
383                  end case;
384          Q_WE_D      <= "01";
385          Q_WE_F      <= '1';
386      else
387          case I_OPC(2 downto 0) is
388              when "000" =>
389                  if (I_OPC(8)) = '0' then
390                      --
391                      -- 1001 0100 0sss 1000 - BSET
392                      -- 1001 0100 1sss 1000 - BCLR
393                      --
394                      Q_BIT(3 downto 0)      <= I_OPC(7 downto 4);
395                      Q_ALU_OP      <= ALU_SREG;
396                      Q_WE_F      <= '1';
397                  else
398                      --
399                      -- 1001 0101 0000 1000 - RET
400                      -- 1001 0101 0001 1000 - RETI
401                      -- 1001 0101 1000 1000 - SLEEP
402                      -- 1001 0101 1001 1000 - BREAK
403                      -- 1001 0101 1100 1000 - LPM      [ R0, (Z) ]
404                      -- 1001 0101 1101 1000 - ELPM     not mega8
405                      -- 1001 0101 1110 1000 - SPM
406                      -- 1001 0101 1111 1000 - SPM #2
407                      -- 1001 0101 1010 1000 - WDR
408                      --
409                      case I_OPC(7 downto 4) is
410                          when "0000" => -- RET
411                              Q_AMOD      <= AMOD_SPii;
412                              if (I_T0 = '1') then
413                                  Q_RD_M      <= '1';
414                              else
415                                  Q_PC_OP      <= PC_LD_S;
416                                  Q_WE_XYZS    <= not I_T0;
417                              end if;
418
419                          when "0001" => -- RETI
420                              Q_ALU_OP      <= ALU_INTR;
421                              Q_IMM(6)      <= '1';
422                              Q_AMOD      <= AMOD_SPii;
423                              if (I_T0 = '1') then
424                                  Q_RD_M      <= '1';
425                              else
426                                  Q_PC_OP      <= PC_LD_S;
427                                  Q_WE_XYZS    <= not I_T0;
428                              end if;
429
430                          when "1000" => -- (i) LPM R0, (Z)

```

18 Listing of opc_deco.vhd

```

431                               Q_DDDDD      <= "00000";
432                               Q_AMOD       <= AMOD_Z;
433                               Q_PMS        <= '1';
434                               Q_WE_D       <= '0' & not I_TO;
435
436                               when "1110" => -- SPM
437                               Q_DDDDD      <= "00000";
438                               Q_AMOD       <= AMOD_Z;
439                               Q_PMS        <= '1';
440                               Q_WE_M       <= "01";
441
442                               when "1111" => -- SPM #2
443                               -- page write: not supported
444
445                               when others =>
446                               end case;
447                               end if;
448
449                               when "001"  =>
450                               --
451                               -- 1001 0100 0000 1001 IJMP
452                               -- 1001 0100 0001 1001 EIJMP  -- not mega8
453                               -- 1001 0101 0000 1001 ICALL
454                               -- 1001 0101 0001 1001 EICALL -- not mega8
455                               --
456                               Q_PC_OP      <= PC_LD_Z;
457                               if (I_OPC(8) = '1') then          -- ICALL
458                               Q_ALU_OP     <= ALU_PC_1;
459                               Q_AMOD       <= AMOD_ddSP;
460                               Q_WE_M       <= "11";
461                               Q_WE_XYZS    <= '1';
462                               end if;
463
464                               when "010"  =>
465                               --
466                               -- 1001 010d dddd 1010 - DEC
467                               --
468                               Q_ALU_OP      <= ALU_DEC;
469                               Q_WE_D       <= "01";
470                               Q_WE_F       <= '1';
471
472                               when "011"  =>
473                               --
474                               -- 1001 0100 KKKK 1011 - DES  -- not mega8
475                               --
476
477                               when "100" | "101" =>
478                               --
479                               -- 1001 010k kkkk 110k - JMP (k = 0 for 16 bit)
480                               -- kkkk kkkk kkkk kkkk
481                               --
482                               Q_PC_OP      <= PC_LD_I;
483
484                               when "110" | "111" =>
485                               --
486                               -- 1001 010k kkkk 111k - CALL (k = 0)
487                               -- kkkk kkkk kkkk kkkk
488                               --
489                               Q_ALU_OP      <= ALU_PC_2;
490                               Q_AMOD       <= AMOD_ddSP;
491                               Q_PC_OP      <= PC_LD_I;
492                               Q_WE_M       <= "11";      -- both PC bytes

```

18 Listing of opc_deco.vhd

```

493                               Q_WE_XYZS      <= '1';
494
495                               when others =>
496                               end case;
497                               end if;
498                               else
499                               --
500                               -- 1001 0110 KKdd KKKK - ADIW
501                               -- 1001 0111 KKdd KKKK - SBIW
502                               --
503                               if (I_OPC(8) = '0') then      Q_ALU_OP      <= ALU_ADIW;
504                               else                          Q_ALU_OP      <= ALU_SBIW;
505                               end if;
506                               Q_IMM(5 downto 4)      <= I_OPC(7 downto 6);
507                               Q_IMM(3 downto 0)      <= I_OPC(3 downto 0);
508                               Q_RSEL      <= RS_IMM;
509                               Q_DDDDD     <= "11" & I_OPC(5 downto 4) & "0";
510
511                               Q_WE_D      <= "11";
512                               Q_WE_F      <= '1';
513                               end if; -- I_OPC(9) = 0/1
514
515                               when "100110" =>
516                               --
517                               -- 1001 1000 AAAA Abbb - CBI
518                               -- 1001 1001 AAAA Abbb - SBIC
519                               -- 1001 1010 AAAA Abbb - SBI
520                               -- 1001 1011 AAAA Abbb - SBIS
521                               --
522                               Q_ALU_OP      <= ALU_BIT_CS;
523                               Q_AMOD      <= AMOD_ABS;
524                               Q_BIT(3)     <= I_OPC(9);    -- set/clear
525
526                               -- IMM = AAAAAA + 0x20
527                               --
528                               Q_IMM(4 downto 0)      <= I_OPC(7 downto 3);
529                               Q_IMM(6 downto 5)      <= "01";
530
531                               Q_RD_M      <= I_T0;
532                               if ((I_OPC(8) = '0') ) then      -- CBI or SBI
533                               Q_WE_M(0)      <= '1';
534                               else                      -- SBIC or SBIS
535                               if (I_T0 = '0') then      -- second cycle.
536                               Q_PC_OP      <= PC_SKIP_T;
537                               end if;
538                               end if;
539
540                               when "100111" => -- MUL
541                               --
542                               -- 1001 11rd dddd rrrr - MUL
543                               --
544                               Q_ALU_OP      <= ALU_MULT;
545                               Q_IMM(7 downto 5)      <= "000"; -- -MUL UU;
546                               Q_WE_01      <= '1';
547                               Q_WE_F      <= '1';
548
549                               when "101100" | "101101" =>
550                               --
551                               -- 1011 0AAd dddd AAAA - IN
552                               --
553                               Q_RSEL      <= RS_DIN;
554                               Q_AMOD      <= AMOD_ABS;

```

18 Listing of opc_deco.vhd

```

555
556      -- IMM = AAAAAA
557      -- + 010000 (0x20)
558      Q_IMM(3 downto 0)      <= I_OPCODE(3 downto 0);
559      Q_IMM(4)            <= I_OPCODE(9);
560      Q_IMM(6 downto 5)      <= "01" + ('0' & I_OPCODE(10 downto 10));
561
562      Q_WE_D            <= "01";
563
564      when "101110" | "101111" =>
565          --
566          -- 1011 1AAr rrrr AAAA - OUT
567          --
568          Q_ALU_OP        <= ALU_D_MV_Q;
569          Q_AMOD         <= AMOD_ABS;
570
571          -- IMM = AAAAAA
572          -- + 010000 (0x20)
573          --
574          Q_IMM(3 downto 0)      <= I_OPCODE(3 downto 0);
575          Q_IMM(4)            <= I_OPCODE(9);
576          Q_IMM(6 downto 5)      <= "01" + ('0' & I_OPCODE(10 downto 10));
577          Q_WE_M            <= "01";
578
579      when "110000" | "110001" | "110010" | "110011" =>
580          --
581          -- 1100 kkkk kkkk kkkk - RJMP
582          --
583          Q_JADR        <= I_PC + (I_OPCODE(11) & I_OPCODE(11) & I_OPCODE(11) & I_OPCODE(11)
584                      & I_OPCODE(11 downto 0)) + X"0001";
585          Q_PC_OP        <= PC_LD_I;
586
587      when "110100" | "110101" | "110110" | "110111" =>
588          --
589          -- 1101 kkkk kkkk kkkk - RCALL
590          --
591          Q_JADR        <= I_PC + (I_OPCODE(11) & I_OPCODE(11) & I_OPCODE(11) & I_OPCODE(11)
592                      & I_OPCODE(11 downto 0)) + X"0001";
593          Q_ALU_OP        <= ALU_PC_1;
594          Q_AMOD         <= AMOD_ddSP;
595          Q_PC_OP        <= PC_LD_I;
596          Q_WE_M            <= "11";      -- both PC bytes
597          Q_WE_XYZS       <= '1';
598
599      when "111000" | "111001" | "111010" | "111011" => -- LDI
600          --
601          -- 1110 KKKK dddd KKKK - LDI Rd, K
602          --
603          Q_ALU_OP        <= ALU_R_MV_Q;
604          Q_RSEL         <= RS_IMM;
605          Q_DDDDD        <= '1' & I_OPCODE(7 downto 4);      -- 16..31
606          Q_IMM(7 downto 0)      <= I_OPCODE(11 downto 8) & I_OPCODE(3 downto 0);
607          Q_WE_D            <= "01";
608
609      when "111100" | "111101" =>
610          --
611          -- 1111 00kk kkkk kbbb - BRBS
612          -- 1111 01kk kkkk kbbb - BRBC
613          --      v
614          -- bbb: status register bit
615          -- v: value (set/cleared) of status register bit
616          --

```

18 Listing of opc_deco.vhd

```
617          Q_JADR      <= I_PC + (I_OPCODE(9) & I_OPCODE(9) & I_OPCODE(9) & I_OPCODE(9)
618                                & I_OPCODE(9) & I_OPCODE(9) & I_OPCODE(9) & I_OPCODE(9)
619                                & I_OPCODE(9) & I_OPCODE(9 downto 3)) + X"0001";
620          Q_PC_OP     <= PC_BCC;
621
622      when "111110" =>
623          --
624          -- 1111 100d dddd 0bbb - BLD
625          -- 1111 101d dddd 0bbb - BST
626          --
627          if I_OPCODE(9) = '0' then    -- BLD: T flag to register
628              Q_ALU_OP      <= ALU_BLD;
629              Q_WE_D        <= "01";
630          else                      -- BST: register to T flag
631              Q_AMOD        <= AMOD_ABS;
632              Q_BIT(3)       <= I_OPCODE(10);
633              Q_IMM(4 downto 0) <= I_OPCODE(8 downto 4);
634              Q_ALU_OP      <= ALU_BIT_CS;
635              Q_WE_F        <= '1';
636          end if;
637
638      when "111111" =>
639          --
640          -- 1111 110r rrrr 0bbb - SBRC
641          -- 1111 111r rrrr 0bbb - SBRS
642          --
643          -- like SBIC, but and general purpose regs instead of I/O regs.
644          --
645          Q_ALU_OP      <= ALU_BIT_CS;
646          Q_AMOD        <= AMOD_ABS;
647          Q_BIT(3)       <= I_OPCODE(9);    -- set/clear bit
648          Q_IMM(4 downto 0) <= I_OPCODE(8 downto 4);
649          if (I_T0 = '0') then
650              Q_PC_OP      <= PC_SKIP_T;
651          end if;
652
653      when others =>
654  end case;
655 end if;
656 end process;
657
658 end Behavioral;
659
```

src/opc_deco.vhd

19 LISTING OF opc_fetch.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      opc_fetch - Behavioral  
23 -- Create Date:     13:00:44 10/30/2009  
24 -- Description:    the opcode fetch stage of a CPU.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.std_logic_1164.ALL;  
30 use IEEE.std_logic_ARITH.ALL;  
31 use IEEE.std_logic_UNSIGNED.ALL;  
32  
33 entity opc_fetch is  
34     port (  I_CLK          : in  std_logic;  
35             I_CLR          : in  std_logic;  
36             I_INTVEC       : in  std_logic_vector( 5 downto 0);  
37             I_LOAD_PC      : in  std_logic;  
38             I_NEW_PC       : in  std_logic_vector(15 downto 0);  
39             I_PM_ADR       : in  std_logic_vector(11 downto 0);  
40             I_SKIP         : in  std_logic;  
41  
42             Q_OPC          : out std_logic_vector(31 downto 0);  
43             Q_PC           : out std_logic_vector(15 downto 0);  
44             Q_PM_DOUT      : out std_logic_vector( 7 downto 0);  
45             Q_T0           : out std_logic);  
46 end opc_fetch;  
47  
48  
49 architecture Behavioral of opc_fetch is  
50  
51 component prog_mem  
52     port (  I_CLK          : in  std_logic;  
53             I_WAIT         : in  std_logic;  
54             I_PC           : in  std_logic_vector(15 downto 0);  
55             I_PM_ADR       : in  std_logic_vector(11 downto 0);  
56  
57             Q_OPC          : out std_logic_vector(31 downto 0);  
58
```

19 LISTING OF opc_fetch.vhd

```

59          Q_PC      : out std_logic_vector (15 downto 0);
60          Q_PM_DOUT : out std_logic_vector ( 7 downto 0));
61      end component;
62
63      signal P_OPC       : std_logic_vector(31 downto 0);
64      signal P_PC        : std_logic_vector(15 downto 0);
65
66      signal L_INVALIDATE : std_logic;
67      signal L_LONG_OP    : std_logic;
68      signal L_NEXT_PC   : std_logic_vector(15 downto 0);
69      signal L_PC         : std_logic_vector(15 downto 0);
70      signal L_T0          : std_logic;
71      signal L_WAIT        : std_logic;
72
73  begin
74
75      pmem : prog_mem
76      port map(   I_CLK      => I_CLK,
77
78                  I_WAIT     => L_WAIT,
79                  I_PC       => L_NEXT_PC,
80                  I_PM_ADDR  => I_PM_ADDR,
81
82                  Q_OPC      => P_OPC,
83                  Q_PC       => P_PC,
84                  Q_PM_DOUT  => Q_PM_DOUT);
85
86  lpc: process(I_CLK)
87  begin
88      if (rising_edge(I_CLK)) then
89          L_PC      <= L_NEXT_PC;
90          L_T0      <= not L_WAIT;
91      end if;
92  end process;
93
94      L_NEXT_PC      <= X"0000"      when (I_CLR      = '1')
95      else L_PC       when (L_WAIT      = '1')
96      else I_NEW_PC   when (I_LOAD_PC = '1')
97      else L_PC + X"0002" when (L_LONG_OP = '1')
98      else L_PC + X"0001";
99
100     -- Two word opcodes:
101     --
102     --      9      3210
103     -- 1001 000d dddd 0000 kkkk kkkk kkkk kkkk - LDS
104     -- 1001 001d dddd 0000 kkkk kkkk kkkk kkkk - SDS
105     -- 1001 010k kkkk 110k kkkk kkkk kkkk kkkk - JMP
106     -- 1001 010k kkkk 111k kkkk kkkk kkkk kkkk - CALL
107     --
108     L_LONG_OP      <= '1' when (((P_OPC(15 downto 9) = "1001010") and
109                               (P_OPC( 3 downto 2) = "11"))           -- JMP, CALL
110                               or ((P_OPC(15 downto 10) = "100100") and
111                               (P_OPC( 3 downto 0) = "0000"))))    -- LDS, STS
112     else '0';
113
114     -- Two cycle opcodes:
115     --
116     -- 1001 000d dddd .... - LDS etc.
117     -- 1001 0101 0000 1000 - RET
118     -- 1001 0101 0001 1000 - RETI
119     -- 1001 1001 AAAA Abbb - SBIC
120     -- 1001 1011 AAAA Abbb - SBIS

```

19 LISTING OF opc_fetch.vhd

```
121      -- 1111 110r rrrr 0bbb - SBRC
122      -- 1111 111r rrrr 0bbb - SBRS
123      --
124      L_WAIT      <= '0'  when (L_INVALIDATE = '1')
125          else '0'  when (I_INTVEC(5)  = '1')
126              else L_T0 when ((P_OPC(15 downto    9) = "1001000" )      -- LDS etc.
127                           or  (P_OPC(15 downto    8) = "10010101")      -- RET etc.
128                           or  ((P_OPC(15 downto 10) = "100110")        -- SBIC, SBIS
129                               and P_OPC(8) = '1')
130                           or  (P_OPC(15 downto 10) = "111111"))      -- SBRC, SBRS
131          else  '0';
132
133      L_INVALIDATE      <= I_CLR or I_SKIP;
134
135      Q_OPC      <= X"00000000" when (L_INVALIDATE = '1')
136          else P_OPC      when (I_INTVEC(5) = '0')
137          else (X"000000" & "00" & I_INTVEC);      -- "interrupt opcode"
138
139      Q_PC       <= P_PC;
140      Q_T0       <= L_T0;
141
142  end Behavioral;
143
```

src/opc_fetch.vhd

20 LISTING OF prog_mem_content.vhd

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.all;
3
4 package prog_mem_content is
5
6     -- content of pe_0 -----
7     constant pe_0_00 : BIT_VECTOR := X"F180C8135798FC118181E0CA1010905100EF1D2C5F8CCCCCCCCCCCC
8     constant pe_0_01 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
9     constant pe_0_02 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
10    constant pe_0_03 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
11    constant pe_0_04 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
12    constant pe_0_05 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
13    constant pe_0_06 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
14    constant pe_0_07 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
15    constant pe_0_08 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
16    constant pe_0_09 : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
17    constant pe_0_0A : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
18    constant pe_0_0B : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
19    constant pe_0_0C : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
20    constant pe_0_0D : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
21    constant pe_0_0E : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
22    constant pe_0_0F : BIT_VECTOR := X"FFFFFFFFFFFFFFF3E5864BEFF1194EEcff8514CE38
23
24    -- content of pe_1 -----
25    constant pe_1_00 : BIT_VECTOR := X"3F930800000088842808F0CBEA0ADA0FB1DC1072644000000000000
26    constant pe_1_01 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
27    constant pe_1_02 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
28    constant pe_1_03 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
29    constant pe_1_04 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
30    constant pe_1_05 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
31    constant pe_1_06 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
32    constant pe_1_07 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
33    constant pe_1_08 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
34    constant pe_1_09 : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
35    constant pe_1_0A : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
36    constant pe_1_0B : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
37    constant pe_1_0C : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
38    constant pe_1_0D : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
39    constant pe_1_0E : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
40    constant pe_1_0F : BIT_VECTOR := X"FFFFFFFFFFFFFFFAC9CBC0DC0C0DC8F0ED109C2FF00
41
42    -- content of pe_2 -----
43    constant pe_2_00 : BIT_VECTOR := X"F7100B00000044404050F0007606760000F54AC0C05444444444444
44    constant pe_2_01 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
45    constant pe_2_02 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
46    constant pe_2_03 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
47    constant pe_2_04 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
48    constant pe_2_05 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
49    constant pe_2_06 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
50    constant pe_2_07 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
51    constant pe_2_08 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
52    constant pe_2_09 : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
53    constant pe_2_0A : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
54    constant pe_2_0B : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
55    constant pe_2_0C : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
56    constant pe_2_0D : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
57    constant pe_2_0E : BIT_VECTOR := X"FFFFFFFFFFFFFFF0101B55F5117B71141335B711F05
```

20 LISTING OF prog_mem_content.vhd

20 LISTING OF prog_mem_content.vhd

src/prog_mem_content.vhd

21 LISTING OF prog_mem.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      prog_mem - Behavioral  
23 -- Create Date:     14:09:04 10/30/2009  
24 -- Description:    the program memory of a CPU.  
25 --  
26 -----  
27 library IEEE;  
28 use IEEE.STD_LOGIC_1164.ALL;  
29 use IEEE.STD_LOGIC_ARITH.ALL;  
30 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
31  
32 -- the content of the program memory.  
33 --  
34 use work.prog_mem_content.all;  
35  
36 entity prog_mem is  
37     port (  I_CLK          : in  std_logic;  
38             I_WAIT         : in  std_logic;  
39             I_PC           : in  std_logic_vector(15 downto 0); -- word address  
40             I_PM_ADR       : in  std_logic_vector(11 downto 0); -- byte address  
41             Q_OPC          : out std_logic_vector(31 downto 0);  
42             Q_PC           : out std_logic_vector(15 downto 0);  
43             Q_PM_DOUT      : out std_logic_vector( 7 downto 0));  
44 end prog_mem;  
45  
46  
47 architecture Behavioral of prog_mem is  
48  
49 constant zero_256 : bit_vector := X"00000000000000000000000000000000"  
50                                         & X"00000000000000000000000000000000";  
51  
52  
53 component RAMB4_S4_S4  
54     generic(INIT_00 : bit_vector := zero_256;  
55                 INIT_01 : bit_vector := zero_256;  
56                 INIT_02 : bit_vector := zero_256;  
57                 INIT_03 : bit_vector := zero_256;  
58                 INIT_04 : bit_vector := zero_256;
```

21 LISTING OF prog_mem.vhd

```

59      INIT_05 : bit_vector := zero_256;
60      INIT_06 : bit_vector := zero_256;
61      INIT_07 : bit_vector := zero_256;
62      INIT_08 : bit_vector := zero_256;
63      INIT_09 : bit_vector := zero_256;
64      INIT_0A : bit_vector := zero_256;
65      INIT_0B : bit_vector := zero_256;
66      INIT_0C : bit_vector := zero_256;
67      INIT_0D : bit_vector := zero_256;
68      INIT_0E : bit_vector := zero_256;
69      INIT_0F : bit_vector := zero_256);
70
71      port (
72          ADDRA    : in  std_logic_vector(9 downto 0);
73          ADDRDB   : in  std_logic_vector(9 downto 0);
74          CLKA     : in  std_ulogic;
75          CLKB     : in  std_ulogic;
76          DIA      : in  std_logic_vector(3 downto 0);
77          DIB      : in  std_logic_vector(3 downto 0);
78          ENA      : in  std_ulogic;
79          ENB      : in  std_ulogic;
80          RSTA     : in  std_ulogic;
81          RSTB     : in  std_ulogic;
82          WEA      : in  std_ulogic;
83          WEB      : in  std_ulogic;
84          DOA      : out std_logic_vector(3 downto 0);
85          DOB      : out std_logic_vector(3 downto 0));
86      end component;
87
88      signal M_OPC_E      : std_logic_vector(15 downto 0);
89      signal M_OPC_O      : std_logic_vector(15 downto 0);
90      signal M_PMD_E      : std_logic_vector(15 downto 0);
91      signal M_PMD_O      : std_logic_vector(15 downto 0);
92
93      signal L_WAIT_N     : std_logic;
94      signal L_PC_0        : std_logic;
95      signal L_PC_E        : std_logic_vector(10 downto 1);
96      signal L_PC_O        : std_logic_vector(10 downto 1);
97      signal L_PMD         : std_logic_vector(15 downto 0);
98      signal L_PM_ADR_1_0  : std_logic_vector( 1 downto 0);
99
100     begin
101
102         pe_0 : RAMB4_S4_S4 -----
103             generic map(INIT_00 => pe_0_00, INIT_01 => pe_0_01, INIT_02 => pe_0_02,
104                         INIT_03 => pe_0_03, INIT_04 => pe_0_04, INIT_05 => pe_0_05,
105                         INIT_06 => pe_0_06, INIT_07 => pe_0_07, INIT_08 => pe_0_08,
106                         INIT_09 => pe_0_09, INIT_0A => pe_0_0A, INIT_0B => pe_0_0B,
107                         INIT_0C => pe_0_0C, INIT_0D => pe_0_0D, INIT_0E => pe_0_0E,
108                         INIT_0F => pe_0_0F)
109             port map(ADDRA => L_PC_E,                                     ADDRDB => I_PM_ADR(11 downto 2),
110                     CLKA   => I_CLK,                                     CLKB   => I_CLK,
111                     DIA    => "0000",                                    DIB    => "0000",
112                     ENA    => L_WAIT_N,                                 ENB    => '1',
113                     RSTA   => '0',                                     RSTB   => '0',
114                     WEA    => '0',                                     WEB    => '0',
115                     DOA    => M_OPC_E(3 downto 0),                   DOB    => M_PMD_E(3 downto 0));
116
117         pe_1 : RAMB4_S4_S4 -----
118             generic map(INIT_00 => pe_1_00, INIT_01 => pe_1_01, INIT_02 => pe_1_02,
119                         INIT_03 => pe_1_03, INIT_04 => pe_1_04, INIT_05 => pe_1_05,
120                         INIT_06 => pe_1_06, INIT_07 => pe_1_07, INIT_08 => pe_1_08,

```

21 LISTING OF prog_mem.vhd

```

121           INIT_09 => pe_1_09, INIT_0A => pe_1_0A, INIT_0B => pe_1_0B,
122           INIT_0C => pe_1_0C, INIT_0D => pe_1_0D, INIT_0E => pe_1_0E,
123           INIT_0F => pe_1_0F)
124   port map (ADDRA => L_PC_E,                                     ADDRDB => I_PM_ADR(11 downto 2),
125             CLKA  => I_CLK,                                         CLKB  => I_CLK,
126             DIA   => "0000",                                         DIB   => "0000",
127             ENA   => L_WAIT_N,                                       ENB   => '1',
128             RSTA  => '0',                                           RSTB  => '0',
129             WEA   => '0',                                           WEB   => '0',
130             DOA   => M_OPC_E(7 downto 4),                           DOB   => M_PMD_E(7 downto 4));
131
132   pe_2 : RAMB4_S4_S4 -----
133   generic map (INIT_00 => pe_2_00, INIT_01 => pe_2_01, INIT_02 => pe_2_02,
134                 INIT_03 => pe_2_03, INIT_04 => pe_2_04, INIT_05 => pe_2_05,
135                 INIT_06 => pe_2_06, INIT_07 => pe_2_07, INIT_08 => pe_2_08,
136                 INIT_09 => pe_2_09, INIT_0A => pe_2_0A, INIT_0B => pe_2_0B,
137                 INIT_0C => pe_2_0C, INIT_0D => pe_2_0D, INIT_0E => pe_2_0E,
138                 INIT_0F => pe_2_0F)
139   port map (ADDRA => L_PC_E,                                     ADDRDB => I_PM_ADR(11 downto 2),
140             CLKA  => I_CLK,                                         CLKB  => I_CLK,
141             DIA   => "0000",                                         DIB   => "0000",
142             ENA   => L_WAIT_N,                                       ENB   => '1',
143             RSTA  => '0',                                           RSTB  => '0',
144             WEA   => '0',                                           WEB   => '0',
145             DOA   => M_OPC_E(11 downto 8),                           DOB   => M_PMD_E(11 downto 8));
146
147   pe_3 : RAMB4_S4_S4 -----
148   generic map (INIT_00 => pe_3_00, INIT_01 => pe_3_01, INIT_02 => pe_3_02,
149                 INIT_03 => pe_3_03, INIT_04 => pe_3_04, INIT_05 => pe_3_05,
150                 INIT_06 => pe_3_06, INIT_07 => pe_3_07, INIT_08 => pe_3_08,
151                 INIT_09 => pe_3_09, INIT_0A => pe_3_0A, INIT_0B => pe_3_0B,
152                 INIT_0C => pe_3_0C, INIT_0D => pe_3_0D, INIT_0E => pe_3_0E,
153                 INIT_0F => pe_3_0F)
154   port map (ADDRA => L_PC_E,                                     ADDRDB => I_PM_ADR(11 downto 2),
155             CLKA  => I_CLK,                                         CLKB  => I_CLK,
156             DIA   => "0000",                                         DIB   => "0000",
157             ENA   => L_WAIT_N,                                       ENB   => '1',
158             RSTA  => '0',                                           RSTB  => '0',
159             WEA   => '0',                                           WEB   => '0',
160             DOA   => M_OPC_E(15 downto 12),                           DOB   => M_PMD_E(15 downto 12));
161
162   po_0 : RAMB4_S4_S4 -----
163   generic map (INIT_00 => po_0_00, INIT_01 => po_0_01, INIT_02 => po_0_02,
164                 INIT_03 => po_0_03, INIT_04 => po_0_04, INIT_05 => po_0_05,
165                 INIT_06 => po_0_06, INIT_07 => po_0_07, INIT_08 => po_0_08,
166                 INIT_09 => po_0_09, INIT_0A => po_0_0A, INIT_0B => po_0_0B,
167                 INIT_0C => po_0_0C, INIT_0D => po_0_0D, INIT_0E => po_0_0E,
168                 INIT_0F => po_0_0F)
169   port map (ADDRA => L_PC_O,                                     ADDRDB => I_PM_ADR(11 downto 2),
170             CLKA  => I_CLK,                                         CLKB  => I_CLK,
171             DIA   => "0000",                                         DIB   => "0000",
172             ENA   => L_WAIT_N,                                       ENB   => '1',
173             RSTA  => '0',                                           RSTB  => '0',
174             WEA   => '0',                                           WEB   => '0',
175             DOA   => M_OPC_O(3 downto 0),                           DOB   => M_PMD_O(3 downto 0));
176
177   po_1 : RAMB4_S4_S4 -----
178   generic map (INIT_00 => po_1_00, INIT_01 => po_1_01, INIT_02 => po_1_02,
179                 INIT_03 => po_1_03, INIT_04 => po_1_04, INIT_05 => po_1_05,
180                 INIT_06 => po_1_06, INIT_07 => po_1_07, INIT_08 => po_1_08,
181                 INIT_09 => po_1_09, INIT_0A => po_1_0A, INIT_0B => po_1_0B,
182                 INIT_0C => po_1_0C, INIT_0D => po_1_0D, INIT_0E => po_1_0E,

```

21 LISTING OF prog_mem.vhd

```

183          INIT_0F => po_1_0F)
184  port map (ADDRA => L_PC_O,
185              CLKA   => I_CLK,
186              DIA    => "0000",
187              ENA    => L_WAIT_N,
188              RSTA   => '0',
189              WEA    => '0',
190              DOA    => M_OPC_O(7 downto 4),
191
192      po_2 : RAMB4_S4_S4 -----
193  generic map (INIT_00 => po_2_00, INIT_01 => po_2_01, INIT_02 => po_2_02,
194                INIT_03 => po_2_03, INIT_04 => po_2_04, INIT_05 => po_2_05,
195                INIT_06 => po_2_06, INIT_07 => po_2_07, INIT_08 => po_2_08,
196                INIT_09 => po_2_09, INIT_0A => po_2_0A, INIT_0B => po_2_0B,
197                INIT_0C => po_2_0C, INIT_0D => po_2_0D, INIT_0E => po_2_0E,
198                INIT_0F => po_2_0F)
199  port map (ADDRA => L_PC_O,
200              CLKA   => I_CLK,
201              DIA    => "0000",
202              ENA    => L_WAIT_N,
203              RSTA   => '0',
204              WEA    => '0',
205              DOA    => M_OPC_O(11 downto 8),
206
207      po_3 : RAMB4_S4_S4 -----
208  generic map (INIT_00 => po_3_00, INIT_01 => po_3_01, INIT_02 => po_3_02,
209                INIT_03 => po_3_03, INIT_04 => po_3_04, INIT_05 => po_3_05,
210                INIT_06 => po_3_06, INIT_07 => po_3_07, INIT_08 => po_3_08,
211                INIT_09 => po_3_09, INIT_0A => po_3_0A, INIT_0B => po_3_0B,
212                INIT_0C => po_3_0C, INIT_0D => po_3_0D, INIT_0E => po_3_0E,
213                INIT_0F => po_3_0F)
214  port map (ADDRA => L_PC_O,
215              CLKA   => I_CLK,
216              DIA    => "0000",
217              ENA    => L_WAIT_N,
218              RSTA   => '0',
219              WEA    => '0',
220              DOA    => M_OPC_O(15 downto 12),
221
222      -- remember I_PC0 and I_PM_ADDR for the output mux.
223      --
224      pc0: process (I_CLK)
225      begin
226          if (rising_edge(I_CLK)) then
227              Q_PC      <= I_PC;
228              L_PM_ADDR_1_0     <= I_PM_ADDR(1 downto 0);
229              if ((I_WAIT = '0')) then
230                  L_PC_0      <= I_PC(0);
231              end if;
232          end if;
233      end process;
234
235      L_WAIT_N      <= not I_WAIT;
236
237      -- we use two memory blocks _E and _O (even and odd).
238      -- This gives us a quad-port memory so that we can access
239      -- I_PC, I_PC + 1, and PM simultaneously.
240      --
241      -- I_PC and I_PC + 1 are handled by port A of the memory while PM
242      -- is handled by port B.
243      --
244      -- Q_OPC(15 ... 0) shall contain the word addressed by I_PC, while

```

21 LISTING OF prog_mem.vhd

```
245      -- Q_OPC(31 ... 16) shall contain the word addressed by I_PC + 1.  
246      --  
247      -- There are two cases:  
248      --  
249      -- case A: I_PC      is even, thus I_PC + 1 is odd  
250      -- case B: I_PC + 1 is odd , thus I_PC is even  
251      --  
252      L_PC_O      <= I_PC(10 downto 1);  
253      L_PC_E      <= I_PC(10 downto 1) + ("000000000" & I_PC(0));  
254      Q_OPC(15 downto 0)      <= M_OPC_E when L_PC_0 = '0' else M_OPC_O;  
255      Q_OPC(31 downto 16)     <= M_OPC_E when L_PC_0 = '1' else M_OPC_O;  
256  
257      L_PMD      <= M_PMD_E           when (L_PM_ADR_1_0(1) = '0') else M_PMD_O;  
258      Q_PM_DOUT    <= L_PMD(7 downto 0) when (L_PM_ADR_1_0(0) = '0')  
259          else L_PMD(15 downto 8);  
260  
261  end Behavioral;  
262
```

src/prog_mem.vhd

22 LISTING OF reg_16.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name: Register - Behavioral  
23 -- Create Date: 12:37:55 10/28/2009  
24 -- Description: a register pair of a CPU.  
25 --  
26 -----  
27 library IEEE;  
28 use IEEE.STD_LOGIC_1164.ALL;  
29 use IEEE.STD_LOGIC_ARITH.ALL;  
30 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
31  
32 entity reg_16 is  
33     port ( I_CLK      : in std_logic;  
34             I_D       : in std_logic_vector (15 downto 0);  
35             I_WE      : in std_logic_vector ( 1 downto 0);  
36             Q        : out std_logic_vector (15 downto 0));  
37 end reg_16;  
38  
39 architecture Behavioral of reg_16 is  
40  
41 signal L           : std_logic_vector (15 downto 0) := X"7777";  
42 begin  
43  
44     process(I_CLK)  
45     begin  
46         if (rising_edge(I_CLK)) then  
47             if (I_WE(1) = '1') then  
48                 L(15 downto 8)      <= I_D(15 downto 8);  
49             end if;  
50             if (I_WE(0) = '1') then  
51                 L( 7 downto 0)      <= I_D( 7 downto 0);  
52             end if;  
53         end if;  
54     end process;  
55  
56     Q      <= L;  
57  
58
```

22 LISTING OF reg_16.vhd

```
59
60      end Behavioral;
61
```

src/reg_16.vhd

23 LISTING OF register_file.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name: RegisterFile - Behavioral  
23 -- Create Date: 12:43:34 10/28/2009  
24 -- Description: a register file (16 register pairs) of a CPU.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 use work.common.ALL;  
34  
35 entity register_file is  
36     port ( I_CLK : in std_logic;  
37             I_AMOD : in std_logic_vector( 5 downto 0);  
38             I_COND : in std_logic_vector( 3 downto 0);  
39             I_DDDDD : in std_logic_vector( 4 downto 0);  
40             I_DIN : in std_logic_vector(15 downto 0);  
41             I_FLAGS : in std_logic_vector( 7 downto 0);  
42             I_IMM : in std_logic_vector(15 downto 0);  
43             I_RRRR : in std_logic_vector( 4 downto 1);  
44             I_WE_01 : in std_logic;  
45             I_WE_D : in std_logic_vector( 1 downto 0);  
46             I_WE_F : in std_logic;  
47             I_WE_M : in std_logic;  
48             I_WE_XYZS : in std_logic;  
49  
50             Q_ADR : out std_logic_vector(15 downto 0);  
51             Q_CC : out std_logic;  
52             Q_D : out std_logic_vector(15 downto 0);  
53             Q_FLAGS : out std_logic_vector( 7 downto 0);  
54             Q_R : out std_logic_vector(15 downto 0);  
55             Q_S : out std_logic_vector( 7 downto 0);  
56             Q_Z : out std_logic_vector(15 downto 0));  
57  
58 end register_file;
```

23 LISTING OF register_file.vhd

```
59
60     architecture Behavioral of register_file is
61
62     component reg_16
63         port ( I_CLK      : in      std_logic;
64                 I_D       : in      std_logic_vector(15 downto 0);
65                 I_WE      : in      std_logic_vector( 1 downto 0);
66
67                 Q        : out     std_logic_vector(15 downto 0));
68     end component;
69
70
71     signal R_R00      : std_logic_vector(15 downto 0);
72     signal R_R02      : std_logic_vector(15 downto 0);
73     signal R_R04      : std_logic_vector(15 downto 0);
74     signal R_R06      : std_logic_vector(15 downto 0);
75     signal R_R08      : std_logic_vector(15 downto 0);
76     signal R_R10      : std_logic_vector(15 downto 0);
77     signal R_R12      : std_logic_vector(15 downto 0);
78     signal R_R14      : std_logic_vector(15 downto 0);
79     signal R_R16      : std_logic_vector(15 downto 0);
80     signal R_R18      : std_logic_vector(15 downto 0);
81     signal R_R20      : std_logic_vector(15 downto 0);
82     signal R_R22      : std_logic_vector(15 downto 0);
83     signal R_R24      : std_logic_vector(15 downto 0);
84     signal R_R26      : std_logic_vector(15 downto 0);
85     signal R_R28      : std_logic_vector(15 downto 0);
86     signal R_R30      : std_logic_vector(15 downto 0);
87     signal R_SP       : std_logic_vector(15 downto 0);      -- stack pointer
88
89     component status_reg is
90         port ( I_CLK      : in      std_logic;
91
92                 I_COND     : in      std_logic_vector ( 3 downto 0);
93                 I_DIN      : in      std_logic_vector ( 7 downto 0);
94                 I_FLAGS    : in      std_logic_vector ( 7 downto 0);
95                 I_WE_F    : in      std_logic;
96                 I_WE_SR   : in      std_logic;
97
98                 Q        : out     std_logic_vector ( 7 downto 0);
99                 Q_CC     : out     std_logic);
100    end component;
101
102    signal S_FLAGS    : std_logic_vector( 7 downto 0);
103
104    signal L_ADDR     : std_logic_vector(15 downto 0);
105    signal L_BASE     : std_logic_vector(15 downto 0);
106    signal L_DDDD     : std_logic_vector( 4 downto 1);
107    signal L_DSP      : std_logic_vector(15 downto 0);
108    signal L_DX       : std_logic_vector(15 downto 0);
109    signal L_DY       : std_logic_vector(15 downto 0);
110    signal L_DZ       : std_logic_vector(15 downto 0);
111    signal L_PRE      : std_logic_vector(15 downto 0);
112    signal L_POST     : std_logic_vector(15 downto 0);
113    signal L_S        : std_logic_vector(15 downto 0);
114    signal L_WE_SP_AMOD: std_logic;
115    signal L_WE       : std_logic_vector(31 downto 0);
116    signal L_WE_A     : std_logic;
117    signal L_WE_D     : std_logic_vector(31 downto 0);
118    signal L_WE_D2    : std_logic_vector( 1 downto 0);
119    signal L_WE_DD    : std_logic_vector(31 downto 0);
120    signal L_WE_IO    : std_logic_vector(31 downto 0);
```

23 LISTING OF register_file.vhd

```

121      signal L_WE_MISC      : std_logic_vector(31 downto 0);
122      signal L_WE_X         : std_logic;
123      signal L_WE_Y         : std_logic;
124      signal L_WE_Z         : std_logic;
125      signal L_WE_SP        : std_logic_vector( 1 downto 0);
126      signal L_WE_SR        : std_logic;
127      signal L_XYZS         : std_logic_vector(15 downto 0);
128
129 begin
130
131     r00: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 1 downto 0), I_D => I_DIN, Q => R
132     r02: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 3 downto 2), I_D => I_DIN, Q => R
133     r04: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 5 downto 4), I_D => I_DIN, Q => R
134     r06: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 7 downto 6), I_D => I_DIN, Q => R
135     r08: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE( 9 downto 8), I_D => I_DIN, Q => R
136     r10: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(11 downto 10), I_D => I_DIN, Q => R
137     r12: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(13 downto 12), I_D => I_DIN, Q => R
138     r14: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(15 downto 14), I_D => I_DIN, Q => R
139     r16: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(17 downto 16), I_D => I_DIN, Q => R
140     r18: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(19 downto 18), I_D => I_DIN, Q => R
141     r20: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(21 downto 20), I_D => I_DIN, Q => R
142     r22: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(23 downto 22), I_D => I_DIN, Q => R
143     r24: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(25 downto 24), I_D => I_DIN, Q => R
144     r26: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(27 downto 26), I_D => L_RX, Q => R
145     r28: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(29 downto 28), I_D => L_DY, Q => R
146     r30: reg_16 port map(I_CLK => I_CLK, I_WE => L_WE(31 downto 30), I_D => L_DZ, Q => R
147     sp:  reg_16 port map(I_CLK => I_CLK, I_WE => L_WE_SP,           I_D => L_DSP, Q => R
148
149 sr: status_reg
150 port map(   I_CLK          => I_CLK,
151              I_COND         => I_COND,
152              I_DIN          => I_DIN(7 downto 0),
153              I_FLAGS         => I_FLAGS,
154              I_WE_F          => I_WE_F,
155              I_WE_SR         => L_WE_SR,
156              Q               => S_FLAGS,
157              Q_CC            => Q_CC);
158
159 -- The output of the register selected by L_ADR.
160 --
161 process(R_R00, R_R02, R_R04, R_R06, R_R08, R_R10, R_R12, R_R14,
162         R_R16, R_R18, R_R20, R_R22, R_R24, R_R26, R_R28, R_R30,
163         R_SP, S_FLAGS, L_ADR(6 downto 1))
164 begin
165     case L_ADR(6 downto 1) is
166         when "000000" => L_S      <= R_R00;
167         when "000001" => L_S      <= R_R02;
168         when "000010" => L_S      <= R_R04;
169         when "000011" => L_S      <= R_R06;
170         when "000100" => L_S      <= R_R08;
171         when "000101" => L_S      <= R_R10;
172         when "000110" => L_S      <= R_R12;
173         when "000111" => L_S      <= R_R14;
174         when "001000" => L_S      <= R_R16;
175         when "001001" => L_S      <= R_R18;
176         when "001010" => L_S      <= R_R20;
177         when "001011" => L_S      <= R_R22;
178         when "001100" => L_S      <= R_R24;
179         when "001101" => L_S      <= R_R26;
180         when "001110" => L_S      <= R_R28;
181         when "001111" => L_S      <= R_R30;
182         when "101111" => L_S      <= R_SP ( 7 downto 0) & X"00";    -- SPL

```

23 LISTING OF register_file.vhd

```

183      when others    => L_S          <= S_FLAGS & R_SP (15 downto 8);    -- SR/SPH
184      end case;
185  end process;
186
187      -- The output of the register pair selected by I_DDDDD.
188      --
189  process(R_R00, R_R02, R_R04, R_R06, R_R08, R_R10, R_R12, R_R14,
190          R_R16, R_R18, R_R20, R_R22, R_R24, R_R26, R_R28, R_R30,
191          I_DDDDD(4 downto 1))
192  begin
193      case I_DDDDD(4 downto 1) is
194          when "0000" => Q_D          <= R_R00;
195          when "0001" => Q_D          <= R_R02;
196          when "0010" => Q_D          <= R_R04;
197          when "0011" => Q_D          <= R_R06;
198          when "0100" => Q_D          <= R_R08;
199          when "0101" => Q_D          <= R_R10;
200          when "0110" => Q_D          <= R_R12;
201          when "0111" => Q_D          <= R_R14;
202          when "1000" => Q_D          <= R_R16;
203          when "1001" => Q_D          <= R_R18;
204          when "1010" => Q_D          <= R_R20;
205          when "1011" => Q_D          <= R_R22;
206          when "1100" => Q_D          <= R_R24;
207          when "1101" => Q_D          <= R_R26;
208          when "1110" => Q_D          <= R_R28;
209          when others => Q_D          <= R_R30;
210      end case;
211  end process;
212
213      -- The output of the register pair selected by I_RRRR.
214      --
215  process(R_R00, R_R02, R_R04, R_R06, R_R08, R_R10, R_R12, R_R14,
216          R_R16, R_R18, R_R20, R_R22, R_R24, R_R26, R_R28, R_R30, I_RRRR)
217  begin
218      case I_RRRR is
219          when "0000" => Q_R          <= R_R00;
220          when "0001" => Q_R          <= R_R02;
221          when "0010" => Q_R          <= R_R04;
222          when "0011" => Q_R          <= R_R06;
223          when "0100" => Q_R          <= R_R08;
224          when "0101" => Q_R          <= R_R10;
225          when "0110" => Q_R          <= R_R12;
226          when "0111" => Q_R          <= R_R14;
227          when "1000" => Q_R          <= R_R16;
228          when "1001" => Q_R          <= R_R18;
229          when "1010" => Q_R          <= R_R20;
230          when "1011" => Q_R          <= R_R22;
231          when "1100" => Q_R          <= R_R24;
232          when "1101" => Q_R          <= R_R26;
233          when "1110" => Q_R          <= R_R28;
234          when others => Q_R          <= R_R30;
235      end case;
236  end process;
237
238      -- the base value of the X/Y/Z/SP register as per I_AMOD.
239      --
240  process(I_AMOD(2 downto 0), I_IMM, R_SP, R_R26, R_R28, R_R30)
241  begin
242      case I_AMOD(2 downto 0) is
243          when AS_SP  => L_BASE        <= R_SP;
244          when AS_Z   => L_BASE        <= R_R30;

```

23 LISTING OF register_file.vhd

```

245      when AS_Y    => L_BASE      <= R_R28;
246      when AS_X    => L_BASE      <= R_R26;
247      when AS_IMM => L_BASE      <= I_IMM;
248      when others => L_BASE      <= X"0000";
249      end case;
250  end process;
251
252  -- the value of the X/Y/Z/SP register after a potential PRE-decrement
253  -- (by 1 or 2) and POST-increment (by 1 or 2).
254  --
255  process(I_AMOD(5 downto 3), I_IMM)
256  begin
257      case I_AMOD(5 downto 3) is
258          when AO_0    => L_PRE      <= X"0000";    L_POST <= X"0000";
259          when AO_i    => L_PRE      <= X"0000";    L_POST <= X"0001";
260          when AO_ii   => L_PRE      <= X"0000";    L_POST <= X"0002";
261          when AO_q    => L_PRE      <= I_IMM;     L_POST <= X"0000";
262          when AO_d    => L_PRE      <= X"FFFF";   L_POST <= X"FFFF";
263          when AO_dd   => L_PRE      <= X"FFFE";   L_POST <= X"FFFE";
264          when others  => L_PRE      <= X"0000";   L_POST <= X"0000";
265      end case;
266  end process;
267
268  L_XYZS      <= L_BASE + L_POST;
269  L_ADR       <= L_BASE + L_PRE;
270
271  L_WE_A       <= I_WE_M when (L_ADR(15 downto 5) = "000000000000") else '0';
272  L_WE_SR      <= I_WE_M when (L_ADR = X"005F") else '0';
273  L_WE_SP_AMOD <= I_WE_XYZS when (I_AMOD(2 downto 0) = AS_SP) else '0';
274  L_WE_SP(1)   <= I_WE_M when (L_ADR = X"005E") else L_WE_SP_AMOD;
275  L_WE_SP(0)   <= I_WE_M when (L_ADR = X"005D") else L_WE_SP_AMOD;
276
277  L_DX         <= L_XYZS when (L_WE_MISC(26) = '1')           else I_DIN;
278  L_DY         <= L_XYZS when (L_WE_MISC(28) = '1')           else I_DIN;
279  L_DZ         <= L_XYZS when (L_WE_MISC(30) = '1')           else I_DIN;
280  L_DSP        <= L_XYZS when (I_AMOD(3 downto 0) = AM_WS) else I_DIN;
281
282  -- the WE signals for the differen registers.
283  --
284  -- case 1: write to an 8-bit register addressed by DDDDD.
285  --
286  -- I_WE_D(0) = '1' and I_DDDDD matches,
287  --
288  L_WE_D( 0)    <= I_WE_D(0) when (I_DDDDD = "00000") else '0';
289  L_WE_D( 1)    <= I_WE_D(0) when (I_DDDDD = "00001") else '0';
290  L_WE_D( 2)    <= I_WE_D(0) when (I_DDDDD = "00010") else '0';
291  L_WE_D( 3)    <= I_WE_D(0) when (I_DDDDD = "00011") else '0';
292  L_WE_D( 4)    <= I_WE_D(0) when (I_DDDDD = "00100") else '0';
293  L_WE_D( 5)    <= I_WE_D(0) when (I_DDDDD = "00101") else '0';
294  L_WE_D( 6)    <= I_WE_D(0) when (I_DDDDD = "00110") else '0';
295  L_WE_D( 7)    <= I_WE_D(0) when (I_DDDDD = "00111") else '0';
296  L_WE_D( 8)    <= I_WE_D(0) when (I_DDDDD = "01000") else '0';
297  L_WE_D( 9)    <= I_WE_D(0) when (I_DDDDD = "01001") else '0';
298  L_WE_D(10)   <= I_WE_D(0) when (I_DDDDD = "01010") else '0';
299  L_WE_D(11)   <= I_WE_D(0) when (I_DDDDD = "01011") else '0';
300  L_WE_D(12)   <= I_WE_D(0) when (I_DDDDD = "01100") else '0';
301  L_WE_D(13)   <= I_WE_D(0) when (I_DDDDD = "01101") else '0';
302  L_WE_D(14)   <= I_WE_D(0) when (I_DDDDD = "01110") else '0';
303  L_WE_D(15)   <= I_WE_D(0) when (I_DDDDD = "01111") else '0';
304  L_WE_D(16)   <= I_WE_D(0) when (I_DDDDD = "10000") else '0';
305  L_WE_D(17)   <= I_WE_D(0) when (I_DDDDD = "10001") else '0';
306  L_WE_D(18)   <= I_WE_D(0) when (I_DDDDD = "10010") else '0';

```

23 LISTING OF register_file.vhd

```

307      L_WE_D(19)      <= I_WE_D(0) when (I_DDDDD = "10011") else '0';
308      L_WE_D(20)      <= I_WE_D(0) when (I_DDDDD = "10100") else '0';
309      L_WE_D(21)      <= I_WE_D(0) when (I_DDDDD = "10101") else '0';
310      L_WE_D(22)      <= I_WE_D(0) when (I_DDDDD = "10110") else '0';
311      L_WE_D(23)      <= I_WE_D(0) when (I_DDDDD = "10111") else '0';
312      L_WE_D(24)      <= I_WE_D(0) when (I_DDDDD = "11000") else '0';
313      L_WE_D(25)      <= I_WE_D(0) when (I_DDDDD = "11001") else '0';
314      L_WE_D(26)      <= I_WE_D(0) when (I_DDDDD = "11010") else '0';
315      L_WE_D(27)      <= I_WE_D(0) when (I_DDDDD = "11011") else '0';
316      L_WE_D(28)      <= I_WE_D(0) when (I_DDDDD = "11100") else '0';
317      L_WE_D(29)      <= I_WE_D(0) when (I_DDDDD = "11101") else '0';
318      L_WE_D(30)      <= I_WE_D(0) when (I_DDDDD = "11110") else '0';
319      L_WE_D(31)      <= I_WE_D(0) when (I_DDDDD = "11111") else '0';
320
321      --
322      -- case 2: write to a 16-bit register pair addressed by DDDD.
323      --
324      -- I_WE_DD(1) = '1' and L_DDDD matches,
325      --
326      L_DDDD      <= I_DDDDD(4 downto 1);
327      L_WE_D2      <= I_WE_D(1) & I_WE_D(1);
328      L_WE_DD( 1 downto 0)      <= L_WE_D2 when (L_DDDD = "0000") else "00";
329      L_WE_DD( 3 downto 2)      <= L_WE_D2 when (L_DDDD = "0001") else "00";
330      L_WE_DD( 5 downto 4)      <= L_WE_D2 when (L_DDDD = "0010") else "00";
331      L_WE_DD( 7 downto 6)      <= L_WE_D2 when (L_DDDD = "0011") else "00";
332      L_WE_DD( 9 downto 8)      <= L_WE_D2 when (L_DDDD = "0100") else "00";
333      L_WE_DD(11 downto 10)     <= L_WE_D2 when (L_DDDD = "0101") else "00";
334      L_WE_DD(13 downto 12)     <= L_WE_D2 when (L_DDDD = "0110") else "00";
335      L_WE_DD(15 downto 14)     <= L_WE_D2 when (L_DDDD = "0111") else "00";
336      L_WE_DD(17 downto 16)     <= L_WE_D2 when (L_DDDD = "1000") else "00";
337      L_WE_DD(19 downto 18)     <= L_WE_D2 when (L_DDDD = "1001") else "00";
338      L_WE_DD(21 downto 20)     <= L_WE_D2 when (L_DDDD = "1010") else "00";
339      L_WE_DD(23 downto 22)     <= L_WE_D2 when (L_DDDD = "1011") else "00";
340      L_WE_DD(25 downto 24)     <= L_WE_D2 when (L_DDDD = "1100") else "00";
341      L_WE_DD(27 downto 26)     <= L_WE_D2 when (L_DDDD = "1101") else "00";
342      L_WE_DD(29 downto 28)     <= L_WE_D2 when (L_DDDD = "1110") else "00";
343      L_WE_DD(31 downto 30)     <= L_WE_D2 when (L_DDDD = "1111") else "00";
344
345      --
346      -- case 3: write to an 8-bit register pair addressed by an I/O address.
347      --
348      -- L_WE_A = '1' and L_ADR(4 downto 0) matches
349      --
350      L_WE_IO( 0)      <= L_WE_A when (L_ADR(4 downto 0) = "00000") else '0';
351      L_WE_IO( 1)      <= L_WE_A when (L_ADR(4 downto 0) = "00001") else '0';
352      L_WE_IO( 2)      <= L_WE_A when (L_ADR(4 downto 0) = "00010") else '0';
353      L_WE_IO( 3)      <= L_WE_A when (L_ADR(4 downto 0) = "00011") else '0';
354      L_WE_IO( 4)      <= L_WE_A when (L_ADR(4 downto 0) = "00100") else '0';
355      L_WE_IO( 5)      <= L_WE_A when (L_ADR(4 downto 0) = "00101") else '0';
356      L_WE_IO( 6)      <= L_WE_A when (L_ADR(4 downto 0) = "00110") else '0';
357      L_WE_IO( 7)      <= L_WE_A when (L_ADR(4 downto 0) = "00111") else '0';
358      L_WE_IO( 8)      <= L_WE_A when (L_ADR(4 downto 0) = "01000") else '0';
359      L_WE_IO( 9)      <= L_WE_A when (L_ADR(4 downto 0) = "01001") else '0';
360      L_WE_IO(10)      <= L_WE_A when (L_ADR(4 downto 0) = "01010") else '0';
361      L_WE_IO(11)      <= L_WE_A when (L_ADR(4 downto 0) = "01011") else '0';
362      L_WE_IO(12)      <= L_WE_A when (L_ADR(4 downto 0) = "01100") else '0';
363      L_WE_IO(13)      <= L_WE_A when (L_ADR(4 downto 0) = "01101") else '0';
364      L_WE_IO(14)      <= L_WE_A when (L_ADR(4 downto 0) = "01110") else '0';
365      L_WE_IO(15)      <= L_WE_A when (L_ADR(4 downto 0) = "01111") else '0';
366      L_WE_IO(16)      <= L_WE_A when (L_ADR(4 downto 0) = "10000") else '0';
367      L_WE_IO(17)      <= L_WE_A when (L_ADR(4 downto 0) = "10001") else '0';
368      L_WE_IO(18)      <= L_WE_A when (L_ADR(4 downto 0) = "10010") else '0';

```

23 LISTING OF register_file.vhd

```

369      L_WE_IO(19)      <= L_WE_A when (L_ADDR(4 downto 0) = "10011") else '0';
370      L_WE_IO(20)      <= L_WE_A when (L_ADDR(4 downto 0) = "10100") else '0';
371      L_WE_IO(21)      <= L_WE_A when (L_ADDR(4 downto 0) = "10101") else '0';
372      L_WE_IO(22)      <= L_WE_A when (L_ADDR(4 downto 0) = "10110") else '0';
373      L_WE_IO(23)      <= L_WE_A when (L_ADDR(4 downto 0) = "10111") else '0';
374      L_WE_IO(24)      <= L_WE_A when (L_ADDR(4 downto 0) = "11000") else '0';
375      L_WE_IO(25)      <= L_WE_A when (L_ADDR(4 downto 0) = "11001") else '0';
376      L_WE_IO(26)      <= L_WE_A when (L_ADDR(4 downto 0) = "11010") else '0';
377      L_WE_IO(27)      <= L_WE_A when (L_ADDR(4 downto 0) = "11011") else '0';
378      L_WE_IO(28)      <= L_WE_A when (L_ADDR(4 downto 0) = "11100") else '0';
379      L_WE_IO(29)      <= L_WE_A when (L_ADDR(4 downto 0) = "11101") else '0';
380      L_WE_IO(30)      <= L_WE_A when (L_ADDR(4 downto 0) = "11110") else '0';
381      L_WE_IO(31)      <= L_WE_A when (L_ADDR(4 downto 0) = "11111") else '0';
382
383      -- case 4 special cases.
384      -- 4a. WE_01 for register pair 0/1 (multiplication opcode).
385      -- 4b. I_WE_XYZS for X (register pairs 26/27) and I_AMOD matches
386      -- 4c. I_WE_XYZS for Y (register pairs 28/29) and I_AMOD matches
387      -- 4d. I_WE_XYZS for Z (register pairs 30/31) and I_AMOD matches
388      --
389      L_WE_X      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WX) else '0';
390      L_WE_Y      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WY) else '0';
391      L_WE_Z      <= I_WE_XYZS when (I_AMOD(3 downto 0) = AM_WZ) else '0';
392      L_WE_MISC   <= L_WE_Z & L_WE_Z &      -- -Z and Z+ address modes r30
393                  L_WE_Y & L_WE_Y &      -- -Y and Y+ address modes r28
394                  L_WE_X & L_WE_X &      -- -X and X+ address modes r26
395                  X"000000" &      -- never                                r24 - r02
396                  I_WE_01 & I_WE_01;    -- multiplication result      r00
397
398      L_WE      <= L_WE_D or L_WE_DD or L_WE_IO or L_WE_MISC;
399
400      Q_S      <= L_S( 7 downto 0) when (L_ADDR(0) = '0') else L_S(15 downto 8);
401      Q_FLAGS  <= S_FLAGS;
402      Q_Z      <= R_R30;
403      Q_ADDR    <= L_ADDR;
404
405  end Behavioral;
406

```

src/register_file.vhd

24 LISTING OF segment7.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      segment7 - Behavioral  
23 -- Create Date:      12:52:16 11/11/2009  
24 -- Description:     a 7 segment LED display interface.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity segment7 is  
34     port ( I_CLK          : in  std_logic;  
35             I_CLR          : in  std_logic;  
36             I_OPC          : in  std_logic_vector(15 downto 0);  
37             I_PC           : in  std_logic_vector(15 downto 0);  
38             Q_7_SEGMENT    : out std_logic_vector( 6 downto 0));  
39  
40 end segment7;  
41  
42 --      Signal      Loc Alt  
43 -----  
44 --      SEG_LED(0)  V3  A  
45 --      SEG_LED(1)  V4  B  
46 --      SEG_LED(2)  W3  C  
47 --      SEG_LED(3)  T4  D  
48 --      SEG_LED(4)  T3  E  
49 --      SEG_LED(5)  U3  F  
50 --      SEG_LED(6)  U4  G  
51  
52  
53 architecture Behavioral of segment7 is  
54  
55 function lmap(VAL: std_logic_vector( 3 downto 0))  
56     return std_logic_vector is  
57 begin  
58     case VAL is  
59         case  
60             0 <= VAL < 10 =>  
61                 return "1111110";  
62             1 <= VAL < 2 =>  
63                 return "1111011";  
64             2 <= VAL < 3 =>  
65                 return "1101111";  
66             3 <= VAL < 4 =>  
67                 return "1110111";  
68             4 <= VAL < 5 =>  
69                 return "0111111";  
70             5 <= VAL < 6 =>  
71                 return "1111001";  
72             6 <= VAL < 7 =>  
73                 return "1110011";  
74             7 <= VAL < 8 =>  
75                 return "1111100";  
76             8 <= VAL < 9 =>  
77                 return "1111111";  
78             9 <= VAL < 10 =>  
79                 return "0111111";  
80             others =>  
81                 return "1111111";  
82         end case;  
83     end case;  
84 end function lmap;  
85  
86 begin  
87     process is  
88         variable VAL: std_logic_vector( 3 downto 0);  
89         variable LED: std_logic_vector( 6 downto 0);  
90     begin  
91         for i in 0 to 9 loop  
92             VAL := i;  
93             LED := lmap(VAL);  
94             Q_7_SEGMENT <= LED;  
95             wait on I_CLK for 1 ns;  
96         end loop;  
97     end process;  
98 end Behavioral;
```

24 LISTING OF segment7.vhd

```

59      when "0000" => return "0111111";    -- 0
60      when "0001" => return "0000110";    -- 1
61      when "0010" => return "1011011";    -- 2
62      when "0011" => return "1001111";    -- 3
63      when "0100" => return "1100110";    -- 4      ----A----      ----0----
64      when "0101" => return "1101101";    -- 5      |      |      |      |
65      when "0110" => return "1111101";    -- 6      F      B      5      1
66      when "0111" => return "0000111";    -- 7      |      |      |      |
67      when "1000" => return "1111111";    -- 8      +---G---+      +---6---+
68      when "1001" => return "1101111";    -- 9      |      |      |      |
69      when "1010" => return "1110111";    -- A      E      C      4      2
70      when "1011" => return "1111100";    -- b      |      |      |      |
71      when "1100" => return "0111001";    -- C      ----D----      ----3----
72      when "1101" => return "1011110";    -- d
73      when "1110" => return "1111001";    -- E
74      when others => return "1110001";    -- F
75  end case;
76 end;
77
78 signal L_CNT      : std_logic_vector(27 downto 0);
79 signal L_OPC       : std_logic_vector(15 downto 0);
80 signal L_PC        : std_logic_vector(15 downto 0);
81 signal L_POS       : std_logic_vector( 3 downto 0);
82
83 begin
84
85 process(I_CLK)      -- 20 MHz
86 begin
87     if (rising_edge(I_CLK)) then
88         if (I_CLR = '1') then
89             L_POS      <= "0000";
90             L_CNT      <= X"0000000";
91             Q_7_SEGMENT      <= "1111111";
92         else
93             L_CNT      <= L_CNT + X"0000001";
94             if (L_CNT = X"0C00000") then
95                 Q_7_SEGMENT      <= "1111111";      -- blank
96             elsif (L_CNT = X"1000000") then
97                 L_CNT      <= X"0000000";
98                 L_POS      <= L_POS + "0001";
99                 case L_POS is
100                     when "0000" => -- blank
101                         Q_7_SEGMENT      <= "1111111";
102                     when "0001" =>
103                         L_PC      <= I_PC;      -- sample PC
104                         L_OPC      <= I_OPC;      -- sample OPC
105                         Q_7_SEGMENT      <= not lmap(L_PC(15 downto 12));
106                     when "0010" =>
107                         Q_7_SEGMENT      <= not lmap(L_PC(11 downto 8));
108                     when "0011" =>
109                         Q_7_SEGMENT      <= not lmap(L_PC( 7 downto 4));
110                     when "0100" =>
111                         Q_7_SEGMENT      <= not lmap(L_PC( 3 downto 0));
112                     when "0101" => -- minus
113                         Q_7_SEGMENT      <= "0111111";
114                     when "0110" =>
115                         Q_7_SEGMENT      <= not lmap(L_OPC(15 downto 12));
116                     when "0111" =>
117                         Q_7_SEGMENT      <= not lmap(L_OPC(11 downto 8));
118                     when "1000" =>
119                         Q_7_SEGMENT      <= not lmap(L_OPC( 7 downto 4));
120                     when "1001" =>

```

24 LISTING OF segment7.vhd

```
121          Q_7_SEGMENT      <= not lmap(L_OPC( 3 downto 0));
122          L_POS           <= "0000";
123          when others =>
124              L_POS           <= "0000";
125          end case;
126          end if;
127      end if;
128      end if;
129  end process;
130
131 end Behavioral;
132
```

src/segment7.vhd

25 LISTING OF status_reg.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name: Register - Behavioral  
23 -- Create Date: 16:15:54 12/26/2009  
24 -- Description: the status register of a CPU.  
25 --  
26 -----  
27 library IEEE;  
28 use IEEE.STD_LOGIC_1164.ALL;  
29 use IEEE.STD_LOGIC_ARITH.ALL;  
30 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
31  
32 entity status_reg is  
33     port ( I_CLK      : in std_logic;  
34             I_COND      : in std_logic_vector ( 3 downto 0);  
35             I_DIN       : in std_logic_vector ( 7 downto 0);  
36             I_FLAGS     : in std_logic_vector ( 7 downto 0);  
37             I_WE_F     : in std_logic;  
38             I_WE_SR    : in std_logic;  
39             Q          : out std_logic_vector ( 7 downto 0);  
40             Q_CC       : out std_logic);  
41 end status_reg;  
42  
43 architecture Behavioral of status_reg is  
44  
45 signal L           : std_logic_vector ( 7 downto 0);  
46 begin  
47  
48     process(I_CLK)  
49     begin  
50         if (rising_edge(I_CLK)) then  
51             if (I_WE_F = '1') then          -- write flags (from ALU)  
52                 L      <= I_FLAGS;  
53             elsif (I_WE_SR = '1') then      -- write I/O  
54                 L      <= I_DIN;  
55             end if;  
56         end if;  
57     end if;
```

25 LISTING OF status_reg.vhd

```
59      end process;
60
61      cond: process(I_COND, L)
62      begin
63          case I_COND(2 downto 0) is
64              when "000" => Q_CC      <= L(0) xor I_COND(3);
65              when "001" => Q_CC      <= L(1) xor I_COND(3);
66              when "010" => Q_CC      <= L(2) xor I_COND(3);
67              when "011" => Q_CC      <= L(3) xor I_COND(3);
68              when "100" => Q_CC      <= L(4) xor I_COND(3);
69              when "101" => Q_CC      <= L(5) xor I_COND(3);
70              when "110" => Q_CC      <= L(6) xor I_COND(3);
71              when others => Q_CC     <= L(7) xor I_COND(3);
72          end case;
73      end process;
74
75      Q      <= L;
76
77  end Behavioral;
78
```

src/status_reg.vhd

26 LISTING OF uart_rx.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Create Date: 14:22:28 11/07/2009  
23 -- Design Name:  
24 -- Module Name: uart_rx - Behavioral  
25 -- Description: a UART receiver.  
26 --  
27 -----  
28 --  
29 library IEEE;  
30 use IEEE.STD_LOGIC_1164.ALL;  
31 use IEEE.STD_LOGIC_ARITH.ALL;  
32 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
33  
34 entity uart_rx is  
35     PORT( I_CLK      : in  std_logic;  
36             I_CLR      : in  std_logic;  
37             I_CE_16    : in  std_logic;          -- 16 times baud rate  
38             I_RX       : in  std_logic;          -- Serial input line  
39             Q_DATA     : out std_logic_vector(7 downto 0);  
40             Q_FLAG     : out std_logic);        -- toggle on every byte received  
41 end uart_rx;  
42  
43 architecture Behavioral of uart_rx is  
44  
45 signal L_POSITION   : std_logic_vector(7 downto 0);      -- sample position  
46 signal L_BUF         : std_logic_vector(9 downto 0);  
47 signal L_FLAG        : std_logic;  
48 signal L_SERIN      : std_logic;                      -- double clock the input  
49 signal L_SER_HOT    : std_logic;                      -- double clock the input  
50  
51 begin  
52  
53     -- double clock the input data...  
54     --  
55     process(I_CLK)  
56     begin  
57         if (rising_edge(I_CLK)) then
```

26 LISTING OF uart_rx.vhd

```

59      if (I_CLR = '1') then
60          L_SERIN      <= '1';
61          L_SER_HOT    <= '1';
62      else
63          L_SERIN      <= I_RX;
64          L_SER_HOT    <= L_SERIN;
65      end if;
66      end if;
67  end process;
68
69  process(I_CLK, L_POSITION)
70  variable START_BIT : boolean;
71  variable STOP_BIT  : boolean;
72  variable STOP_POS  : boolean;
73
74  begin
75      START_BIT := L_POSITION(7 downto 4) = X"0";
76      STOP_BIT  := L_POSITION(7 downto 4) = X"9";
77      STOP_POS  := STOP_BIT and L_POSITION(3 downto 2) = "11"; -- 3/4 of stop bit
78
79      if (rising_edge(I_CLK)) then
80          if (I_CLR = '1') then
81              L_FLAG      <= '0';
82              L_POSITION   <= X"00";      -- idle
83              L_BUF       <= "1111111111";
84              Q_DATA      <= "00000000";
85          elsif (I_CE_16 = '1') then
86              if (L_POSITION = X"00") then           -- uart idle
87                  L_BUF      <= "1111111111";
88                  if (L_SER_HOT = '0') then           -- start bit received
89                      L_POSITION   <= X"01";
90                  end if;
91              else
92                  L_POSITION   <= L_POSITION + X"01";
93                  if (L_POSITION(3 downto 0) = "0111") then      -- 1/2 bit
94                      L_BUF      <= L_SER_HOT & L_BUF(9 downto 1);      -- sample data
95                      --
96                      -- validate start bit
97                      --
98                      if (START_BIT and L_SER_HOT = '1') then      -- 1/2 start bit
99                          L_POSITION   <= X"00";
100                     end if;
101
102                     if (STOP_BIT) then           -- 1/2 stop bit
103                         Q_DATA      <= L_BUF(9 downto 2);
104                     end if;
105                     elsif (STOP_POS) then           -- 3/4 stop bit
106                         L_FLAG      <= L_FLAG xor (L_BUF(9) and not L_BUF(0));
107                         L_POSITION   <= X"00";
108                     end if;
109                     end if;
110                 end if;
111             end if;
112         end process;
113
114     Q_FLAG      <= L_FLAG;
115
116 end Behavioral;
117

```

src/uart_rx.vhd

27 LISTING OF uart_tx.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      uart_tx - Behavioral  
23 -- Create Date:     14:21:59 11/07/2009  
24 -- Description:    a UART receiver.  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity uart_tx is  
34     port(  I_CLK       : in  std_logic;  
35             I_CLR       : in  std_logic;           -- RESET  
36             I_CE_1     : in  std_logic;           -- BAUD rate clock enable  
37             I_DATA     : in  std_logic_vector(7 downto 0);  -- DATA to be sent  
38             I_FLAG     : in  std_logic;           -- toggle to send data  
39             Q_TX       : out std_logic;           -- Serial output line  
40             Q_FLAG     : out std_logic);          -- Transmitting Flag  
41 end uart_tx;  
42  
43 architecture Behavioral of uart_tx is  
44  
45 signal L_BUF          : std_logic_vector(7 downto 0);  
46 signal L_TODO         : std_logic_vector(3 downto 0);      -- bits to send  
47 signal L_FLAG         : std_logic;  
48  
49 begin  
50  
51     process(I_CLK)  
52     begin  
53         if (rising_edge(I_CLK)) then  
54             if (I_CLR = '1') then  
55                 Q_TX      <= '1';  
56                 L_BUF      <= "11111111";  
57                 L_TODO     <= "0000";  
58                 L_FLAG     <= I_FLAG;           -- idle
```

27 LISTING OF uart_tx.vhd

```
59      elsif (I_CE_1 = '1') then
60          if (L_TODO /= "0000") then          -- transmitting
61              Q_TX      <= L_BUF(0);           -- next bit
62              L_BUF      <= '1' & L_BUF(7 downto 1);
63              if (L_TODO = "0001") then
64                  L_FLAG     <= I_FLAG;
65              end if;
66              L_TODO      <= L_TODO - "0001";
67              elsif (L_FLAG /= I_FLAG) then    -- new byte
68                  Q_TX      <= '0';            -- start bit
69                  L_BUF      <= I_DATA;        -- data bits
70                  L_TODO      <= "1001";
71              end if;
72          end if;
73      end if;
74  end process;
75
76  Q_FLAG      <= L_FLAG;
77
78 end Behavioral;
79
```

src/uart_tx.vhd

28 LISTING OF RAMB4_S4_S4.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name:      prog_mem - Behavioral  
23 -- Create Date:     14:09:04 10/30/2009  
24 -- Description:    a block memory module  
25 --  
26 -----  
27  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity RAMB4_S4_S4 is  
34     generic(INIT_00 : bit_vector := X"00000000000000000000000000000000"  
35                             & "00000000000000000000000000000000";  
36         INIT_01 : bit_vector := X"00000000000000000000000000000000"  
37                             & X"00000000000000000000000000000000";  
38         INIT_02 : bit_vector := X"00000000000000000000000000000000"  
39                             & X"00000000000000000000000000000000";  
40         INIT_03 : bit_vector := X"00000000000000000000000000000000"  
41                             & X"00000000000000000000000000000000";  
42         INIT_04 : bit_vector := X"00000000000000000000000000000000"  
43                             & X"00000000000000000000000000000000";  
44         INIT_05 : bit_vector := X"00000000000000000000000000000000"  
45                             & X"00000000000000000000000000000000";  
46         INIT_06 : bit_vector := X"00000000000000000000000000000000"  
47                             & X"00000000000000000000000000000000";  
48         INIT_07 : bit_vector := X"00000000000000000000000000000000"  
49                             & X"00000000000000000000000000000000";  
50         INIT_08 : bit_vector := X"00000000000000000000000000000000"  
51                             & X"00000000000000000000000000000000";  
52         INIT_09 : bit_vector := X"00000000000000000000000000000000"  
53                             & X"00000000000000000000000000000000";  
54         INIT_0A : bit_vector := X"00000000000000000000000000000000"  
55                             & X"00000000000000000000000000000000";  
56         INIT_0B : bit_vector := X"00000000000000000000000000000000"  
57                             & X"00000000000000000000000000000000";  
58         INIT_0C : bit_vector := X"00000000000000000000000000000000"
```

28 LISTING OF RAMB4_S4_S4.vhd

28 LISTING OF RAMB4_S4_S4.vhd

```
121      end if;
122
123      if (rising_edge(CLKB)) then
124          if (ENB = '1') then
125              DOB(3)      <= cv(DATA(conv_integer(ADDRB & "11")));
126              DOB(2)      <= cv(DATA(conv_integer(ADDRB & "10")));
127              DOB(1)      <= cv(DATA(conv_integer(ADDRB & "01")));
128              DOB(0)      <= cv(DATA(conv_integer(ADDRB & "00")));
129          if (WEB = '1') then
130              DATA(conv_integer(ADDRB & "11"))      <= cvl(DIB(3));
131              DATA(conv_integer(ADDRB & "10"))      <= cvl(DIB(2));
132              DATA(conv_integer(ADDRB & "01"))      <= cvl(DIB(1));
133              DATA(conv_integer(ADDRB & "00"))      <= cvl(DIB(0));
134          end if;
135      end if;
136  end process;
137
138 end Behavioral;
139
140
```

test/RAMB4_S4_S4.vhd

29 LISTING OF test_tb.vhd

```
1 -----  
2 --  
3 -- Copyright (C) 2009, 2010 Dr. Juergen Sauermann  
4 --  
5 -- This code is free software: you can redistribute it and/or modify  
6 -- it under the terms of the GNU General Public License as published by  
7 -- the Free Software Foundation, either version 3 of the License, or  
8 -- (at your option) any later version.  
9 --  
10 -- This code is distributed in the hope that it will be useful,  
11 -- but WITHOUT ANY WARRANTY; without even the implied warranty of  
12 -- MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. See the  
13 -- GNU General Public License for more details.  
14 --  
15 -- You should have received a copy of the GNU General Public License  
16 -- along with this code (see the file named COPYING).  
17 -- If not, see http://www.gnu.org/licenses/.  
18 --  
19 -----  
20 -----  
21 --  
22 -- Module Name: alu - Behavioral  
23 -- Create Date: 16:47:24 12/29/2009  
24 -- Description: arithmetic logic unit of a CPU  
25 --  
26 -----  
27 --  
28 library IEEE;  
29 use IEEE.STD_LOGIC_1164.ALL;  
30 use IEEE.STD_LOGIC_ARITH.ALL;  
31 use IEEE.STD_LOGIC_UNSIGNED.ALL;  
32  
33 entity testbench is  
34 end testbench;  
35  
36 architecture Behavioral of testbench is  
37  
38 component avr_fpga  
39     port ( I_CLK_100 : in std_logic;  
40             I_SWITCH : in std_logic_vector(9 downto 0);  
41             I_RX : in std_logic;  
42  
43             Q_7_SEGMENT : out std_logic_vector(6 downto 0);  
44             Q_LEDS : out std_logic_vector(3 downto 0);  
45             Q_TX : out std_logic);  
46 end component;  
47  
48 signal L_CLK_100 : std_logic;  
49 signal L_LEDS : std_logic_vector(3 downto 0);  
50 signal L_7_SEGMENT : std_logic_vector(6 downto 0);  
51 signal L_RX : std_logic;  
52 signal L_SWITCH : std_logic_vector(9 downto 0);  
53 signal L_TX : std_logic;  
54  
55 signal L_CLK_COUNT : integer := 0;  
56  
57 begin
```

29 LISTING OF test_tb.vhd

```
59      fpga: avr_fpga
60      port map(    I_CLK_100    => L_CLK_100,
61                  I_SWITCH     => L_SWITCH,
62                  I_RX         => L_RX,
63
64                  Q_LEDs        => L_LEDs,
65                  Q_7_SEGMENT  => L_7_SEGMENT,
66                  Q_TX          => L_TX);
67
68      process -- clock process for CLK_100,
69      begin
70          clock_loop : loop
71              L_CLK_100      <= transport '0';
72              wait for 5 ns;
73
74              L_CLK_100      <= transport '1';
75              wait for 5 ns;
76          end loop clock_loop;
77      end process;
78
79      process(L_CLK_100)
80      begin
81          if (rising_edge(L_CLK_100)) then
82              case L_CLK_COUNT is
83                  when 0 => L_SWITCH      <= "0011100000";  L_RX <= '0';
84                  when 2 => L_SWITCH(9 downto 8)      <= "11";
85                  when others =>
86                      end case;
87              L_CLK_COUNT      <= L_CLK_COUNT + 1;
88          end if;
89      end process;
90  end Behavioral;
91
```

test/test_tb.vhd

30 LISTING OF avr_fpga.ucf

```
1      NET      I_CLK_100          PERIOD = 10 ns;
2      NET      L_CLK           PERIOD = 45 ns;
3
4      NET      I_CLK_100          TNM_NET = I_CLK_100;
5      NET      L_CLK           TNM_NET = L_CLK;
6
7      NET      I_CLK_100          LOC = AA12;
8      NET      I_RX            LOC = M3;
9      NET      Q_TX            LOC = M4;
10
11     # 7 segment LED display
12     #
13    NET      Q_7_SEGMENT      LOC = V3;
14    NET      Q_7_SEGMENT      LOC = V4;
15    NET      Q_7_SEGMENT      LOC = W3;
16    NET      Q_7_SEGMENT      LOC = T4;
17    NET      Q_7_SEGMENT      LOC = T3;
18    NET      Q_7_SEGMENT      LOC = U3;
19    NET      Q_7_SEGMENT      LOC = U4;
20
21     # single LEDs
22     #
23    NET      Q_LEDS          LOC = N1;
24    NET      Q_LEDS          LOC = N2;
25    NET      Q_LEDS          LOC = P1;
26    NET      Q_LEDS          LOC = P2;
27
28     # DIP switch(0 ... 7) and two pushbuttons (8, 9)
29     #
30    NET      I_SWITCH         LOC = H2;
31    NET      I_SWITCH         LOC = H1;
32    NET      I_SWITCH         LOC = J2;
33    NET      I_SWITCH         LOC = J1;
34    NET      I_SWITCH         LOC = K2;
35    NET      I_SWITCH         LOC = K1;
36    NET      I_SWITCH         LOC = L2;
37    NET      I_SWITCH         LOC = L1;
38    NET      I_SWITCH         LOC = R1;
39    NET      I_SWITCH         LOC = R2;
40
41    NET      I_SWITCH         PULLUP;
42
```

src/avr_fpga.ucf

31 LISTING OF Makefile

```
1      PROJECT=avr_core
2
3      # the vhdl source files (except testbench)
4      #
5      FILES          += src/*.vhd
6
7      # the testbench sources and binary.
8      #
9      SIMFILES        = test/test_tb.vhd
10     SIMFILES        += test/RAMB4_S4_S4.vhd
11     SIMFILES        += test/RAM32X1S.vhd
12     SIMTOP          = testbench
13
14     # When to stop the simulation
15     #
16     # GHDL_SIM_OPT   = --assert-level=error
17     GHDL_SIM_OPT    = --stop-time=40us
18
19     SIMDIR          = simu
20
21     FLAGS           = --ieee=synopsys --warn-no-vital-generic -fexplicit --std=93c
22
23     all:
24         make compile
25         make run 2>& 1 | grep -v std_logic_arith
26         make view
27
28     compile:
29         @mkdir -p simu
30         @echo -----
31         ghdl -i $(FLAGS) --workdir=simu --work=work $(SIMFILES) $(FILES)
32         @echo -----
33         @echo -----
34         ghdl -m $(FLAGS) --workdir=simu --work=work $(SIMTOP)
35         @echo
36         @mv $(SIMTOP) simu/$(SIMTOP)
37
38     run:
39         @$(SIMDIR)/$(SIMTOP) $(GHDL_SIM_OPT) --vcdgz=$(SIMDIR)/$(SIMTOP).vcdgz
40
41     view:
42         gunzip --stdout $(SIMDIR)/$(SIMTOP).vcdgz | gtkwave --vcd gtkwave.save
43
44     clean:
45         ghdl --clean --workdir=simu
46
```

Makefile

32 LISTING OF hello.c

```
1  #include "stdint.h"
2  #include "avr/io.h"
3  #include "avr/pgmspace.h"
4
5  #undef F_CPU
6  #define F_CPU 25000000UL
7  #include "util/delay.h"
8
9
10         //-----//
11         //
12         //      print char cc on UART.          //
13         //      return number of chars printed (i.e. 1).  //
14         //
15         //-----//
16
17         uint8_t
18         uart_putchar(uint8_t cc)
19         {
20             while ((UCSRA & (1      <<UDRE)) == 0)      ;
21             UDR = cc;
22             return 1;
23         }
24
25         //-----//
26         //
27         //      print char cc on 7 segment display.        //
28         //      return number of chars printed (i.e. 1).  //
29         //
30         // The segments of the display are encoded like this:
31         //
32         //
33         //      segment      PORT B
34         //      name        Bit number
35         //      ----A----  ----0----
36         //      |          |    |    |
37         //      F          B    5    1
38         //      |          |    |    |
39         //      ----G----  ----6----
40         //      |          |    |    |
41         //      E          C    4    2
42         //      |          |    |    |
43         //      ----D----  ----3----
44         //
45         //-----//
46
47         #define SEG7(G, F, E, D, C, B, A)      (~G      <
app/hello.c
```

33 LISTING OF make_mem.cc

```
1  #include "assert.h"
2  #include "stdio.h"
3  #include "stdint.h"
4  #include "string.h"
5
6  const char * hex_file = 0;
7  const char * vhdl_file = 0;
8
9  uint8_t buffer[0x10000];
10
11 //-----
12 uint32_t
13 get_byte(const char * cp)
14 {
15     uint32_t value;
16     const char cc[3] = { cp[0], cp[1], 0 };
17     const int cnt = sscanf(cc, "%X", &value);
18     assert(cnt == 1);
19     return value;
20 }
21
22 void
23 read_file(FILE * in)
24 {
25     memset(buffer, 0xFF, sizeof(buffer));
26     char line[200];
27     for (;;)
28     {
29         const char * s = fgets(line, sizeof(line) - 2, in);
30         if (s == 0) return;
31         assert(*s++ == ':');
32         const uint32_t len      = get_byte(s);
33         const uint32_t ah       = get_byte(s + 2);
34         const uint32_t al       = get_byte(s + 4);
35         const uint32_t rectype = get_byte(s + 6);
36         const char * d = s + 8;
37         const uint32_t addr = ah      <<8 | al;
38
39         uint32_t csum = len + ah + al + rectype;
40         assert((addr + len)      <= 0x10000);
41         for (uint32_t l = 0; l      <len; ++l)
42         {
43             const uint32_t byte = get_byte(d);
44             d += 2;
45             buffer[addr + l] = byte;
46             csum += byte;
47         }
48
49         csum = 0xFF & -csum;
50         const uint32_t sum = get_byte(d);
51         assert(sum == csum);
52     }
53 }
54
55 void
56 write_vector(FILE * out, bool odd, uint32_t mem, uint32_t v)
57 {
58     const uint8_t * base = buffer;
```

33 LISTING OF make_mem.cc

```

59
60     // total memory is 2 even bytes, 2 odd bytes, 2 even bytes, ...
61     //
62     if (odd)    base += 2;
63
64     // total memory is 4 kByte organized into 8 memories.
65     // thus each of the 16 vectors covers 256 bytes.
66     //
67     base += v*256;
68
69     // memories 0 and 1 are the low byte of the opcode while
70     // memories 2 and 3 are the high byte.
71     //
72     if (mem >= 2)    ++base;
73
74     const char * px = odd ? "po" : "pe";
75     fprintf(out, "constant %s_%u_%2.2X : BIT_VECTOR := X\"", px, mem, v);
76     for (int32_t d = 63; d >= 0; --d)
77     {
78         uint32_t q = base[4*d];
79         if (mem & 1)    q >= 4;        // high nibble
80         else           q &= 0x0F;      // low nibble
81         fprintf(out, "%X", q);
82     }
83
84     fprintf(out, "\";\r\n");
85 }
86 //-----
87 void
88 write_mem(FILE * out, bool odd, uint32_t mem)
89 {
90     const char * px = odd ? "po" : "pe";
91
92     fprintf(out, "-- content of %s_%u -----"
93             "-----\r\n", px, mem);
94
95     for (uint32_t v = 0; v < 16; ++v)
96         write_vector(out, odd, mem, v);
97
98     fprintf(out, "\r\n");
99 }
100 //-----
101 void
102 write_file(FILE * out)
103 {
104     fprintf(out,
105     "\r\n"
106     "library IEEE;\r\n"
107     "use IEEE.STD_LOGIC_1164.all;\r\n"
108     "\r\n"
109     "package prog_mem_content is\r\n"
110     "\r\n");
111
112     for (uint32_t m = 0; m < 4; ++m)
113         write_mem(out, false, m);
114
115     for (uint32_t m = 0; m < 4; ++m)
116         write_mem(out, true, m);
117
118     fprintf(out,
119     "end prog_mem_content;\r\n"
120     "\r\n");

```

33 LISTING OF make_mem.cc

```
121     }
122 //-----
123 int
124 main(int argc, char * argv[])
125 {
126     if (argc > 1)    hex_file = argv[1];
127     if (argc > 2)    vhdl_file = argv[2];
128
129     FILE * in = stdin;
130     if (hex_file)    in = fopen(hex_file, "r");
131     assert(in);
132     read_file(in);
133     fclose(in);
134
135     FILE * out = stdout;
136     if (vhdl_file)   out = fopen(vhdl_file, "w");
137     write_file(out);
138     assert(out);
139 }
140 //-----
```

tools/make_mem.cc

34 LISTING OF end_conv.cc

```
1 #include "assert.h"
2 #include "ctype.h"
3 #include "stdio.h"
4 #include "string.h"
5
6 //-----
7 int
8 main(int argc, const char * argv)
9 {
10 char buffer[2000];
11 int pc, val, val2;
12
13     for (;;)
14     {
15         char * s = fgets(buffer, sizeof(buffer) - 2, stdin);
16         if (s == 0)    return 0;
17
18         // map lines ' xx:' and 'xxxxxxxx' to 2* the hex value.
19         //
20         if (
21             (isxdigit(s[0]) || s[0] == ' ') &&
22             (isxdigit(s[1]) || s[1] == ' ') &&
23             (isxdigit(s[2]) || s[2] == ' ') &&
24             isxdigit(s[3]) && s[4] == ':') // ' xx:'
25         {
26             assert(1 == sscanf(s, "%x:", &pc));
27             if (pc & 1)      printf("%4X+:", pc/2);
28             else            printf("%4X:", pc/2);
29             s += 5;
30         }
31         else if (isxdigit(s[0]) && isxdigit(s[1]) && isxdigit(s[2]) &&
32                 isxdigit(s[3]) && isxdigit(s[4]) && isxdigit(s[5]) &&
33                 isxdigit(s[6]) && isxdigit(s[7])) // 'xxxxxxxx'
34         {
35             assert(1 == sscanf(s, "%x", &pc));
36             if (pc & 1)    printf("%8.8X+:", pc/2);
37             else           printf("%8.8X:", pc/2);
38             s += 8;
39         }
40         else // other: copy verbatim
41         {
42             printf("%s", s);
43             continue;
44         }
45
46         while (isblank(*s))    printf("%c", *s++);
47
48         // endian swap.
49         //
50         while (isxdigit(s[0]) &&
51                 isxdigit(s[1]) &&
52                     s[2] == ' ' &&
53                     isxdigit(s[3]) &&
54                     isxdigit(s[4]) &&
55                     s[5] == ' ')
56         {
57             assert(2 == sscanf(s, "%x %x ", &val, &val2));
58             printf("%2.2X%2.2X ", val2, val);
59         }
60     }
61 }
```

34 LISTING OF end_conv.cc

```
59             s += 6;
60         }
61
62         char * s1 = strstr(s, ".+");
63         char * s2 = strstr(s, "-");
64         if (s1)
65         {
66             assert(1 == sscanf(s1 + 2, "%d", &val));
67             assert((val & 1) == 0);
68             sprintf(s1, " 0x%X", (pc + val)/2 + 1);
69             printf(s);
70             s = s1 + strlen(s1) + 1;
71         }
72         else if (s2)
73         {
74             assert(1 == sscanf(s2 + 2, "%d", &val));
75             assert((val & 1) == 0);
76             sprintf(s2, " 0x%X", (pc - val)/2 + 1);
77             printf(s);
78             s = s2 + strlen(s2) + 1;
79         }
80         printf("%s", s);
81     }
82 //-----
```

tools/end_conv.cc