 


Digital Systems and Microprocessor Design (H7068)




8.2. Inside UoS Educational Processor

Daniel Roggen
d.roggen@sussex.ac.uk



Architecture

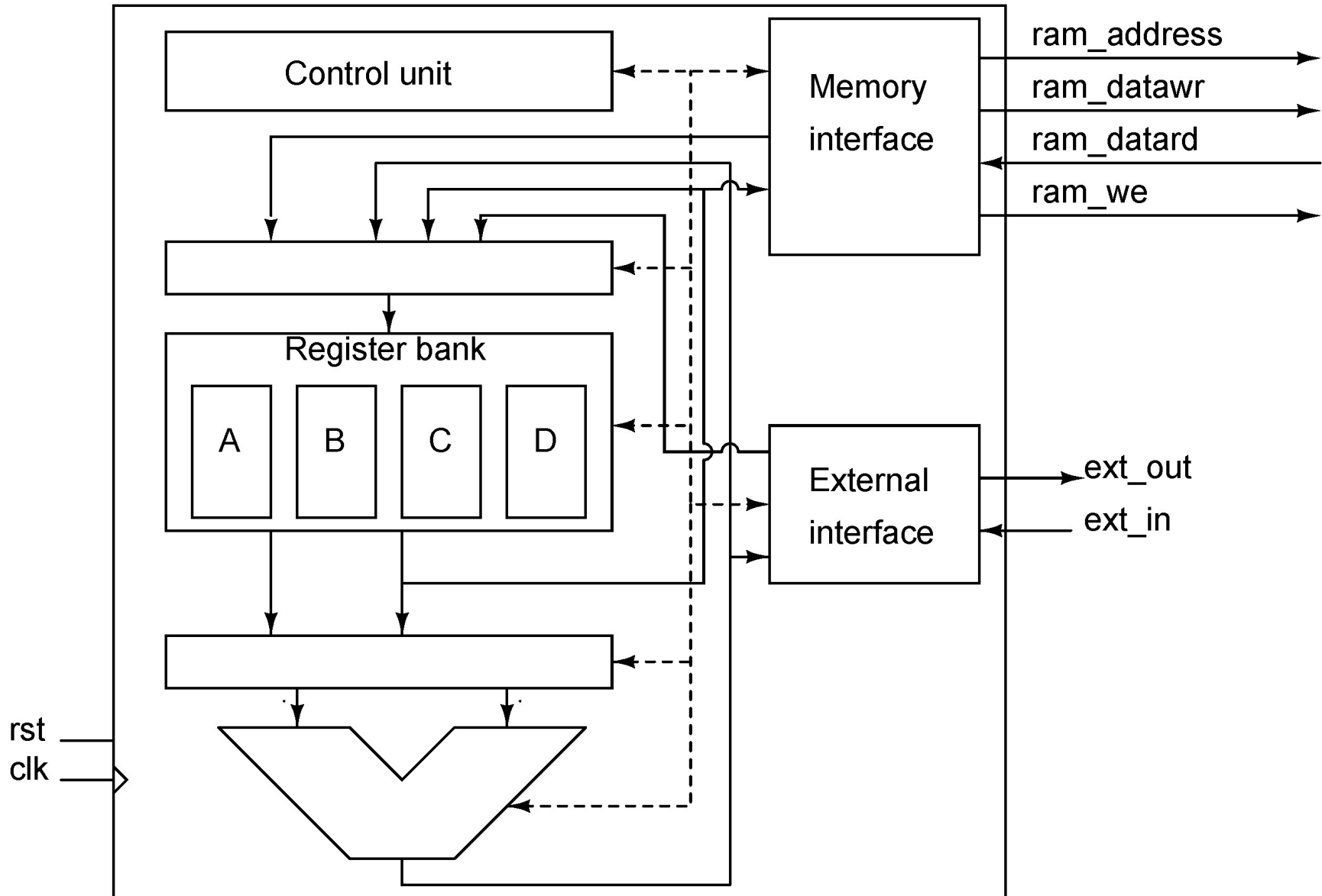




VHDL files

- `cpu.vhd`: top file for CPU
- `cpusequencer.vhd`: fetch/execute sequence
- `cpuregbank.vhd`: register file
- `cpualu.vhd`: ALU



Fetch/Execute sequence

 


	Address	Content
Memory dump:	0:	10
	1:	23
	2:	30
	3:	15

- 3 clock cycles per instruction
 - Fetch high
 - Fetch low
 - Execute...
- Circuit must organize this sequence



Fetch/Execute sequence

- In cpusequencer.vhd

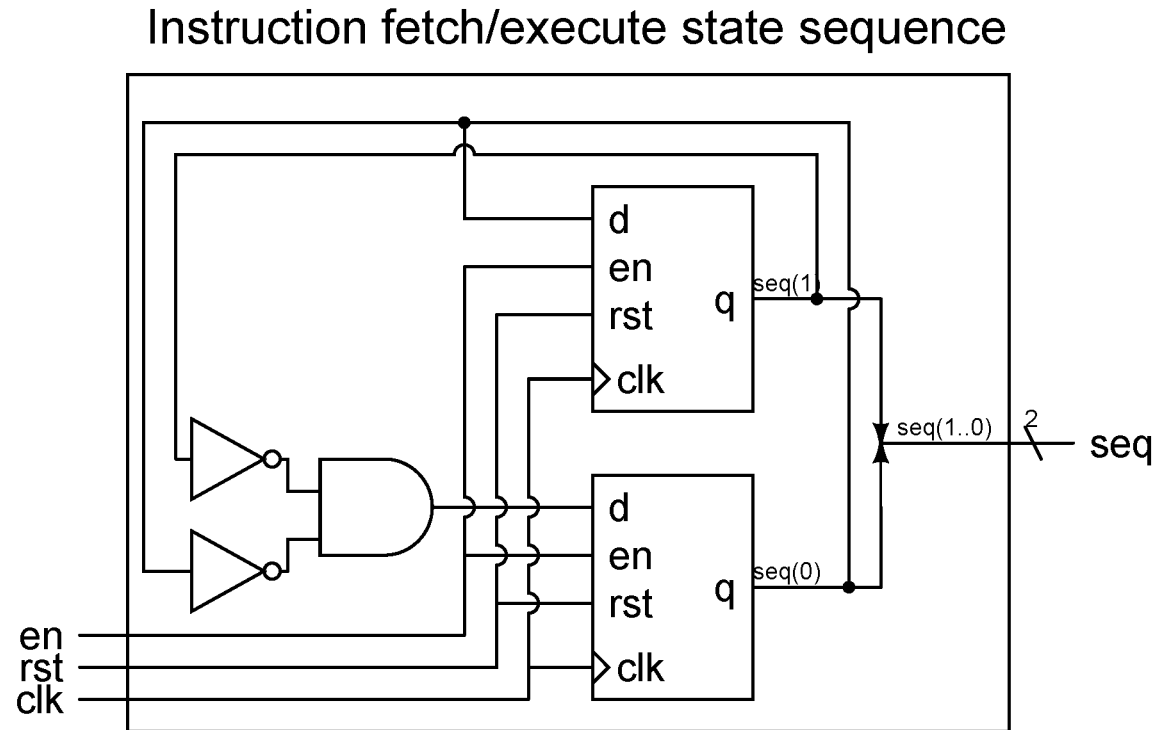

- Up counter until 2 (10b): 00=fetchh, 01=fetchl, 10=exec



Fetch/Execute sequence

```
entity cpusequencer is
  port(
    clk : in STD_LOGIC;
    rst : in STD_LOGIC;
    en : in STD_LOGIC;
    seq : out STD_LOGIC_VECTOR(1 downto 0)
  );
end cpusequencer;
```

- **clk:** clock
- **rst:** reset
- **en:** enable (currently not used: always wired to 1)
- **seq:** 2-bit code for fetchh, fetchl, exec



Fetch/Execute sequence

```
process (clk)
```

clock in sensitivity list

```
begin
```

```
  if rising_edge(clk) then
```

All happens on rising clock edge

```
    if rst='1' then
```

```
      s<="00";
```

Reset

```
    else
```

Normal behavior: if enabled, increment and wrap around at 2

```
      if en='1' then
```

```
        if s="10" then
```

```
          s <= "00";
```

```
        else
```

```
          s <= s+1;
```

```
        end if;
```

```
      end if;
```

```
    end if;
```

```
  end if;
```


```
end process;
```

```
seq <= s;
```

- VHDL does additions with '+'!
- Not taught in this module.
- Synthesizer chooses an implementation on its own
- Choice not critical here with 2 bits; with more bits specific adder architectures may be preferred



Register file (register bank)

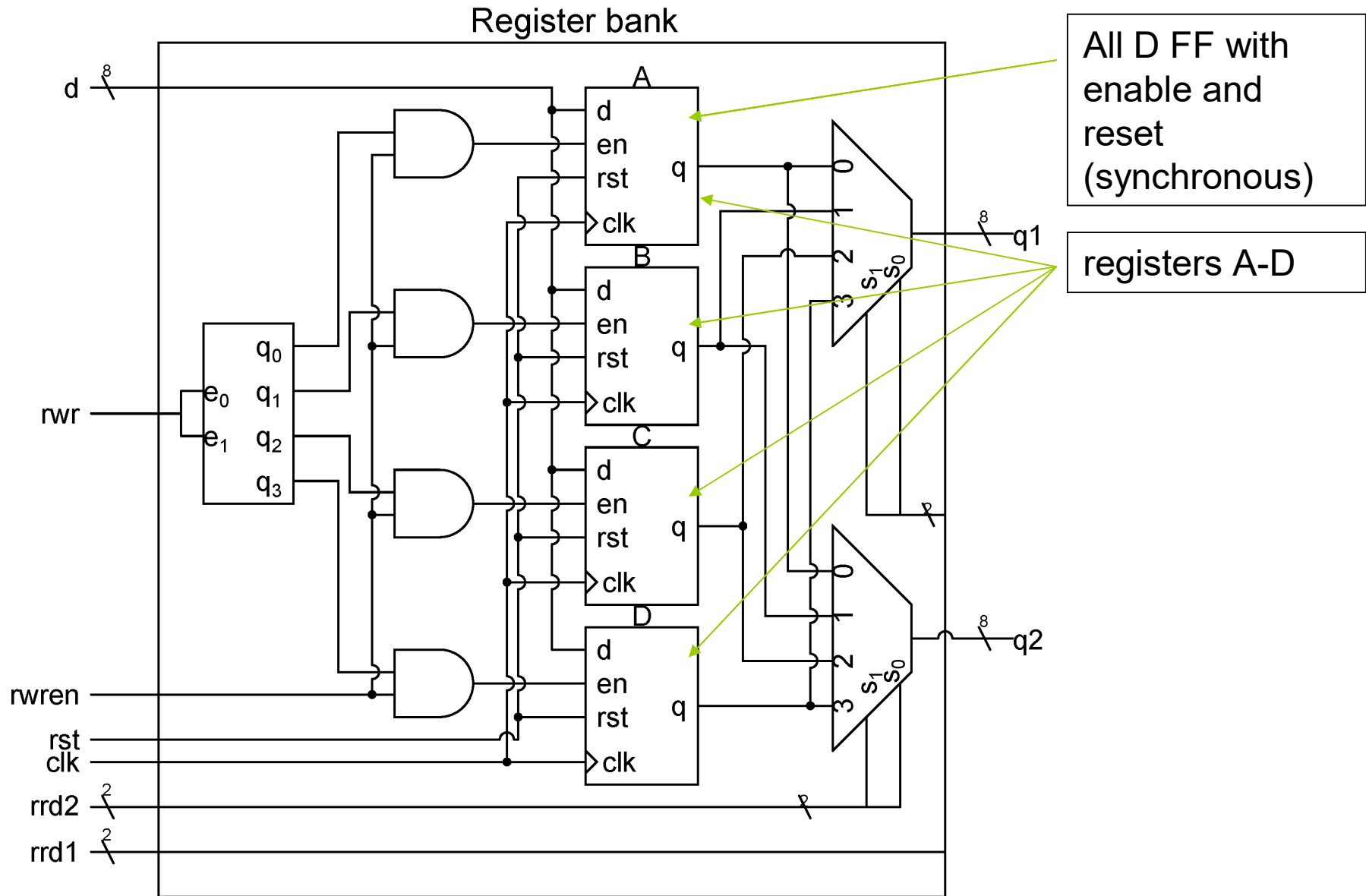



Register file (register bank)

- Reminder: move instruction
- Always operation between **dst** and **src**, with result in **dst**
- Let's consider what to read from our register bank:
 - The register defined by **dst** and **src** (even if we deal with an immediate-this is handled elsewhere)

Instructions	instruction (15..8)						Instruction (7..0)									
	Opcode				dd#m	sd#m	dreg		src							
<code>mov r, r</code>	0	0	0	0	0	0	r	r	-	-	-	-	-	-	r	r
<code>mov r, i</code>	0	0	0	1	0	0	r	r	i	i	i	i	i	i	i	i
<code>mov r, [r]</code>	0	0	0	0	0	1	r	r	-	-	-	-	-	-	r	r
<code>mov r, [i]</code>	0	0	0	1	0	1	r	r	i	i	i	i	i	i	i	i
<code>mov [r], r</code>	0	0	0	0	1	0	r	r	-	-	-	-	-	-	r	r
<code>mov [r], i</code>	0	0	0	1	1	0	r	r	i	i	i	i	i	i	i	i



Register file (register bank)

```
entity cpuregbank is
```

```
  port(
```

```
    clk : in STD_LOGIC;
```

```
    rrd1 : in STD_LOGIC_VECTOR(1 downto 0);
```

```
    rrd2 : in STD_LOGIC_VECTOR(1 downto 0);
```

```
    rwr : in STD_LOGIC_VECTOR(1 downto 0);
```

```
    rwren : in STD_LOGIC;
```

```
    rst : in STD_LOGIC;
```

```
    d : in STD_LOGIC_VECTOR(7 downto 0);
```

```
    q1 : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    q2 : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    -- Only for debugging
```

```
    dbg_qa : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    dbg_qb : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    dbg_qc : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    dbg_qd : out STD_LOGIC_VECTOR(7 downto 0);
```

```
  );
```

```
end cpuregbank;
```

register to read from
(the 2 bits come from
src or dst in the
instruction!)

register to write to
(always dst)

rwren: enable write
d: data to write

outputs of the register
bank

This would not be here
in a "production"
processor: here to
display the content of
the register on the 7
segment display



Register file (register bank)

architecture Behavioral of cpuregbank is

```
signal enables: STD_LOGIC_VECTOR(3 downto 0);  
signal qa,qb,qc,qd: STD_LOGIC_VECTOR(7 downto 0);
```

begin

```
ra: entity work.dffre generic map (N=>8) port  
map (clk=>clk,en=>enables(0),rst=>rst,d=>d,q=>qa);
```

```
rb: entity work.dffre generic map (N=>8) port  
map (clk=>clk,en=>enables(1),rst=>rst,d=>d,q=>qb);
```

```
rc: entity work.dffre generic map (N=>8) port  
map (clk=>clk,en=>enables(2),rst=>rst,d=>d,q=>qc);
```

```
rd: entity work.dffre generic map (N=>8) port  
map (clk=>clk,en=>enables(3),rst=>rst,d=>d,q=>qd);
```

enable each register
q: output of each
register

Instantiate a register
with reset and enable.

Generic map:
parameterized register.



Register file (register bank)

2-4 decoder: when write is enabled one of the register is enabled for write

```
with rwr select
    enables <="0001" and rwren&rwren&rwren&rwren when "00",
            "0010" and rwren&rwren&rwren&rwren when "01",
            "0100" and rwren&rwren&rwren&rwren when "10",
            "1000" and rwren&rwren&rwren&rwren when others;
```

```
with rrd1 select
    q1 <=    qa when "00",
            qb when "01",
            qc when "10",
            qd when others;
```

first output multiplexer

```
with rrd2 select
    q2 <=    qa when "00",
            qb when "01",
            qc when "10",
            qd when others;
```

second output multiplexer



Register

```
entity dffre is
```

```
  generic (N : integer);
```

```
  port(
```

```
    clk : in STD_LOGIC;
```

```
    en  : in STD_LOGIC;
```

```
    rst: in STD_LOGIC;
```

```
    d  : in STD_LOGIC_VECTOR(N-1 downto 0);
```

```
    q  : out STD_LOGIC_VECTOR(N-1 downto 0)
```

```
  );
```

```
end dffre;
```

generic: useful to create components that can be parameterized

Here N is the number of bits of the D flip-flop



Register

architecture Behavioral of dffre is
begin

```
process (clk)
```

```
begin
```

```
    if rising_edge(clk) then
```

all on rising edge

```
        if rst='1' then
```

```
            q<=(others=>'0');
```

synchronous reset

```
        else
```

```
            if en='1' then
```

```
                q<=d;
```

copy if enabled

```
            end if;
```

```
        end if;
```

```
    end if;
```

```
end process;
```




VHDL generic

In the component declaration:


```
entity entity_name is
    generic (generic list);
    port (port list);
end entity_name;
```

In the component instantiation:
 
```
label: entity work.comp_name
    generic map (generic_association_list)
    port map (port_association_list);
```



ALU

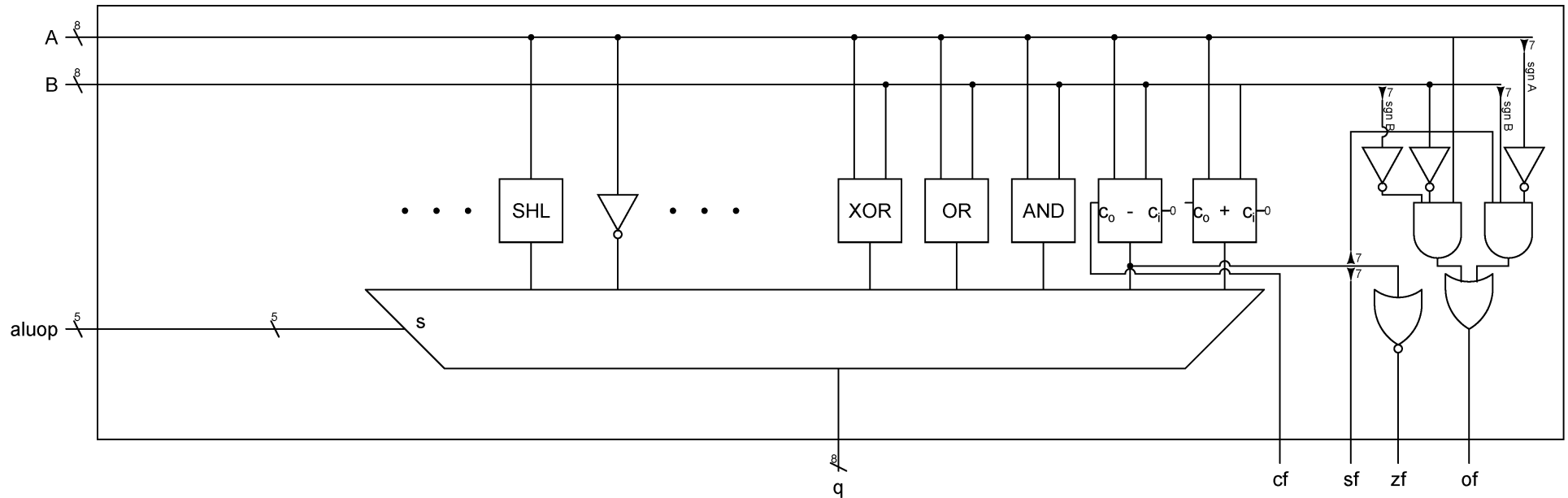

- A, B: input of the ALU (8 bits)
- **aluop: operation to perform** (5 bits)
 - bit 14 to bit 10 of instruction to identify the type of operation
 - (part opcode and part other bits of the instruction)
- Implemented as **multiplexer**
- flags as discrete logic



ALU

Instructions	instruction (15..8)						Instruction (7..0)									
ALU 2 op	opcode			\bar{R}/I	ALU op		dreg		src							
add r, r	0	0	1	0	0	0	r	r	-	-	-	-	-	-	r	r
add r, i	0	0	1	1	0	0	r	r	i	i	i	i	i	i	i	i
xor r, r	0	1	0	0	0	0	r	r	-	-	-	-	-	-	r	r

Test	opcode			\bar{R}/I	ALU op		dreg		immedite / reg							
cmp r, r	0	1	0	0	0	1	r	r	-	-	-	-	-	-	r	r
cmp r, i	0	1	0	1	0	1	r	r	i	i	i	i	i	i	i	i

Instructions	instruction (15..8)						Instruction (7..0)									
ALU 1 op	opcode			ALU op			dreg									
not r	0	1	1	0	0	0	r	r	-	-	-	-	-	-	-	-
shr r	0	1	1	0	0	1	r	r	-	-	-	-	-	-	-	-
...																

Only the bits in red are necessary to define the ALU operation!



ALU

```
entity cpualu is
```

```
  port (
```

```
    clk : in STD_LOGIC;
```

```
    rst : in STD_LOGIC;
```

```
    op  : in STD_LOGIC_VECTOR(4 downto 0);
```

```
    a   : in STD_LOGIC_VECTOR(7 downto 0);
```

```
    b   : in STD_LOGIC_VECTOR(7 downto 0);
```

```
    q   : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    f   : out STD_LOGIC_VECTOR(3 downto 0)
```

```
  );
```

```
end cpualu;
```

Input A,B

Output

Flags

- Flags are always returned, but only used if the instruction is "cmp": control unit stores the flag in a flag register



ALU

```
r <= a+b when op(4 downto 3)="01" and op(1 downto 0)="00" else
     sub(7 downto 0) when op(4 downto 3)="01" and op(1 downto 0)="01" else
     a and b when op(4 downto 3)="01" and op(1 downto 0)="10" else
     a or b when op(4 downto 3)="01" and op(1 downto 0)="11" else
     a xor b when op(4 downto 3)="10" and op(1 downto 0)="00" else
     not a when op(4 downto 0)="11000" else
     '0' & a(7 downto 1) when op(4 downto 0)="11001" else
     a(0) & a(7 downto 1) when op(4 downto 0)="11010" else
     a(7) & a(7 downto 1) when op(4 downto 0)="11011" else
     a(6 downto 0) & a(7) when op(4 downto 0)="11100" else
     "00000000";
```

- Multiplexer
- Can you recognize an instruction?
- Add is 001000rr -----rr
- or 001100rr iiiiiiiii
- (in red op)
- Therefore we react is op(4..3)=01 and op(1..0)=00



ALU

```
sf <= sub(7);  
zf <= not(sub(7) or sub(6) or sub(5) or sub(4) or sub(3) or sub(2) or sub(1) or  
sub(0));  
cf <= sub(8);  
ovf <= (not a(7) and b(7) and sub(7)) or (a(7) and not b(7) and not sub(7));
```

```
f<=zf&ovf&cf&sf;  
q<=r;
```

Combine flags in a
vector

- **Sign** flag is bit 7 of the subtraction
- **Zero** flag obtained by oring
- **Carry** flag is bit 8 of the subtraction (only 8 bits are returned but subtraction done on 9 bits to obtain the carry)
- **Overflow** flag: triggers when the result flips sign:
 - positive minus negative must give positive
 - negative minus positive must give negative
 - Otherwise it's an overflow



Top level CPU entity

```
entity cpu is
```

```
  generic(N : integer);
```

```
  port(
```

```
    clk : in STD_LOGIC;
```

```
    rst : in STD_LOGIC;
```

External interface

```
    ext_in : in STD_LOGIC_VECTOR(7 downto 0);
```

```
    ext_out : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    ram_we : out STD_LOGIC;
```

```
    ram_address : out STD_LOGIC_VECTOR(N-1 downto 0);
```

```
    ram_datawr : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    ram_datard : in STD_LOGIC_VECTOR(7 downto 0);
```

```
    -- Only for debugging
```

```
    dbg_qa : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    dbg_qb : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    dbg_qc : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    dbg_qd : out STD_LOGIC_VECTOR(7 downto 0);
```

```
    dbg_instr : out STD_LOGIC_VECTOR(15 downto 0);
```

```
    dbg_seq : out STD_LOGIC_VECTOR(1 downto 0);
```

```
    dbg_flags : out STD_LOGIC_VECTOR(3 downto 0)
```

Memory interface

```
  );
```

```
end cpu;
```



CPU: instantiating the register bank

```
comp_regs: entity work.cpuregbank port map (
```

```
  clk=>clk, rst=>rst,
```

```
  rrd1=>instruction(9 downto 8),
```

```
  rrd2=>instruction(1 downto 0),
```

1st register is "dst"
2nd register is "src"

```
  rwr=>instruction(9 downto 8),
```

write register is "dst "

```
  rwren=>regwren,
```

```
  d=>wrdata,
```

Controls the write

```
  q1=>reg1out, q2=>reg2out) ;
```

1st and 2nd register
output

- The **instruction set** is designed to help the control unit
- Source and destination **always in the same location** in the instruction
 - **reg1out** is the value in the "dst" register
 - **reg2out** is the value in the "src" register
- It does not hurt to "wire up" src and dst to the register bank, even if the instruction does not use src/dst (the control unit handles that)
- Write only occurs with a **Move** or an **ALU** instruction!



CPU: instantiating fetch/execute

```
comp_seq: entity work.cpusequencer port  
  map (clk=>clk, rst=>rst, en=>'1', seq=>seq) ;
```

```
fetchh <=      '1' when seq="00" else  
              '0' ;  
fetchl <=      '1' when seq="01" else  
              '0' ;  
execute <=    '1' when seq="10" else  
              '0' ;  
fetch <= fetchl or fetchh;
```

Helper signals - not mandatory but makes reading simpler



CPU: fetch instruction

```
comp_instrh: entity work.dffre generic map(N=>8)
  port map(clk=>clk,rst=>rst,en=>fetchh,d=>ram_datard,
  q=>instruction(15 downto 8));

comp_instrl: entity work.dffre generic map(N=>8) port
  map(clk=>clk,rst=>rst,en=>fetchl,d=>ram_datard,
  q=>instruction(7 downto 0));
```

- instruction is the **16-bit instruction read from memory**
- It is 16-bit register realized by **two 8-bit D flip-flops**
- First flip-flop enabled on "fetch high"
- Second flip-flop enabled on "fetch low"



CPU: Program counter / instruction pointer

```
comp_ip: entity work.dffre generic map(N=>N) port
  map (clk=>clk, rst=>rst, en=>'1', d=>ipnext, q=>ip);

  ipnext <= ip+1 when fetch='1' else
    ip when jump='0' else
    jumpip;
```

- `ip` is the address where the instruction is read from
- N-bit `D flip-flop`
 - In the laboratory N is 5 bits (0...1F). It's a Design choice
- `ipnext` is the input of the D flip-flop



CPU: Program counter / instruction pointer

```
comp_ip: entity work.dffre generic map(N=>N) port
  map (clk=>clk, rst=>rst, en=>'1', d=>ipnext, q=>ip) ;

  ipnext <= ip+1 when fetch='1' else
    ip when jump='0' else
    jumpip;
```

- **When** to write: at each clock cycle!
- **What** to write:
 - Fetch (high or low): ipnext = ip+1
 - Exec:
 - ipnext does not change if the instruction is not a jump
 - ipnext changes if it is an absolute jump, or a conditional jump with the condition valid
 - (indicated by the signal jump)



CPU: Jump

Instructions	instruction (15..8)								Instruction (7..0)							
Jump Unsigned: JA, JAE, JB, JBE	opcode			\overline{R} / I	Jump type				immedite / reg							
jmp r	1	0	1	0	0	0	0	0	-	-	-	-	-	-	r	r
jmp i	1	0	1	1	0	0	0	0	i	i	i	i	i	i	i	i
je/jz r	1	0	1	0	0	0	0	1	-	-	-	-	-	-	r	r
je/jz i	1	0	1	1	0	0	0	1	i	i	i	i	i	i	i	i
jne/jnz r	1	0	1	0	1	0	0	1	-	-	-	-	-	-	r	r
jne/jnz i	1	0	1	1	1	0	0	1	i	i	i	i	i	i	i	i
ja r	1	0	1	0	0	0	1	0	-	-	-	-	-	-	r	r
ja i	1	0	1	1	0	0	1	0	i	i	i	i	i	i	i	i
jb r	1	0	1	0	1	0	1	1	-	-	-	-	-	-	r	r
jb i	1	0	1	1	1	0	1	1	i	i	i	i	i	i	i	i

- Unconditional jumps for 101x000 only
- Address is register or immediate: it is **source** defined before



CPU: Jump

```
jumpip <= source(N-1 downto 0);
```

Where to jump if we were to do it

```
jump <= '1' when instruction(15 downto 13) = "101" and  
      jumpconditionvalid='1' else  
      '0';
```

jump if there is a jump instruction
and the jump condition is valid

```
jumpconditionvalid <=
```

```
'1' when instruction(11 downto 8) = "0000" else
```

```
-- je/jz
```

always valid (unconditional jump)

```
'1' when instruction(11 downto 8) = "0001" and zf='1' else
```

```
-- jne/jnz
```

```
'1' when instruction(11 downto 8) = "1001" and zf='0' else
```

Conditional jump when not zero:
check the zero flag

```
-- ja
```

```
'1' when instruction(11 downto 8) = "0010" and zf='0' and  
cf='0' else
```

```
-- jb
```

```
'1' when instruction(11 downto 8) = "1011" and zf='0' and  
cf='1'
```

```
else '0';
```



CPU: source (helper signal)

```
source <= reg2out when instruction(12)='0' else  
        instruction(7 downto 0);
```

- Many instructions use a "source": Move, ALU, Jump, out
- All these instructions use as source:
 - an **immediate** in the lower 8 bits of the instruction if R#/I=1
 - a **register** (output of the register bank) if R#/I=0
- R#/I is always instruction(12)
- source takes care of providing the right source (immediate or register) using a **multiplexer**
 - Either the immediate
 - or the 2nd output of register bank (src)



CPU: when to write to register

- **regwren**: helper signal indicating **when to write** to register (register file)
- **Write to register** only during **execute cycle**
- **And**:
 - The instruction is a **Move**
 - Or the instruction is **ALU** (but **not "cmp"**)
 - Or the instruction is **ln**

```
execute=1 and (  
  (instr(15..13)=000 and instr(11)=0) or  
  instr(15..13)=001 or  
  (instr(15..13)=010 and instr(11..10) /= 01)  
  instr(15..13)=011  
)
```



CPU: what to write

- **wrdata**: helper signal containing the **data to write**:
 - Data for **memory** and **register write**
 - wrdata is **connected** to the **register bank write input**!
- What to write:
 - **Move direct** instruction: the data to write is "source" (either immediate or register)
 - **Move from memory** instr.: write what the memory chip provides
 - **ALU instruction**: write the output of the ALU
 - **In instruction**: write what is on the input of the external interface

```
wrdata =  
  source when instr(15..10)=000X00  
  ram_datard when instr(15..10)=000X01  
  aluqout when instr(15..13)=001  
  aluqout when instr(15..13)=010  
  aluqout when instr(15..13)=011  
  ext_in when instr(15..10)=110X01
```



CPU: memory interface

- **What** to write (put on the data bus)?
 - wrdata always
- What to put on the **address** bus?
- **When** to write?



CPU: memory interface

```
ram_address <=
  ip when fetch='1' else
  reg2out(N-1 downto 0) when instruction(15 downto 10)="000001" else
  instruction(N-1 downto 0) when instruction(15 downto 10)="000101" else
  reg1out(N-1 downto 0) when instruction(15 downto 10)="000010" else
  reg1out(N-1 downto 0) when instruction(15 downto 10)="000110" else
  (others=>'0');
```

- Address:
 - IP during the **fetch** cycles
 - The content of the **src register** or of the **immediate** for a move **from** memory
 - the content of the **dst register** for a move **to** memory
 - Otherwise zero
 - Explains why the first CPU lab showed always a zero on the address!



CPU: when to write to memory?

- Move to memory during the **exec** cycle:
 - mov [b],23h

```
ram_we <=
  '1' when execute='1' and instruction(15 downto 13)="000"
  and instruction(11 downto 10)="10"
  else '0';
```



CPU: External interface

- External interface output is an 8-bit D flip-flop
- **When** to write: during exec when instruction is "out"
- **What** to write: source (i.e. register or immediate)

```
comp_regextout :
```

```
entity work.dffre generic map (N=>8)
```

```
port map (clk=>clk, rst=>rst, en=>ext_wren,  
d=>source, q=>ext_out) ;
```

```
ext_wren <=
```

```
'1' when execute='1' and instruction(15 downto 13) =  
"110" and instruction(11 downto 10)="00"  
else '0' ;
```





CPU: flags

- SF, CF, OF, ZF are stored in a 4-bit D flip-flop
- **When** to write: during exec and "cmp" instruction
- **What** to write: the flag output of the ALU

```
comp_flags:    entity work.dffre
  generic map(N=>4)
  port map(clk=>clk, rst=>rst, en=>flagwren, d=>alufout, q=>flags);
```

```
flagwren <= '1' when execute='1' and instruction(15 downto
  13)="010" and instruction(11 downto 10)="01"
  else '0';
```

CPU

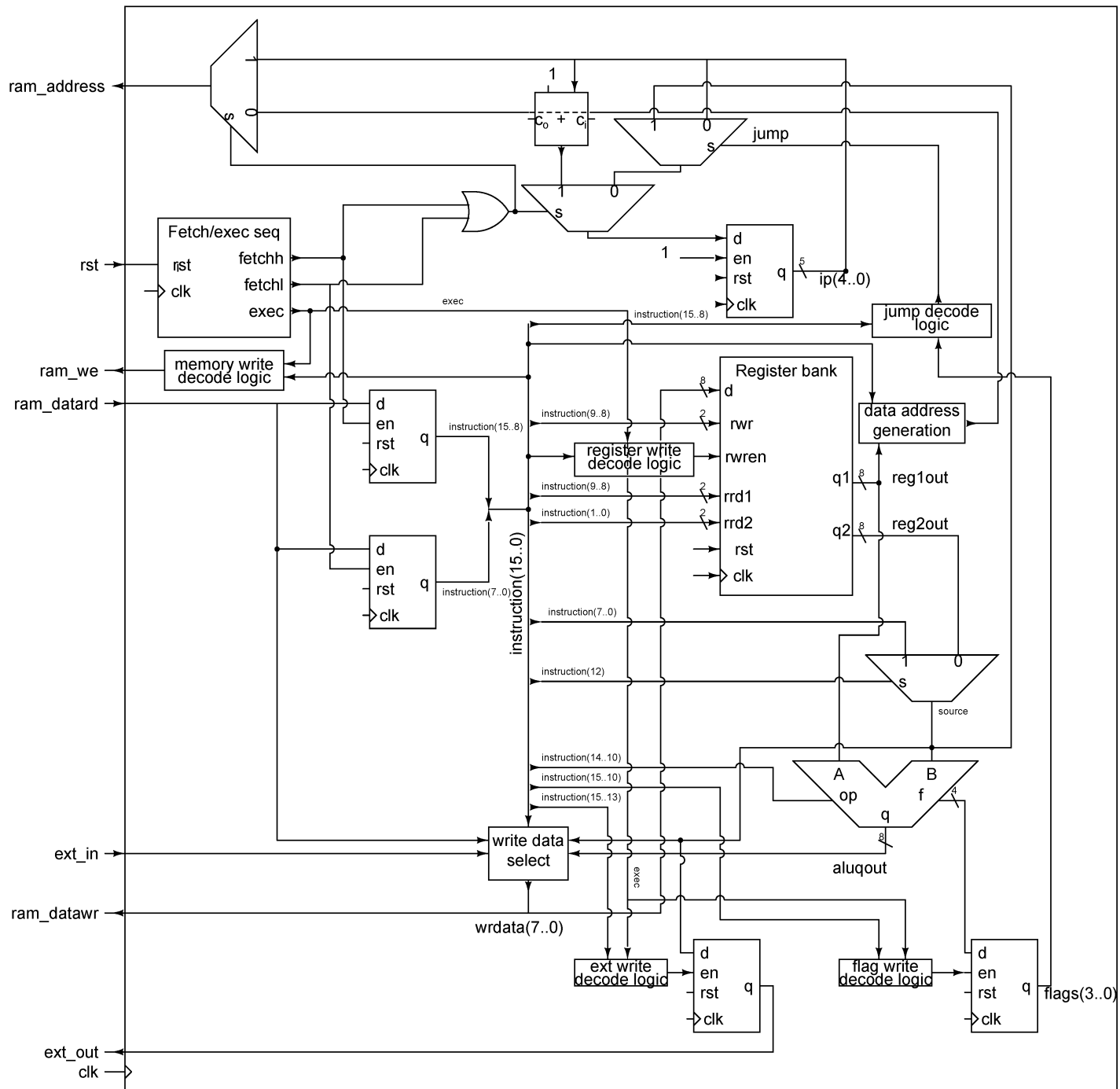 



Jump decode logic

```
instr(15..13)=101 and  
instr(11..8)=0000 or  
(instr(11..8)=0001 and zf=1) or  
(instr(11..8)=1001 and zf=0)  
)
```

Register write decode logic

```
execute=1 and (  
(instr(15..13)=000 and instr(11)=0) or  
instr(15..13)=001 or  
(instr(15..13)=010 and instr(11..10) /= 01)  
instr(15..13)=011  
)
```

Memory write decode logic

```
execute=1 and instr(15..10)=000X10
```

External write decode logic

```
execute=1 and instr(15..13)=110
```

Flag write decode logic

```
execute=1 and instr(15..10)=010X01
```

Write data select

```
wrdata =  
source when instr(15..10)=000X00  
ram_datard when instr(15..10)=000X01  
aluqout when instr(15..13)=001  
aluqout when instr(15..13)=010  
aluqout when instr(15..13)=011  
ext_in when instr(15..10)=110X01
```

Data address generation

```
address =  
reg1out when instr(15..10)=000001  
instr(7..0) when instr(15..10)=000101  
reg1out when instr(15..10)=000010  
reg1out when instr(15..10)=000110
```



Summary

- Brief insight into the processor architecture
- Basic understanding of the control unit function:
 - deciding what and when to "store" data in register
- Sufficient knowledge to perform the coursework assignment on:
 - Modifying the instruction set (adding instruction)
 - Tracing the state of key signals for a given instruction